

D 71639
\$2.25


70p
202

July 1982

Electronics & Computing

MONTHLY

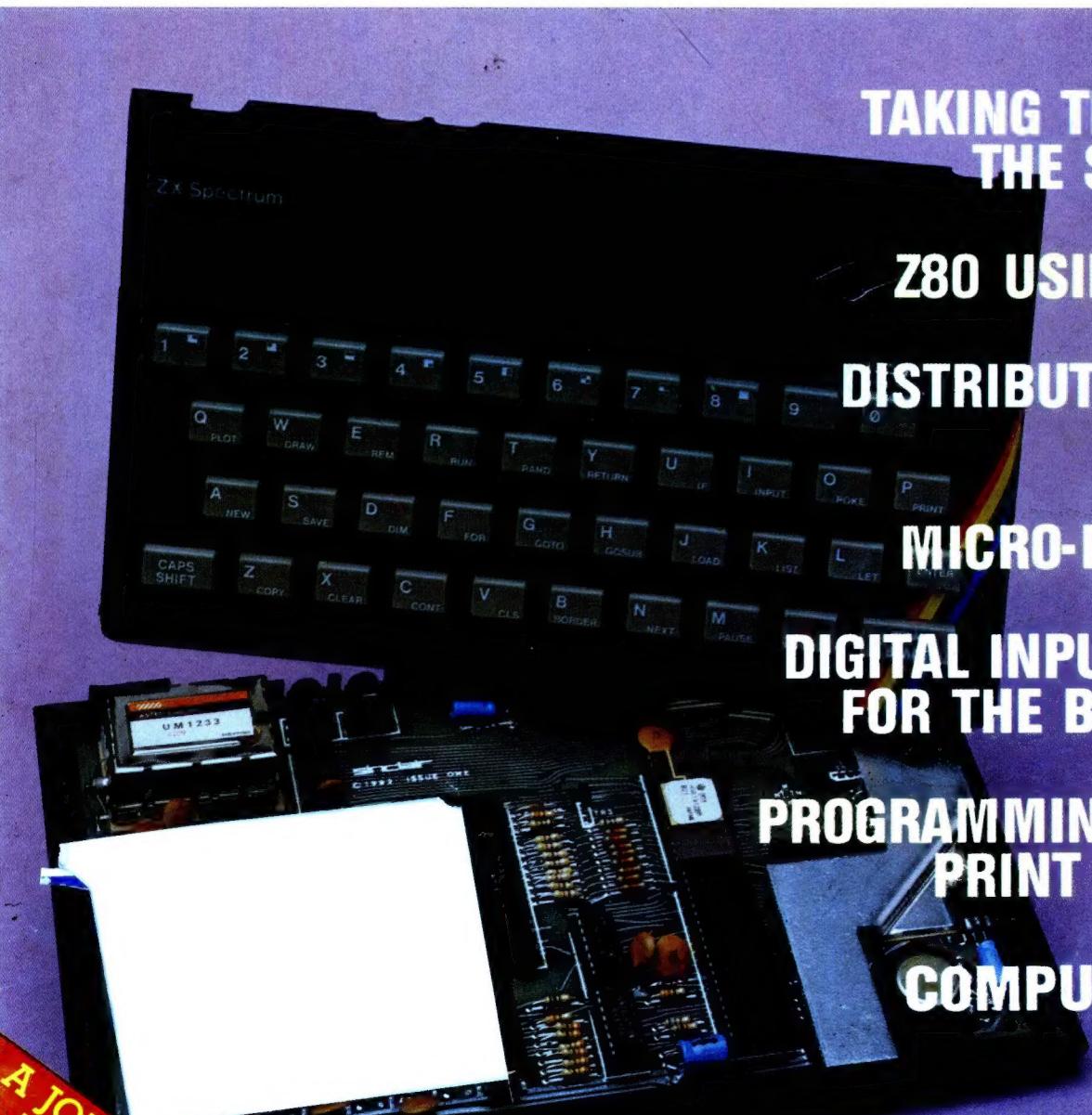Britain's First Electronics & Computer Applications Magazine



TAKING THE LID OFF
THE SPECTRUM

Z80 USING MENTA

DISTRIBUTION - ZX81

NASCOM
MICRO-ED REVIEW

DIGITAL INPUT/OUTPUT
FOR THE BBC MICRO

PROGRAMMING A HAND
PRINT TERMINAL

COMPUTER AIDED
DESIGN

PRINTERFACING THE ATOM

A JOURNEY TO
THE STARS

3D COMPUTERS



+17 FREE PROGRAMS
+BASIC COURSE

£475

MZ-80B
£995

PC-3201
£1,350



PERIPHERALS ADD-ONS PROGRAMS
AVAILABLE EX-STOCK

SURBITON COMPUTER SHOP ON THE A3.
KINGSTON-BY-PASS, 230 TOLWORTH RISE SOUTH,
TOLWORTH, SURBITON, SURREY. **01-337 4317**

WATFORD'S LARGEST NASCOM DEALER

We offer the complete range of fully assembled systems as well as kits, plus additional memory cards — IO Boards — Single Stroke Dual Disc Drives — Monitors, etc.

- We provide complete software support including bespoke programming by our own programs.

The satisfied client is the most important factor for our company and we enjoy using our breadth of experience to arrive at a solution suited specifically to each individual client or customer.

ZX80

JRS SOFTWARE

19 WAYSIDE AVENUE, WORTHING, SUSSEX, BN13 3JU
TELEPHONE WORTHING 65891 (Evenings and Weekends only)

ZX81

As reviewed in 'YOU' COMPUTER'

March, 1982

16K RAM PACK

£29.95 (\$59.95)

Quite simply the best available
+FREE Alien Attack (7K M/Code)
on cassette — value £6.75



Fully built, tested and guaranteed.
Uses existing power supply (min. 600 m.s.).

Compatible with printer.

No wobble problems.

Gold plated edge connector for perfect contact with your ZX81.

Normally despatched within 10 days of receipt of your order.

AND NOW — 64K RAM PACK

Same quality as the 16K to give massive memory to your ZX81.

£62.95 (\$125)

CASSETTE professionally recorded by SOFTUDI NEWS STUDIOS

GAMES PACK — Beat this for value! 8 x 16K programs PLUS 2 x 1K programs FOR

3-D Battle (M/Code-16K) — Fast moving space battle with continuous count down of energy levels.

City Bomb (M/Code-16K) — Destroy the buildings and send your plane. Your fuel has nearly gone and you circle the city tower and tower.

Warp Wars (Basic & M/Code-16K) — Features realistic space craft missed by M/Code for previously solid M/Code fan with instant response.

Space Invaders (M/Code-16K) — Games without crossing or doubling back on your path but watch out for the expanding black holes.

Snake (Basic & M/Code-16K) — A game of thought and skill. Pass through all the marked previous spots at M/Code fan with instant response.

Sweet Tooth (Basic & M/Code-16K) — M/Code routines used to move your fat face round the screen and gobble the sweets.

PLUS: Slalom and Black Holes (previously sold together for £4.95)

An ESSENTIAL addition to your 16K RAM ZX81 for ZX80 8K ROM!

TOOLKIT — Written by PAUL HOLMES. Provides the following additional facilities:

Line renumber — You state starting number and increment value.

Search and replace — Changes every occurrence of a character as you require.

Free space — tells you how many free bytes you have left.

SPECIAL GRAPHICS ROUTINES

Hyper graphics mode — graphics never seen on a ZX81 before.

Open — instantly sets up as many empty print lines as you require. 1K version only!

Fill — used in conjunction with OPEN fills your screen instantly with your specified character.

Reverse — changes each character on your screen to its inverse video.

TAP ROUTINE — provides a system WAIT condition until a signal is received in memory location you specify.

All these routines are written in machine code and together take up only 164 BYTES of your precious RAM — an incredible achievement!

The price is incredible too! ONLY £2.95 (£7.95) for cassette, including FULL instructions and example programs.

ALSO available 16K version ONLY £4.95 (£9.95) which includes all the above. PLUS GOTO's and GSUB's included in line renumber.

Search for and list every line containing specified character.

16K VERSION

NEW GRAPHICS TOOLKIT (Another masterpiece by PAUL HOLMES)

22 exciting MACHINE CODE routines that give you control over your screen as never before!

(ZX81 - 16K RAM ONLY)

DRAW UNDRAW draws or deletes your mouse character string. It can be in a REM statement and may define as many different shapes as you like and draw or undraw each at will at whichever screen position you choose.

FOREGROUND ON/OFF use this to "protect" existing characters on your screen. When on new shapes will appear to slide behind and re-emerge from other shapes.

BORDER UNBORDER Draws a border round the edges of your screen area. Edit lines can be used if required. Your border is protected when foreground is on.

FILL Fills any number of lines you specify, starting at any line you specify, by your chosen character.

REVERSE Converts all characters to their inverse video, control as in FILL.

PRINT POSITION CONTROLS

UP DOWN | Alter your next PRINT position in the direction indicated

LEFT RIGHT |

EDIT/PRINT Moves next PRINT position to first edit line

SCROLL facilities

UPSCROLL

DOWNSCROLL

RIGHTSCROLL

LEFTSCROLL

Scroll your screen in the direction indicated

ONSCREEN OFFSCREEN turns your screen on or off

BACKGROUND ON/OFF

Ells your screen your specified character.

When foreground is on existing information is unaffected and shapes will appear to pass in front of your background, without deleting it.

SEARCH AND REPLACE will search the screen for every occurrence of the character you specify and replace it with your new character.

SQUARE draws a square or rectangle from your specific co ordinates.

ALL these routines are in machine code for

SUPER FAST response! Simply load GRAPHICS

TOOLKIT, which repositions itself at the end of

your RAM, then load your own programs or key in

a routine. GRAPHICS TOOLKIT uses only 164 BYTES of

your RAM and that includes space to load the

programmers TOOLKIT described above (16K RAM version)



Please send me details and price list for which I enclose a large S.A.E.

Name

Address

..... Phone


or telephone to place an order during shop hours to:
Watford (0923) 40601 or 44057

Signed

Send to The Computer Centre, Watford Ltd. (Dept. ECM)
150 High Street, Watford, Herts. WD1 2EN

SPECIAL FREE OFFER READ ON! **VIC 20**

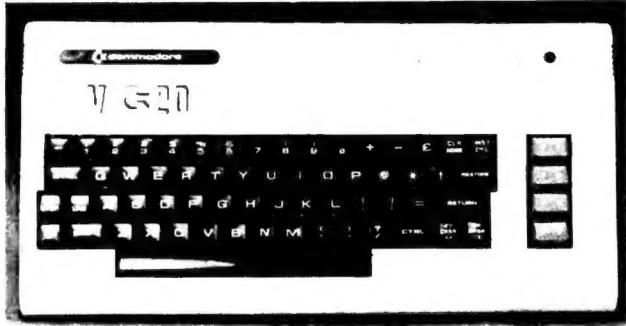THE FIRST FULL FEATURED COLOUR COMPUTER AT UNDER £200!!



FEATURES

*Sound *Colour *5K Memory Expandable to 27K *Standard PET Basic *Full size typewriter Keyboard *Graphics *Plug-in memory expansion *Low-priced peripherals.

SPECIAL OFFERS AVAILABLE WHEN ORDERING YOUR VIC 20 COMPUTER

**3K RAM CARTRIDGE FREE
or 8K RAM CARTRIDGE £32.95 inc. VAT
or 16K RAM CARTRIDGE £54.95 incl. VAT**

PLUS FREE GAMES TAPE WITH
EVERY CASSETTE DECK ORDERED

THE FOLLOWING ITEMS NOW AVAILABLE

VIC 20 Colour/Sound Computer	<input type="checkbox"/> £189.95 incl. VAT*
VIC Data Cassette Deck	<input type="checkbox"/> £44.95 incl. VAT
VIC 3K RAM Cartridge	<input type="checkbox"/> £29.95 incl. VAT
VIC 8 K RAM Cartridge	<input type="checkbox"/> £44.95 incl. VAT
VIC 16K RAM Cartridge	<input type="checkbox"/> £74.95 incl. VAT
VIC Joystick Control	<input type="checkbox"/> £7.50 incl. VAT
Arion VIC Expansion Unit	<input type="checkbox"/> £97.75 incl. VAT*
Machine Code Monitor Cartridge	<input type="checkbox"/> £34.95 incl. VAT
Programmers Aid Cartridge	<input type="checkbox"/> £34.95 incl. VAT
"Avenger" ROM Games Cartridge	<input type="checkbox"/> £19.95 incl. VAT
"Super Slot" ROM Games Cartridge	<input type="checkbox"/> £19.95 incl. VAT
"Alien" ROM Games Cartridge	<input type="checkbox"/> £19.95 incl. VAT
"Super Lander" ROM Games Cartridge	<input type="checkbox"/> £19.95 incl. VAT
"Road Race" ROM Games Cartridge	<input type="checkbox"/> £19.95 incl. VAT
Introduction to Basic (Part I)	<input type="checkbox"/> £14.95 incl. VAT
Carriage & Ins. on items marked*	<input type="checkbox"/> £3.45 incl. VAT
TOTAL	

All prices Subject to Manufacturers Price Changes

437 Stoney Stanton Road,
Coventry, CV6 5EA
West Midlands
Tel: (0203) 661162

IBEK
SYSTEMS

Name:

Address:

Please charge my Barclaycard/Access No.

Signed:


Or telephone order.

ECM 7/82

Exclusive Special Offer

E & CM/
WATFORD
ELECTRONICS
16K
RAM CARD

**£19.95
each
plus 50p
p. & p.**

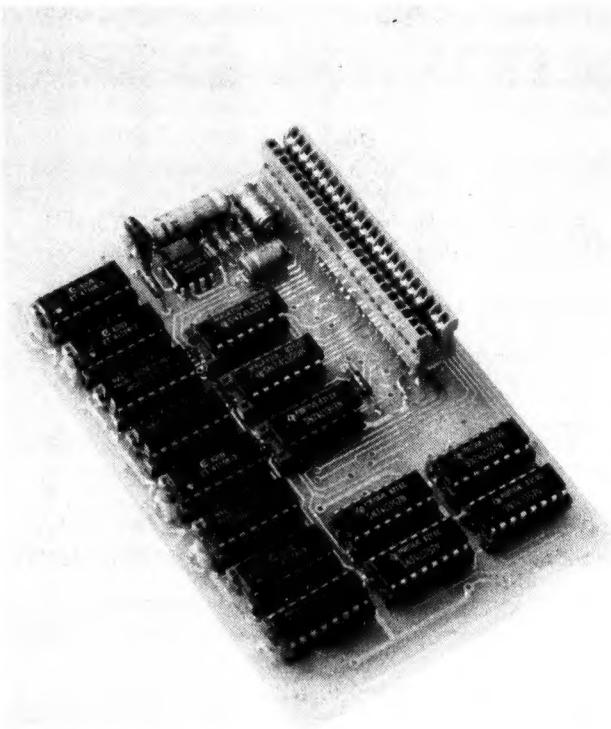

Designed especially to fit the ZX81.

The plug-in card comes uncased, completely assembled and on glass-fibre pcb.

Each unit is fitted with a gold-plated edge connector.

Orders to:

**16K RAM CARD Special Offer,
Watford Electronics,
33/35 Cardiff Road,
WATFORD,
Herts. WD1 8ED**

One 16K RAM Card per order only.

Please supply one 16K RAM Card.

I have enclosed £20.45 which includes VAT/p. & p.

Name

Address

.....

Memory Expansion Service By Post

A 2K ZX81 is many more times more useful than the standard 1K as now approx. 1,100 characters of programme can be stored and still leave room for a full display. The installation of a 2K RAM chip involves the disassembly of the computer and some soldering (see E&CM Jan 82), as many owners do not feel confident to carry out this task — Bolton Electronics are offering to do this for them.

To avail of this service, simply send the computer to Bolton Electronics at the above address. The inclusive charge for this service is £14.95 which includes the 2K RAM chip, the necessary sockets etc., testing and the return postage.

Alternatively the parts and full instructions can be supplied for £10.35 inc. V.A.T. and postage.

School Software Competition

Transam Computers and Hutchinson Education announce a new microcomputer software competition aimed at primary and secondary school teachers. Prizes totalling £1,750 will be awarded to the first twelve winners with guaranteed publication of winning programs. Royalties will be paid to authors and all copyright fully respected.

Prime Programs is a joint venture of Transam and Hutchinson Education. One of its main objectives is to encourage the production of high quality educational software and, accordingly, high standards of programming, robustness and documentation will be looked for. Equally, the educational value of the programs will be a central consideration.

Entry forms giving full details are available from 'Prime Programs' 17 Conway Street, W1P 6JD. The closing date for the competition is 1st July 1982 and prize winners will be announced in Autumn 1982.

Prime Programs also hope to publish a book of listings of the 40 best programs submitted other than prize winners. This will be in addition to individual winning programs which will be published separately.

Where possible, all winning programs will be available to run on a variety of different microcomputers.

The competition is planned as an annual event.

It is hoped that primary schools will enter programs this year but Graham Clifton said 'We expect that substantially more primary schools will have microcomputers in 1983 and we are keen to include as many schools as possible.'

Further information is available from: Bob Osborne at Hutchinson Education 17 Conway Street, London W1P 6JD. (01-387 2811)

Graham Clifton at Transam Computers Ltd, 59-61 Theobald's Road, Holborn, London WC1. (01-405 5240/2113)

Acorn ADD-ONS

An E&CM reader is making available to other Acorn users a range of ready assembled peripherals. The new equipment consists of a sound generator which is available with either 1,2 or 3 AY-3-8910 sound chips, built in amp and speaker and up to 6 eight bit I/O ports. There is also an 8 way joystick with 4 extra push buttons which plugs into one of the sound generators ports (up to six joysticks can be used simultaneously with the largest sound generator model) or into a joystick port adapter which uses the ports of the VIA in the ATOM. (The joystick port adapter can also be used as 2 general I/O ports with handshake). The joystick will also plug directly into the Technomatic ZX80/81 user port. A more powerful 5V 5A power supply is available with or without mains suppression.


For more information send a SAE to: R Shillito, 5 Ingarfield Road, Holland, Clacton, Essex, CO15 5XA.

KEYBOARD FITS ONTO ZX81

Kempston Electronics are launching a novel keyboard for the 81 which fits directly in place of the existing touch sensitive keypad.

The keys are mounted on a p.c.b., which is finished in the same colours as the ZX81. To attach the new keyboard the touch sensitive pad is simply peeled off and the new full size board is dropped into place. The p.c.b., is an exact fit and a ribbon cable is used to attach the keyboard to the ZX81.

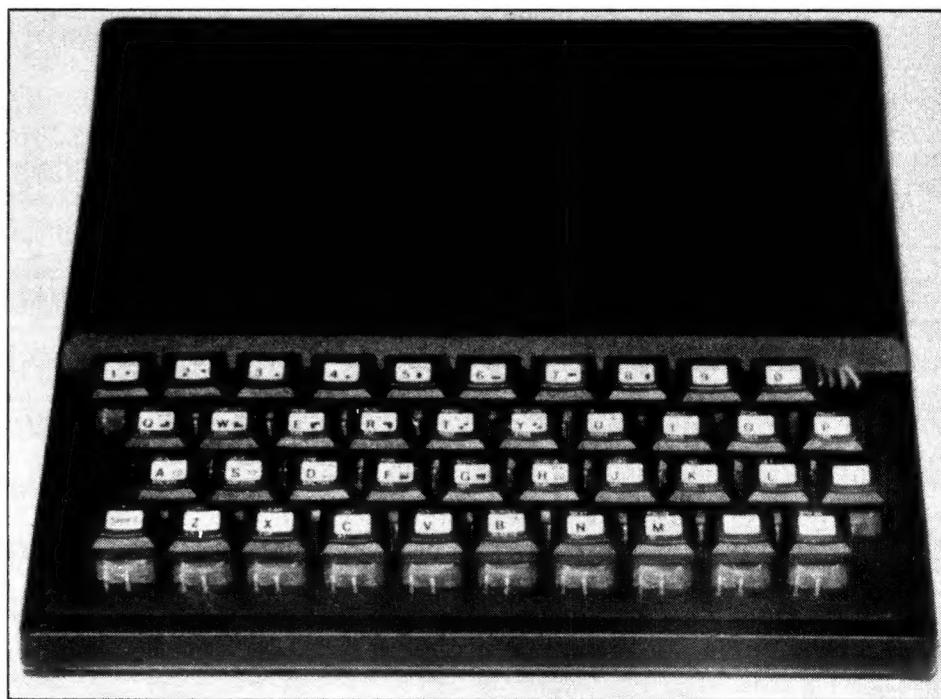The keyboard is sold as a kit and can be obtained directly from Kempston Electronics, 50 Adamson Court, Hillingdon Road, Kempston, Bedford.




New Ethernet Development Tools

Thame Systems Limited the distributor for Ungermann-Bass has just released details of a new Network Configuration Facility (NCF-2). The system consists of a 5 Megabyte Winchester disk housed together with a 1 Megabyte floppy diskette unit and intelligent controller having an IEEE 488 interface.

The NCF-2 is connected to Net/One by plugging into a 6412 application processor board which can be fitted into any Network Interface Unit (NIU2A).

By using a Whitesmiths C compiler it is possible to produce non-standard software modules for applications not covered by standard Net/One software.

The standard operating

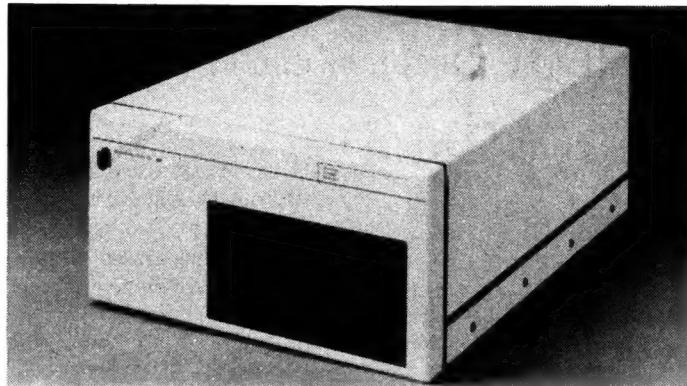

system used by the NCF-2 is CP/M and when not in use as a Network Development Tool the NCF-2 may be accessed by privileged users who can run standard CP/M based software packages.

Enhancements to Net/One software mean that diagnostic functions can be invoked from the NCF-2 even by remote telephone connection if desired.

At startup or when adding additional equipment to the network, the NCF-2 is used to provide the various programmes and Network Inter-

face Unit definitions which are down-loaded into each N.I.U.

After receiving their programme load each N.I.U. is able to operate without further reference to the NCF-2.

The NCF-2 contains all the information required to restore the Network in the event of a complete power failure. It also provides security checks in the event of an illegal user attempting to connect to Net/One.

For further information contact Ron Davis, Thame Systems Limited, 084 421 5471.

DOS for Nascom Users

A complete disk operating system designed specifically for the Nascom 1,2 and 3 microcomputers has been introduced by Gemini Microcomputers Limited.

Called PolyDOS, the system is fully compatible with existing software written for NAS-SYS 1 or 3, which means programs can be saved on disk without any changes. Installing PolyDOS requires no hardware modifications; however the Nascom must have a minimum of 48K RAM and use either a GM8 15 floppy disk system with a Gemini GM8 09 floppy disk controller card, or a Gemini GM805 floppy disk system. Different PolyDOS versions are available for the two systems.

Under PolyDOS the GM815 disk system supports both double sided single density and double sided double density giving 175KB and 315KB total storage per drive, respectively. The GM805 system will support only single density format. Single density disks, however, are interchangeable between the two systems.

The PolyDOS system includes a 4K Disk BASIC extension program, a disk-based editor and an assembler. An extension to the Nascom ROM BASIC, Disk BASIC will run existing BASIC programs without modification. The disk assembler, PolyZap, is probably the most advanced assembler ever written for the Nascom. Features include conditional assembly, multiple input files, and referencing of external symbol table files.

Three utility programs are supplied with PolyDOS at no extra cost: SuperZap, FORMAT, and BACKUP. SuperZap allows editing of

sectors on a disk. Sectors are displayed in hex and ASCII and, by moving the cursor, bytes to be modified can be selected. The program called FORMAT will format and verify disks. BACKUP allows the user to make back-up copies of disks, as well as enabling disks to be converted from single to double density format and vice versa.

PolyDOS is supplied as a system disk and two 2708 EPROMS. The documentation is divided into five manuals: user's guide, system programmer's guide, editor manual, assembler manual, and Disk BASIC manual. The complete PolyDOS package costs just £90 plus VAT and is available from any Micro-Value dealer.

For further information contact David Neal at Media Marketing Services Ltd on 01-437 8146 or John Marshall at Gemini Microcomputers Ltd on (02403) 28321.

ZX99 Automatic Tape Drive Controller

Data-Assette are launching the first of their hardware add-ons for the ZX81, which slots into the expansion board still allowing use of the ZX Printer and 16K RAM pack.

The ZX99 is the logical extension to the ZX81, giving it real data-processing power. Business systems, word processing and information retrieval all now come within reach, making your ZX81 a fully fledged information handling system — and that's what computers are all about.

Under full software control, you can handle up to four tape recorders at once, (two for loading and two for saving), through their 'remote' sockets. The unit enables you to use tape storage to hold data files — not just programs — up to 200K bytes on a single cassette.

This is achieved through powerful USR commands in the ZX99's Tape operating system held in its own built in ROM. The recording format is totally matched to the ZX81, so there are no compatibility problems, you can even use the ZX99 to make directory listings of your ordinary program storage tapes. It also features a full tape to tape copy program evoked by a single USR command.

As if this were not enough, the ZX99 also provides you with a (RS232C) serial output interface, that allows you to drive one of the wide range of printers that accept the standard ASCII data. (If you already own a ZX printer, the system is fully compatible).

With its combination of data storage and printer drive the ZX99 gives your ZX81 all the extra capabilities that it needs.

For further information contact:
Data-Assette,
44 Shorotan Street,
London NW1.



MicroValue Represent The Serious Computer User

Anyone serious about putting their computer to meaningful use will wish to expand the system and may well find their local computer store unable to assist for a variety of reasons.

A new idea launched by a group of independent computer shops is collaborating to provide customers with the benefits of the multiples, i.e., bulk purchase discounts and uniformity of product and, in addition, service. MicroValue is quite novel since it is neither a franchise network nor a single company. There are parallels to be drawn between MicroValue and, say, Photomarkets, which operates a similar basis.

The marketing strategy draws strength from numbers, however with MicroValue it goes further since each dealer undertakes to handle repairs and enquiries on advertised products irrespective from which MicroValue outlet they were purchased. This is no mean offer since the group decided to throw out the normal 90 day warranty on computer equipment and give a full 12 months warranty on all built systems and peripherals.

Dedicated Dealers

The refreshing aspect of MicroValue is that all the members are dedicated to furthering computing. That is not to say they don't sell other products, since many do, but computers are not in their shops because they are fashionable. They are there because the dealer believes in

them and has grown up with them.

As testimony to this claim is the example shown by MicroValue dealers prior to the group's inception. The original dealers (there are a couple of recent additions) were all suppliers and devoted followers of Nascom Microcomputers. When that company ran into difficulties customers who had bought Nascom equipment with a view to expanding it faced an uncertain future. No-one knew that Lucas Logic would eventually buy Nascom Micocomputers, so there was, understandably a fair degree of despondency among dealers and users. Being one of the first truly British micro pioneers, Nascom had a considerable loyal following.

The original MicroValue dealers could have dumped this following and switched to other micros for there were many around at this time and, indeed, some of the dealers were already selling Sharps and other machines. Instead, they banded together and resolved to continue advertising as well as developing compatible expansion boards. From that resolution came the idea to pool advertising funds and adopt a common marketing policy. For several months, the joint advertisements appeared under a Nascom headline but as more and more of the dealers' own boards and software came on stream it became inappropriate to apply the Nascom name and a new umbrella title was sought.

New Name

The search ended with an agreement on the name MicroValue, which was promptly registered much to everyone's surprise that no-one else had thought of such an obvious name before. Although each member dealer adopted the name, they continued to maintain their own identities and independence but have remained loyal to the original concept of promoting and developing Nascom compatible products. This has now blossomed into a concerted effort to establish a British bus standard, known as 80-BUS, which encompasses not only Nascom products but also those of Gemini Microcomputers, — a British company which last year launched the MultiBoard system.

Both are built and tested systems using MultiBoard modules and, hence, the 80-BUS bus structure.

New 80-BUS boards include a powerful Z80 CPU board with 64K of on board dynamic RAM; IEEE 488 board; A/D conversion board; 32K Static RAM board; an intelligent colour board; and several others.

MicroValue Dealers

Bits & PCs
4 Westgate, Wetherby,
W. Yorks
Tel: (0937) 63774

Computer Interfacing &
Equipment Ltd.
The Micro-Spares Shop,
19 Roseburn Terrace,
Edinburgh EH12 5NG
Tel: (031) 337 5611

ElectroValue Ltd
28 St Judes, Englefield Green,
Egham, Surrey TW20 0HB
Tel: (0784) 33603

E.V. Computing
700 Burnage Lane, Burnage,
Manchester M19 1NA
Tel: (061) 431 4866

Henrys Radio
404 Edgware Road, London
W2. Tel: (01) 402 6822

Interface Components Ltd
Oakfield Corner, Sycamore
Road, Amersham, Bucks.
Tel: (02403) 22307

Leeds Computer Centre
62 The Balcony, Merrion
Centre, Leeds.
Tel: (0532) 458877

Skytronics
2 North Road, The Park,
Nottingham.
Tel: (0602) 45053/54215

Target Electronics
16 Cherry Lane, Bristol
BS1 3NG
Tel: (0272) 421196.

Low-cost Big Memory Machine

Low-cost micro-system pioneer John Marshall, has developed a competitively priced micro-computer with an impressive specification.


Called "Galaxy-1" the computer has been built around the MultiBoard system — and established range of micro-board modules developed by Gemini a year ago and in wide use by manufacturers of micro computer products.

The proven hardware includes twin Z80 microprocessors, 64K bytes of dynamic random access memory, two double density 5.25in floppy drives giving 400K storage per drive, and a detachable 59-key keyboard. The second micro-processor controls all video functions, thus freeing the entire 64K dynamic RAM for program execution.

Galaxy-1 is supplied with a comprehensive selection of software including the CP/M 2.2. disk operating system and COMAL-80 — a powerful extended BASIC from Denmark that features a number of the structures found in PASCAL. Gemini have also added a useful text editor and formatter called GEM-PEN, which offers a number of word processing facilities, GEM-

Galaxy-1 Specification.

Processors:	Twin ZX80A at 4MHz (no wait states)
Memory: Z80-1:	64K dynamic RAM 2K phantom ROM 2K monitor ROM
Z80-2:	2K workspace RAM 2K screen RAM 2K character generator ROM 2K character generator RAM 64 character input buffer Full ASCII encoding 59 keys 2-key rollover Caps lock function Cursor control keys 80 x 25 display format inverse video 160 x 75 pixel graphics programmable character set programmable special functions 2 x 5.25in drives
Keyboard:	400K storage per drive Double density RS232 interface Programmable baud rates Modem control signals 1200 baud CUTS cassette interface Centronics parallel interface Light pen input IV P-to-P Video output
Video:	1200 baud CUTS cassette interface Centronics parallel interface Light pen input IV P-to-P Video output
Disk:	400K storage per drive Double density RS232 interface Programmable baud rates Modem control signals 1200 baud CUTS cassette interface Centronics parallel interface Light pen input IV P-to-P Video output
Serial I/O:	400K storage per drive Double density RS232 interface Programmable baud rates Modem control signals 1200 baud CUTS cassette interface Centronics parallel interface Light pen input IV P-to-P Video output
Parallel I/O:	400K storage per drive Double density RS232 interface Programmable baud rates Modem control signals 1200 baud CUTS cassette interface Centronics parallel interface Light pen input IV P-to-P Video output
Other I/O:	400K storage per drive Double density RS232 interface Programmable baud rates Modem control signals 1200 baud CUTS cassette interface Centronics parallel interface Light pen input IV P-to-P Video output
Software included:	CP/M 2.2 Operating System COMAL-80 Structures BASIC GEM-PEN Text Editor Formatter GEM-ZAP Z80 Editor Assembler GEM-DEBUG De-bugging utility

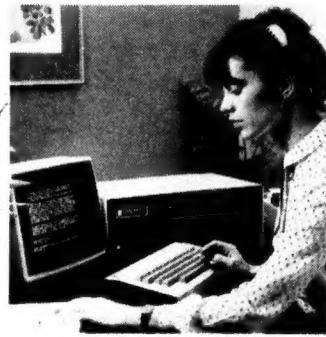

BBC Micro-National Service Centre Set-Up

Production of the BBC Micro-computer is currently over 6,400 units per month. By the end of July both the existing subcontractors are estimating a combined output of over 12,000 units per month. A third sub-contractor has just been appointed who will produce a further 3,000 units per month. They will switch to the overseas markets when the backlog of sales has been reduced. At the moment production of the two machines is split 3 to 5 to the standard Model A and the enhanced Model B respectively.

Model A computers are now delivered within 21 days of receipt of orders and a limited quantity are being shipped to dealers. Model B computers still have a backlog of some 12,000 units which at present demand will be cleared by the first week in August.

Services Centres

Seventy Acorn dealers have undertaken to provide after sales service and advice for the BBC Microcomputer. They are being equipped with automatic test/diagnostic systems and service manuals. They all recently attended a two day technical seminar in Cambridge recently.

An agreement has now been finalised with Retail Control Systems Ltd in Middlesex to provide a nationwide repair service for all parts of the system as a back-up to the dealer or to handle repairs now being dealt with by Acorn Computers via BL Marketing.

Retail Control Systems Ltd will also provide, at a very reasonable fee, maintenance contracts for all customers but in particular, those with substantial installations of BBC computers such as schools and colleges.

ZX81 PROGRAM CRASHES SOLVED.

STOP SINCLAIR RAM PACK Wobble

Send for our sturdy 2mm Aluminium cradle to hold your ZX81 and RAM pack firmly together.

FULLY INCLUSIVE PRICE

SEND ONLY

£5.49

(Post & Pack etc. included)

Please make all cheques or P.O.'s payable to:

**CALPAR ELECTRONICS LTD.,
LILAC CRESCENT, BEESTON,
NOTTINGHAM NG9 1PX.**

QUANTITY
REQUIRED

AMOUNT
SENT £

NAME

ADDRESS

POST CODE

DELIVERY 7 TO 14 DAYS.

ACORN PLUS!

CONTROL UNIVERSAL LTD announce three ways to get a first class service on Acorn and Acord Compatible products.

1. RING IN AN ORDER NUMBER — FAST DESPATCH.
2. TURN UP AND COLLECT THE GOODS — OVER THE COUNTER SERVICE IN OUR SHOWROOM.
3. WRITE IN AN ORDER — FAST DESPATCH.

If you don't have an account you can use Access or Visa

Colleges, Government bodies and large companies have automatic credit facilities.

The following are normally held in stock

ACORN

Atom — All Atom games, books and accessories.

System 1 (System 2, 3 & 4 parts held in stock.
System assembly takes 1 to 3 weeks.)

CPU CARDS — 6502 and 6809

VDU CARDS — 40 and 80 COLUMN

32K DRAM CARD

CASSETTE INTERFACE CARD

DISK CONTROLLER CARD and DISK DRIVES

ECONET for ATOM and EUROCARD SYSTEMS

Ascii KEYBOARD (encoded type in enclosure)

TWELVE BIT ANALOG CARD

EPROM PROGRAMMER CARD

EUORACKS and ENCLOSURES

VERSATILE INTERFACE CARD (i/o + RS 232)

EUROCARD FRONT PANELS.

ACORD COMPATIBLE CARDS by CONTROL UNIVERSAL

CUMEN — UNIVERSAL MEMORY CARRIER with 8 sockets for 2k, 4k or 8k ROM, PROM or RAM, has battery back-up for CMOS.

CUDRAM — 34k bytes of dynamic RAM: can use 16 cards one system = 896k bytes (ready July '82).

CUGRAPH — VERY HIGH RESOLUTION text and graphics, 256 x 512 dots, 8 colours (ready June '82).

CUBIT, CUMOT, CUNINE. CPU Cards with 4k RAM + 4k PROM + VIA + Power-on restart: use 6502, 6802, 6809 respectively.

CUKEY — 52 key non-encoded non-enclosed Ascii keyboard for CUBIT, CUMOT and CUNINE.

CUBIO — Four VIA's or PIA's on one card = 80 i/o Channels.

CUBAN — Eight bit analog interface — 16 analog input, one analog output + VIA.

Send for detailed catalogue to
CONTROL UNIVERSAL LTD.

Unit 2 Andersons Court, Newnham Road,
Cambridge, CB3 9EZ.
Tel: Cambridge (0223) 358757

TEXAS INSTRUMENTS HOME COMPUTER STOCKISTS

ABERDEEN Dixons ALTRINCHAM Boots ASHFORD
Rumbelows BARNET Rumbelows BASILDON Rumbelows
BASINGSTOKE Boots BATH Boots, Microstyle BEDFORD
Carlow Radio, Rumbelows, Boots, Comserve BILLERICAY
Rumbelows BIRKENHEAD Dixons BIRMINGHAM Dixons,
Comet, Hwards Home Stores, Boots BLACKPOOL Boots
BLETCHELEY Rumbelows BOREHAMWOOD Rumbelows
BRADFORD Ackroyd Typewriters BRAINTREE Rumbelows
BRENTWOOD Rumbelows BRIGHTON Game, Boots BRISTOL
Dixons BROMLEY Rumbelows, Boots BROMYARD Acoutape
Sound CAMBRIDGE Rumbelows, Dixons, Heffers
CANTERBURY Rumbelows, Dixons CARDIFF Boots, Dixons,
Computer Business Systems CARLISLE Dixons CHELMSFORD
Dixons, Rumbelows CHESTER Boots CHINGFORD Rumbelows
COLCHESTER Rumbelows CORBY Computer Supermarket
CREWE Midshires CROYDON Boots, Dixons, Allders
DARTFORD Rumbelows DERBY Datron Microcentre, Boots
DORRIDGE Taylor Wilson DUNSTABLE Rumbelows
EASTBOURNE Rumbelows EDINBURGH Robox, Esco, Texas
Instruments, Dixons, B.E.M. ENFIELD Rumbelows EXETER Peter
Scott, Boots, Dixons GLASGOW Boots, Esco, Robox, Dixons
GT. YARMOUTH Rumbelows HANLEY Boots HARLOW
Rumbelows HATFIELD Rumbelows HEMEL HEMPSTEAD
Rumbelows, Dixons HITCHIN Rumbelows HODDESON
Rumbelows HULL Radius Computers, Boots, Dixons, Peter Tutty
ILFORD Boots IPSWICH Rumbelows KINGSTON Dixons
LEEDS Dixons, Boots, Comet LEICESTER Dixons, Boots
LEIGHTON BUZZARD Computopia LETCHWORTH
Rumbelows LINCOLN Dixons LIVERPOOL Dixons, B.E.C.
Beaver Radio, Computerworld LONDON: Balham Argos Bow
Rumbelows Brent Cross Dixons, Boots Camden Town
Rumbelows City Road Sumlock Bondair Clerkenwell
Star Business Machines Curtain Road Eurocalc Ealing Adda
Computers EC1 Argos EC2 Mountandene Edmonton
Rumbelows Finchley Road Star Business Machines Fulham
Mondial Goodge Street Star Business Machines Hackney
Rumbelows Hammersmith Dixons Hendon Futronic Holborn
Dixons Hounslow Boots Kensington High Street Video Palace
Knightsbridge Video Palace, Harrods, Futronic (at Chiesmans)
Loughton Rumbelows Marble Arch Star Business Machines
Moorfield Dixons Moorgate Star Business Machines New
Bond Street Dixons Oxford Street Selfridges, H.M.V., Dixons
Regent Street Star Business Machines Tottenham Court
Road Landau, Eurocalc Victoria Street Futronic (at Army &
Navy) Wandsworth R.E.W. Wood Green Boots, Rumbelows
Woolwich Rumbelows LUTON Dixons, Rumbelows
MAIDSTONE Dixons, Boots, Rumbelows MALDON Rumbelows
MANCHESTER Orbit, Boots, Dixons MIDDLESBROUGH Boots,
Dixons MILTON KEYNES Rumbelows, Dixons NEWBURY
Dixons NEWCASTLE Boots, Dixons NORTHAMPTON Dixons
NORWICH Dixons, Rumbelows NOTTINGHAM Bestmoor,
Dixons, Boots ORPINGTON Rumbelows OXFORD Science
Studio PETERBOROUGH Boots PLYMOUTH J.A.D., Dixons
PORTSMOUTH Boots, Dixons POTTERS BAR Rumbelows
PRESTON Dixons RAMSGATE Dixons RAYLEIGH Rumbelows
READING Dixons RENFREW Comet ROMFORD Rumbelows,
Dixons RUSHDEN Computer Contact SANDY Electron Systems
SCARBOROUGH Video + SHEFFIELD Datron Microcentre,
Dixons, Video +, Wigfalls SITTINGBOURNE Rumbelows
SLOUGH Boots, Texas Instruments SOUTHAMPTON Dixons,
The Maths Box SOUTHBEND Rumbelows, Dixons, Futronic
(at Keddies) ST. ALBANS Rumbelows STEVENAGE Dixons,
Rumbelows STRATFORD Rumbelows SUDSBURY Rumbelows
SWANSEA Dixons TONBRIDGE Rumbelows WALTHAM
CROSS Rumbelows WALTHAMSTOW Rumbelows WARE
Rumbelows WARRINGTON Boots WATFORD Computer Plus,
Computer Centre, WELWYN GARDEN CITY Rumbelows
WETHERBY Bits & Pieces WOLVERHAMPTON Dixons
WOODFORD Rumbelows
Also available at Greens within major branches of Debenhams.


You can't get a Home Computer from Texas Instruments under 16 K RAM.



Make the right move into computing with the Home Computer from Texas Instruments. It gives you a large combined RAM/ROM capacity up to 110 K Byte and the ability to expand with a full range of peripherals and software. So as your knowledge of computers increases the TI Home Computer will grow with you.

Just compare the versatility of the TI Home Computer with its price - you'll find it real value for money that will prove to be a good long term investment.

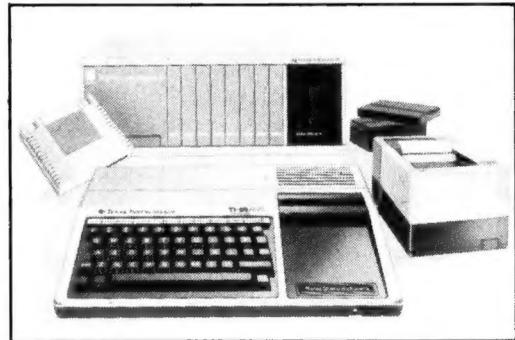The TI-99/4A is a sophisticated computer designed not only for the beginner with its ease of operation, but also for the professional with its vast computing power through a 16 bit microprocessor. And it simply plugs into an ordinary household TV set.



With its high resolution graphics with 32 characters over 24 lines in 16 colours (256 x 192 dots), 3 tones in five octaves plus noise, and BASIC as standard equipment and options such as other programming languages - UCSD-PASCAL, TI-LOGO and ASSEMBLER - and speech synthesis, you'll find that the TI 99/4A more than compares with the competition. Especially when the starting price is £340 or less. When you want to solve problems there are over 600 software programs available worldwide - including more than 40 on easy-to-use Solid State Software® Modules.

After all, from the inventors of the microprocessor, integrated circuit and microcomputer, it's only natural to expect high technology at a realistic price.



Enjoy a new world of learning.

**TEXAS INSTRUMENTS
LIMITED**

LETTERS PAGE

Dear Sirs,

In my business we use a Pet CBM 3032 with disk drive and a Printerm printer for a variety of duties including invoicing, costings, some analysis of production and data storage. With the exception of data storage (PETAID from Stage One) I wrote the programmes myself, all in Basic.

I now wish to move to a slightly more powerful system with CP/M and feel that Superbrain looks to offer value for money. However I have no experience at all of CP/M and as I shall be having the new system in my home where I can work without interruption we shall still retain the CBM. I note that Basic can be used on CP/M systems but am not sure exactly what this means. Can I, for example, write programmes in Basic on a Superbrain (if that is what I buy) in my home and then use the same programmes in my office on CBM machine. If the answer is no can you suggest an alternative CP/M machine where the answer would be yes. My point in wishing to go CP/M is to move into an area where software is readily available as I feel that CBM has not really made the move from hobby/home/school type machine into the business world whereas it seems that CP/M machines have.

My programming knowledge is limited, being self taught from books and experience. I would be most grateful for any suggestions you are able to offer. The price area I have in mind is around the £3000 mark (perhaps a little more) to cover a complete system including drives and a reasonably good quality printer, not necessarily including any software although it would be nice to have a database programme and a wordprocessing programme within the price if it should prove possible.

I look forward to your advice either by letter or printed in the magazine.

Yours faithfully,
D.E. Higgins.

Dear Sir,

I enjoyed Reg Boor's "Technical Graph Plotting with the ZX81" in the March 1982 issue, and if the listings shown in Figures 1,2,3, & 4 are examples of the ZX81 printer then it speaks well for the device. I must get one. However, I can't agree that Fig. 4 was a print-out of the listing shown below the graph. Line 340 should read "FOR X = 1/(2*SX) TO 1.25 STEP 1/(5*SX)". At least, that line works better on my ZX81 than the line given in the article.

Peter Grinstead,
Pennance Road,
Falmouth.

Dear Sir,

I was interested in your article on BBC interfacing in the May issue of Electronics and Computing and am responding to your invitation to suggest topics for further articles.

What interests me and, I suspect, many other readers is robotics and hence articles on hardware details of interfacing stepper motors and associated equipment together with the software controls would be immensely useful.

Your Sincerely,
Jon Greenman.

Dear Sir,

I wonder if any of your readers can help with a ZX81 problem? I have noticed that when the computer is switched on there is background interference with stereophonic radio reception—a kind of "chortling" noise. Even if the radio is connected to an external VHF aerial (not a TV aerial) and at the opposite end of the house the interference still persists. It sounds as if the computer is producing electrical discharges which are picked up directly by the radio independently of the aerial.

I feel sure that there must be some method of suppressing these unwanted noises but no one I have spoken to so far has been able to suggest one. Does anyone have any ideas?

Brian Bagot
Woodlands Close,
Cranleigh,
Surrey.

Dear Sir,


I was interested to read your article "Interfacing the B.B.C. Microcomputer" in the May issue of Electronics & Computing. With regard to future articles I would be particularly interested in applications in the Physics Laboratory e.g. data logging and analysis.

As you may know Lincolnshire County Council have

bought every secondary school a B.B.C. micro. The County Advisor for Microelectronics has organised a series of in-service courses to run shortly on which I am lecturing on control/electronics aspects. In connection with this I have designed and prototyped a general purpose interface box with 4 dedicated input lines and 4 dedicated output lines all protected by optical isolators. The output lines can switch 180 ohm, 60 ma relays. The box is also protected with zener diodes and short circuit protection devices. If you would like further details (circuit diagram, p.c.b. pattern) I would be pleased to supply them.

Finally if you have details of the operating system machine code calls I would appreciate a copy.

Dr. J. Marsden,
Wragby Road,
Lincoln.

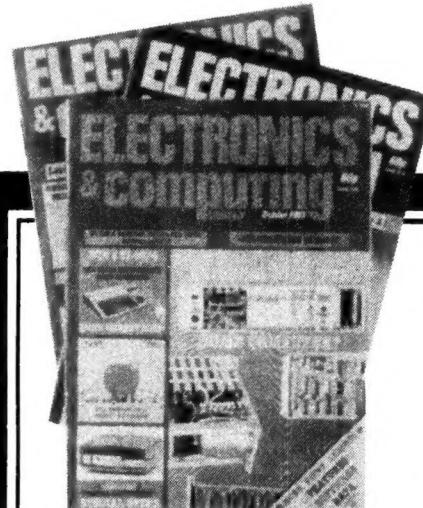

Back issues now available by post

BACK ISSUE ORDER FORM

Please send the following issues:

Post to
Electronics & Computing
Monthly
Back Issues
67 High St.
Dawson,
Northants

..... enclose 80 pence
for each issue required

NAME

address

The commonest form of human interaction with a computer system is via the use of some form of keypad or keyboard. Devices of this type can be used to facilitate the input of individual alphanumeric characters - as might be used in a simple menu selection procedure. A more useful mode of operation, however, is that which enables a collection of consecutive characters to be typed - thereby enabling the input of a message string.

Such strings may be used to command the computer to perform one of its many electronic data processing, computational or control functions. Thus, the message strings: ADD 3+2, SORT JACK, EDIT MARY, and SWOFF 295 may be used to initiate numeric addition, file sorting, file editing, and, control switching operations, respectively.

If the keyboard device is associated with a CRT screen then more sophisticated types of input transaction can be implemented. For example, through the use of suitable keyboard control keys it is usually possible for the user to move a screen cursor and locate it within any of the available screen character positions. Typically, these constitute a matrix of 24 rows by 80 columns — making a total of 1920 positions in all. Given that the user's terminal is reasonably intelligent it is always possible to determine the position at which the cursor resides. A facility of this sort gives an added dimension to the user's input capability. Now, in addition to specifying a message string, the user can control the physical location at which this will be positioned on the screen. In many situations this may have special significance since the location of a message on the CRT surface may determine its semantics or meaning. Suppose, for example, that the string being typed is positioned at row 12, column 20; the control software resident within the terminal might now be programmed to accept and validate this as a SURNAME value. Similarly, should the cursor be positioned at row 18, column 30, then, this may be taken to indicate that an AGE value is being typed. From these examples it is easy to see that the position of

PROGRAMMING A HAND PRINT TERMINAL

by Philip G Barker

the cursor helps to determine the meaning of the data being entered.

A hand print terminal works in an analogous fashion to the screen/keyboard system outlined above. However, instead of typing and positioning a cursor the user prints message strings on a specially designed data capture document. This is positioned above a pressure sensitive surface in such a way that the terminal hardware is able to deduce both the nature of the characters being written and their position on the surface.

A typical arrangement for such a system is illustrated in figure 1. The data capture document that is shown here allows the input of four items of data: a person's name, his/her age, sex and salary. In order to give instructions to the user the terminal is equipped with a single (40 character) line display. The diagram shows this being used to prompt the user to enter appropriate salary data. This would now be achieved by printing a string of decimal digits within the five vacant boxes next to the salary keyword on the document.


The pressure sensitive surface may be regarded as being subdivided into a grid of small squares, each side being of length 0.25 inch. Individual squares are identified by their column and row numbers. Embedded within the terminal is a microcomputer system. This is responsible for character recognition and position determination. Thus, when the user writes a character on the data capture document the row number (R), column number (C), and ASCII value (A) of the symbol written are each determined. This information is then made available to the host computer to which the terminal is attached. The software in the host now has to analyse this triplet of values and decide what to do with them.

MECHANISM OF OPERATION

There are several different approaches to the design and construction of intelligent devices capable of recognising hand printed text. One of the simplest of these measuring the resistance, in two dimensions, across a specially prepared conducting sheet. The principle of the method is illustrated in figure 2. Sketch (A) shows a cross section of a pressure sensitive pad that operates on this principle. Two conducting membranes are held parallel to each other by stretching them over an insulated rectangular frame (shown shaded). Data capture documents are placed on the upper of the two conducting surfaces. When a user writes on this document, the pressure of the pencil stroke forces the two membranes into contact thereby completing an electrical circuit — as shown in sketch (B). By accurately measuring the resistance in the X and Y directions — see sketch (C) — it is possible to determine the absolute coordinates of the point of contact of the writing instrument. These can easily be converted into row and column numbers within the matrix grid system described above.

In addition to calculating the grid coordinates at which information is being written the hardware in the terminal must attempt to deduce which characters the user is scribing on the surface of the document. Various mechanisms exist for doing this; most of them depend upon some form of pattern recognition procedure. Two of these techniques are briefly outlined below.

FIGURE 1. Data Entry Via A Hand Print Terminal.

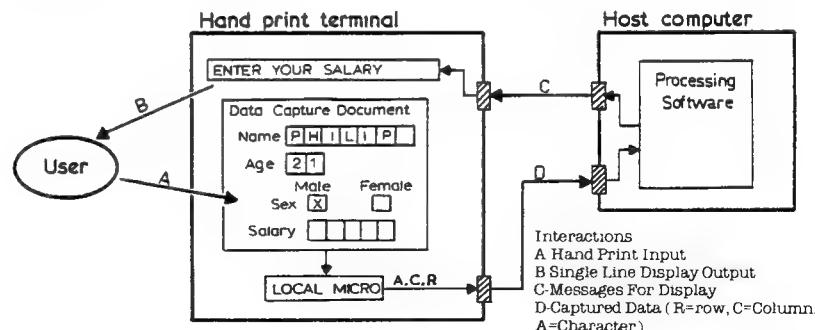


Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite


BRANDLEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM

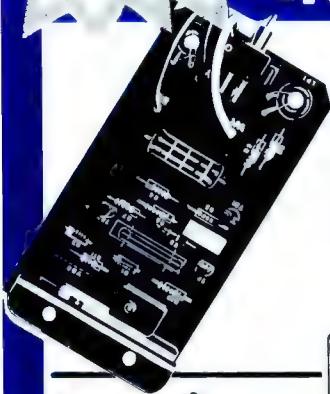


SX1000 Electronic Ignition

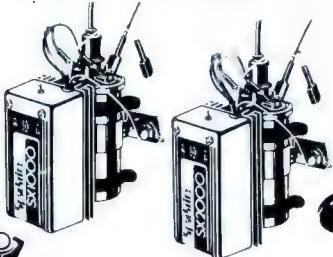- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




SX2000 Electronic Ignition

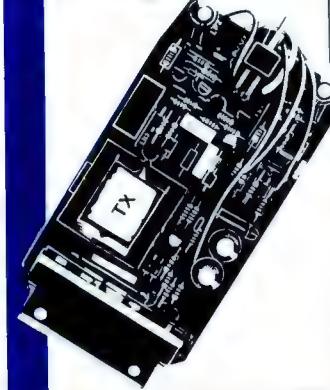- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles



AT-80 Electronic Car Security System

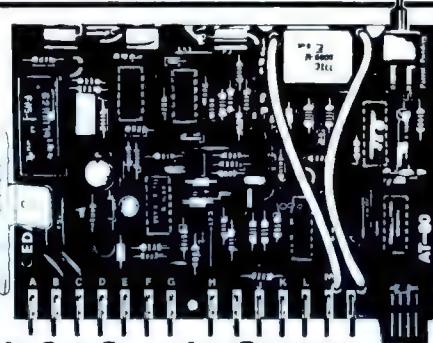- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble




MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble




TX2002 Electronic Ignition

- The ultimate system • Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive.
- Extended coil energy storage circuit
- Magnetic contactless distributor trigger-head
- Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

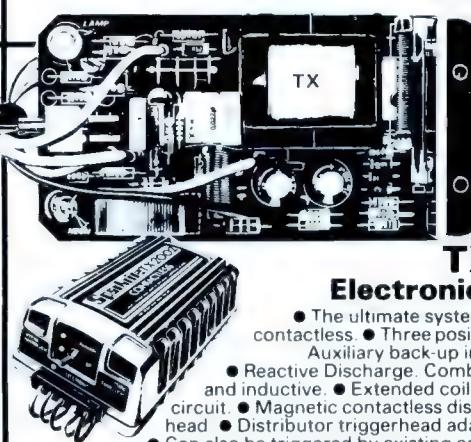

VOYAGER Car Drive Computer

- A most sophisticated accessory. • Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd
- Affords 12 functions centred on Fuel, Speed, Distance and Time. • Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on. • Facility to operate LOG and TRIP functions independently or synchronously.
- Large 10mm high 400ft-L fluorescent display with auto intensity.
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%.
- Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours.
- Full Imperial and Metric calibrations.
- Over 300 components to assemble
- A real challenge for the electronics enthusiast!

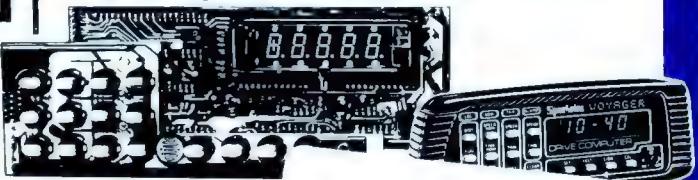

All EDA-SPARKRITE products and designs are fully covered by one or more Warranties

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 1

	SELF ASSEMBLY KIT	READY BUILT UNITS
SX 1000	£12.95	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
AT. 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£ 9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

Allow 28 days for delivery

NAME _____
ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDER

£ _____ KIT REF. _____

CHEQUE NO. 24 hr. Answerphone
PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD
SEND ONLY SAE IF BROCHURE IS REQUIRED

BRANDLEAD

CUT OUT THE COUPON NOW!

(B) Use of a Touch Table


FIELD	ROW	COLUMN	TRANSACTION TYPE	ENTRY ORDER	DATA TYPE
Retrieve	1	3	Single Peck	2	Peck
Register	1	16	Stroke	1	Stroke
Restart	1	21	Single Peck	2	Peck
Insert	1	30	Single Peck	2	Peck
Time	4-15	5-8	Character Stroke	3 or ?	Numeric
Temp	4-15	12-14	Character Stroke	4 or ?	Numeric
Flow	4-15	17-18	Character Stroke	5 or ?	Numeric
		20-21			
Terminate	15-16	30-31	Single Peck	?	Peck

TYPES OF TRANSACTION

We have established that the pressure sensitive surface upon which the user writes may be regarded as a matrix of squares. The hardware built into the terminal then provides the host computer with both position and value data. When designing data capture documents for use with a hand print terminal it is thus feasible to define input strategies that depend upon either or both of these types of data values. Thus, it is extremely easy to implement a 1-of-N menu selection based upon position data alone. Similarly, string values can be input by repetitive application of this 1-of-N selection procedure. In general, the different kinds of input transactions used with the hand print terminal fall into four broad categories:

- (a) Single Peck
- (b) Multiple Peck
- (c) Character Stroking
- (d) Peck and Ring

Figure 6 Software Development Aids
(A) Use of State-Transistor Graphs

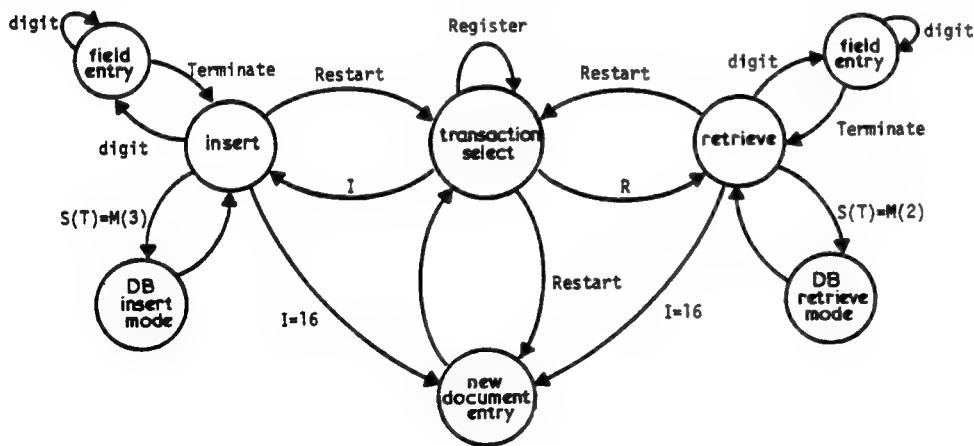

Each of these are illustrated schematically in figure 4.

The top of the diagram (case A) shows a three option horizontal menu. A document that utilises this type of menu would facilitate data entry by allowing the user to touch (or 'peck') the relevant option box with a pen or pencil. The coordinates of the point of contact could then be converted (by software in the host computer) into an appropriate information value.

Similarly, in case B, the twelve element horizontal menu allows numeric strings of digits to be entered by simply touching, in succession, the option boxes appropriate to the value that is to be input. The end-of-transaction box (EOT) is provided in order to facilitate the entry of variable length strings of digits.

In case C, the person entering the data would print alphabetic characters in the vacant boxes that are located to the right of the SURNAME keyword. If need be, the user can perform real time error correction by over-printing in boxes corresponding to characters that have been mis-recognised.

When entry of the data value is complete (and correct) the user simply packs the box containing the X-symbol.

The peck and ring transaction (case D) allows the user to define various items in documents containing pictorial information. Thus, in the example shown, the user might peck the DEFINE segment within the vertical menu located on the right-hand side of the document. This puts the system into object definition mode. Next, the user touches the sub-component of the picture that is to be defined (say, the first floor left-hand window). This is then 'ringed around' to define the physical area of the document that the item occupies. Data values associated with this item may now be entered into the computer system via an appropriate keyboard dialogue. This data might include part-number, stock level, unit cost, supplier, reorder level and so on. Once definition is complete, subsequent pecks of the pre-defined areas of the document may be used to retrieve and modify previously entered data values. The peck and ring transaction is one of the more advanced types of interaction modes and will not be discussed further. Instead, we concentrate on simple peck and character stroking transactions.

The remaining section of this paper describes a simple case study that is designed to illustrate the techniques of software development for a hand print terminal. Only two of the four basic transaction types are employed for data entry.

THE CASE STUDY

The entry of information into a data base and subsequent retrieval of values from it are nowadays two commonly employed

operations. In the case study described here, we show how these operations may be implemented by printing decimal digits at appropriate points on a specially designed data capture document similar to that shown in figure 5. Such a document would permit a machine operator to record the running conditions (temperature and flow rate) of an electrical pump as a function of time. This is achieved by filling in successive vacant rows of boxes in each of the three tables labelled TIME, TEMP and FLOW. Inspection of figure 5 reveals that certain of the rows contain data values while others remain yet to be filled. The next set of data would be entered into the sequence of boxes that constitute the seventh row of each of the tables.

As well as entering data into the system for storage the operator may wish to interrogate the past history of the machine's performance. This may be achieved by retrieving and examining previously entered data. Two types of retrieval request could be made: single key and double key. The first of these would require the terminal operator to enter a value for any one of the three possible search keys (time, temperature or flow). The system would then respond by supplying the values of the remaining two unknown process variables. Thus, when in retrieval mode, entry of a value in the temperature table would cause the software in the host computer to find the time and flow values corresponding to the given machine running temperature. Similarly, if two search key values are entered (there are three possible combinations) then the software would determine the unknown value of the third variable. For example, entry of a temperature and a flow value would cause the software in the host to retrieve the time at which those machine conditions were observed and recorded.

Inspection of the data capture document shown in figure 5 will reveal that there are three distinct areas used by the terminal operator. At the top there is a horizontal menu containing four option boxes. Beneath this are the three vertical tables used for the entry of data values; these permit up to twelve transactions to be performed before the document has to be replaced by a new one. The third area, the Terminate Transaction or T-box, is used to indicate the successful completion of the entry of individual numeric data fields.

The procedure for using the document and hand print terminal would be as follows. The host computer would prompt the user (via the terminal's display) to position the data capture document on the pressure sensitive surface. This would then be registered by 'ticking' the REGISTER

box. Document registration allows the built-in microcomputer to compute correction factors that compensate for any misalignment of the document. Once registered, the user can select a transaction type by touching either the RETRIEVE box or the INSERT box. The selected transaction type then prevails until one or other of two conditions arise. If, at any time, the user pecks the RESTART box then the system immediately reverts to 'command' mode. This then allows the selection of an alternative transaction. A similar thing happens, automatically, when the data capture document becomes full and has to be replaced by another.

FIGURE 7 DATA CAPTURE ALGORITHMS

1. Print "Enter Document";
2. Wait(10);
Getchar(R,C,A);
If R=1 and C=16 then goto 3;
Goto 1;
3. Print "Please Register Document";
Getchar(R,C,A);
If R=1 and C=16 and (A="/" or A=" ") then goto 4;
Goto 3;
4. Print "Document Registered OK";
I=4;
Wait(10);
5. Print "Enter Transaction Type";
6. Getchar(R,C,A);
If R=1 and C=3 then goto 8; (*retrieve operation*)
If R=1 and C=30 then goto 7; (*insert operation*)
If R=1 and C=21 then goto 1; (*restart operation*)
Goto 6;
7. Print "Enter TIME Value";
7.1 Getchar(R,C,A);
If R=1 and C=21 then goto 5; (*restart operation*)
If R=1 then goto 7.2;
If C isin [5..8] and A isin [0..9]
then begin;
 Update time value;
 Update display;
 Goto 7.1;
end;
else goto 7.1;
- 7.2 If R isin [15..16] and C isin [30..31]
then begin;
 Enter time value into data base buffer;
 Goto 7.3;
end;
else goto 7.1;
- 7.3 Print "Enter TEMP Value";
Getchar(R,C,A);
0
0
0
etc.
- 7.5 Print "Enter FLOW Value";
Getchar(R,C,A);
0
0
0
etc.
- 7.7 Update data base system;
Increment I;
If I > 15 then begin;
 I=4;
 Print "Enter New Document";
 Goto 2;
end;
else goto 7;
- 8.0 Print "Enter Retrieval Request";
Temp=null; Time=null; Flow=null; Count=0;

Suppose a new document has been placed on the terminal's writing surface and that the system is in transaction selection mode. It is required to enter some machine status data into the computer storage system. The operator pecks the INSERT box thereby selecting data insertion mode. A time value (0336) is then written in the first row of the left-most table and the T-box then touched. Next, a temperature value (136) is printed in the central table and the T-box pecked again. Finally, the flow value (4782 — there is an implied decimal point) is written in the right-most table and the T-box pecked once more. As soon as

Continued on Page 67.

- 8.1 Getchar(R,C,A);
If R=1 and C=21 then goto 5;
If R isin [15..16] and C isin [30..31] and Count=1
then begin;
 Count=0;
 Enter Data Base Retrieve mode;
 Increment I;
 If I > 15 then begin;
 I=4;
 Print "Enter New Document";
 Goto 2; end;
 else goto 8.0;
end;
If R=1 then goto 8.1;
- 8.2 If C isin [5..8] and A isin [0..9] and time=null
then enter time-field routine; (*Step 8.2*)
else if C isin [12..14] and A isin [0..9] and temp=null
then enter temp-field routine; (*Step 8.3*)
else if (C isin [17..18] or C isin [20..21]) and A isin [0..9] and flow=null
then enter field-flow routine; (*Step 8.4*)
else goto 8.1;
If restart then goto 5;
If count=1 then goto 8.1
else begin;
 Count=0;
 Enter Data Base Retrieve mode;
 Increment I;
 If I > 15 then begin;
 I=4;
 Print "Enter New Document";
 Goto 2;
 end;
else goto 8.0;
end;
- 8.21 Time-Field Routine;
Update time value;
Display time value;
Getchar(R,C,A);
If R=1 and C=21
then begin;
 Time=null; Temp=null; Flow=null;
 Restart=true;
 Exit;
end;
If R isin [15..16] and C isin [30..31]
then begin;
 Enter time value into data base buffer;
 Increment Count;
 Exit;
end;
- 8.22 Temp-Field Routine;
etc.
- 8.3 Flow-Field Routine;
etc.
- 8.4 Flow-Field Routine;
etc.

Croydon Micros

FOR THE COMPLETE ANSWER



IF YOU WANT ASSISTANCE IN CHOOSING A MICRO FOR BUSINESS, OR
YOUR HOME,

COME TO OUR NEW CROYDON PREMISES

FOR PROFESSIONAL SERVICE

Ring Malcolm Greenaway now on:

01-689 4349

ELTRON HOUSE, 20 WHITEHORSE ROAD, CROYDON CR9 2NA

MZ-80A £477 Complete with Disks & Printer £1799

MZ-80B £999 Complete with Disks & Printer £2299

IBM from £2800. EXTEL with networks from £7000

ATHANA & BASF disks from £15.20. PAPER & RIBBONS

EPSON F/T1 £349. TRANSTEC 12" Green Monitor £85

* Specialists in Interface Design & Manufacture *

Prices exclude VAT and Delivery FRONTREALM LTD (T/A) All major Credit Cards accepted

"We have thought seriously about calling this machine NOT THE BBC COMPUTER", said Clive Sinclair when he announced the Spectrum. It was generally taken as an example of Clive Sinclair's dry wit at the time; but I think he meant it.

In many respects, it's a shame he said it, and it's a shame that Sinclair has let the BBCF computer get so far under his skin, because I don't feel the comparison is relevant. Neither is it as favourable to Sinclair as his publicity machine says.

My opinion of what the Spectrum is can be summed up like this: "Sinclair has taken the incredibly successful design of the ZX81, and has improved it beyond all recognition. He has overcome every reservation which everybody has ever had about that machine — its rather dodgy cassette tape interface, its unfriendly flat keyboard, its very difficult machine code interface, and its low-quality black-and-white display — and has not only 'got it right' but has turned them all into assets. And he has (probably) struck an ideal balance between what the ZX81 users can afford, and what extras they are prepared to pay extra for. But the machine is one of the slowest on the market. And anybody who has got the money for the BBC micro is letting himself in for some envious moments if he opts for the Spectrum instead, because the gap in price reflects a real gap in features".

The beauty of the ZX81 was that it was cheap. It was the cheapest "real" computer in the world, and with it, hundreds of thousands of people have taken the plunge and found: "Gracious! I can understand programming!" And they've done it without risking their total spare money budget.

The Spectrum is not as cheap — by now, surely everybody knows that we pay £125 for a Spectrum with 16 Kbytes of operating software and 16 Kbytes of user memory. By contrast, a ZX81 with 16 Kbytes of user memory now costs £100, because the add-on memory pack price has been cut.

Sinclair thinks that there are still enough people around who can't afford more than the £60 which it costs to get a ZX81 (if you know where to buy) that he can carry on making the beast. But he also thinks that enough of them have decided that they need the extra 16 K rampack, to make them take a £125 computer with extra features, seriously.

So: what are these "extra features" that we have to judge worth the extra £25?

Machine Summary

The first, unfortunately, is one we have to take on trust. Unfortunately, because it is undoubtedly the most important — a direct access storage device for £50 — the thing called the Microdrive.

Taking The Lid the SPECTRUM

by Guy Kewney



The second is an enhanced Basic language. It still omits the one thing which I think essential in such a machine, and that is easy access to machine code, but for all its faults, Basic is useable, and widely known. "Better", here, risks becoming the enemy of "good" (as Adam Osborne always tells me when I suggest possible improvements to something) and obviously Basic is good enough to use. Especially with new features.

The third is colour and programmable graphics.

Fourth, a respectable keyboard. Not a good keyboard, and with its faults, but at least you can use it without wondering if your finger has slipped off the key.

Fifth, sound generation. There is a silly design fault here, and it is one which I can't forgive — the sound is inaudibly soft, and it takes a tedious performance of plugging and unplugging to amplify it.

Sixth, an operating system. We never had one on the ZX81, and sadly we missed it, too. We get screen handling, tape handling, terminals handling, and network handling where previously we only had program save and load.

Seventh, we have auto-repeat on keys. Perhaps I should have put this first — it's something I'd pay extra £25 for, on the ZX81, without asking any more questions beyond "who do I make the cheque out to?"

And of course, there are a bag-full of other little things. Words Can have small (lower-case) letters as well as capitals. You can time things. You can write your own Basic commands. You don't have to plug the add-on memory pack on. There is a network. And a lot more.

Okay, we are probably on the point of losing our fellow-readers who don't have a ZX81, and don't know what it does.

The Spectrum in context

The first thing which a prospective buyer would notice about the Sinclair (any Sinclair) if they took one home for a week, is that there is only one thing to learn. On all other computers, you have to learn the language, and if you are not already familiar with typewriters, you have to learn the keyboard. On this machine, the language is the keyboard.

off

In other words, instead of typing PRINT, you press the P key, and the machine types PRINT for you.

It sounds wonderful, until you realise that there are around 90 different words in the Basic language. There are 40 keys on the Sinclair keyboard, and they also have to carry the numbers 0 to 9, the letters A to Z, all the punctuation, calculation, and editing functions, plus colour codes. At that point, only the fact that you have spent all your money on the machine persuades you to stick at it, and learn the way round the keyboard.

But the advantages go deep, for all their apparent elusiveness. On a Sinclair, you are never suddenly stuck for a command, and have to page through the manual to find it and how to spell it (and how many brackets (not forgetting how many layers of bracket (assuming you only use one form of bracket))) because it's there in front of you. Nine times out of ten, if you do use the command incorrectly, the machine will show you exactly where you have gone wrong.

To illustrate what I mean: on the Acorn BBCmicro, it is possible to put spaces into Basic statements where spaces should not be. PRINT TAB 20 should move you 20 spaces along the line on the screen. But it must not have a space between TAB and 20, or the machine thinks TAB is the label of some specified number (a variable) and hunts through the list of variables before stopping the program with a terse message to say that there is no such variable.

It can take a very long time before you realise that a space is causing your problem. And this is exactly the sort of frustrating thing which the Sinclair design prevents.

The drawback of the system can be seen from a glance at the keys with numbers 2, 3, 4, 5, 6, and 7 on them. Each key has six different possible meanings, and you can search for the one you need for minutes at a time before you find it.

Fortunately for Sinclair, he doesn't have to argue about the fact that users find this acceptable. His ZX81 sales have proved it — at least for a rock-bottom price machine.

The other thing about the Sinclair which newcomers need to be told, is the editor.

Basic as a language has one enormous advantage over anything that came before, and that is its ability to sort a program into order, no matter what order you write it. As long as the line number is right, the machine editor will put it in the right place.

However things have moved on since Basic was invented, and a lot of people who write Basic editors have failed to realise this.

For a start, we no longer talk to computers by typing on a Teletype, with paper in it. Computers today have video displays. Originally, video displays were designed to behave as though they were paper in a printing device — they were known as "glass Teletypes" — so that the software which ran on the computer would continue to run when a glass TTY was connected. That is, the letters that the user typed appeared on the screen one by one, as if an invisible key was hitting it. And after typing a letter, the market or "cursor" which showed where the next letter would be typed, moved to the right, as if a print head had moved across the paper.

And, naturally, once you had written a whole line, the paper moved up. It was gone, dirty, covered in ink. Even if it wasn't actually there. Even if it was really a character generated by having the computer look at an area of memory, and display the characters it found there.

Basic programs fit into memory. It is quite easy to have the computer look through the area of memory in which it has stored the Basic program characters, and show what is there.

But because, long ago, people pretended that there was a bit of paper in a teleprinter, Basic doesn't normally look at an area of memory. Instead, it digs out a few lines from that area of memory (the program area) and moves them into another area (the display memory) where they are shown on the screen. If you want to look at the next line of Basic, it gets printed at the bottom of the paper. If you want to look at the previous line, you have to erase the whole video memory, and go back to the program area, and dig out a previous line, and re-write that into the video memory. Just as if you were printing a new page.

Sinclair's Basic doesn't do anything so potty. If you have LISTed lines 400 to 500, and realise that you want to see line 390, you just move the cursor up. Line 500 probably slips off the bottom of the screen, and line 390 appears at the top.

If you type line 30, then line 50, then line 10, then line 60, then line 20, then line 40, then line 10 again, most Basic machines would show you a "listing" like this:

```
30 REM THIRD LINE
50 REM FIFTH LINE
10 REM FIRST LINE
60 REM SIXTH LINE
20 REM SECOND LINE
40 REM FOURTH LINE
10 REM NEW FIRST LINE
```

which you're welcome to try to understand. To clarify things, you type LIST, and get the whole program, correctly ordered. But if the screen has room for 20 lines, and the program is 300 lines long, it all flashes by, and you end up with just the last 20. Sinclair Basic would always have them in order, at the top of the screen. And after it had LISTed the first 20 lines, it would stop, and ask you if you wanted more: "Scroll?" it asks politely.

The machine in detail

1 The Microdrive

This is almost certainly a floppy disc. The word "almost" goes in because as recently as April, people close to Sinclair were still unsure whether has new diskette design would be picked in preference to a very fast tape cartridge. Note — cartridge, not cassette. A cartridge, normally, is much faster and more controllable than a music compact cassette. It can move forward, back, fast and slow, under machine control. At best, the compact cassette can stop and start when the computer turns it off and on. Now, Clive says that it will be a diskette, and he is obviously counting heavily on that device to put him ahead of any competition. But that doesn't mean that he's giving anything away about it.

Apart from the fact that it will work with commands SAVE, VERIFY, LOAD AND MERGE which are available on the audio cassette interface, the manual refuses to admit to anything other than that there are some other keywords—OPEN#, CLOSE#, MOVE, ERASE, CAT, and FORMAT — which "will not work without Microdrive etc".

Data and program storage, for the time being, goes on the audio cassette. But this is a far nicer system than we used to have on the ZX81, where you could save a program or load it, and that was that. People who wanted to save data would have to disguise it as part of a program — in a long REM statement, for instance. Now, you can not only load and save data on tape as well as programs (and read them back in) but can check that they are correctly saved with the VERIFY command. You can also use the LINE command when saving a program, and when the program is LOADED again, it will start running all by itself from the line number. Most important, however, the machine actually shows you the name of the program or block which it has found on the tape. No human being will ever be able to distinguish one program from another by listening to the tape, and in the past, people were reduced to making vocal announcements before saving their programs. The opportunities for error were enormous.

It is even possible to dump a display to tape, and subsequently load it back onto the screen, with the command SAVE (or LOAD) "picture" CODE 16384,6912. The two numbers are the start address, and the length. They are automatically generated by the statement LOAD (or SAVE) "picture" SCREEN\$. Picture is the name of the block, of course.

MERGE is worth special mention — it lets you LOAD a program on top of a previous one, just as though the new lines were being typed in from the keyboard (without a NEW command). So the line numbers stay the same unless the MERGE program has a line of the same. Then, the new line is substituted.

SPECTRUM FEATURE

It is also possible to save the load new graphics characters (see below).

After all that enthusiasm, and adding that Sinclair has devised a system to make all this loading and saving much more reliable than on the ZX81, there are some reservations.

First, it may be more reliable than before, but it is far from reliable. My experience of using the system showed that around a quarter of the time, the LOAD command responded with "Tape loading error" rather than "OK". Providing the program was properly verified, that isn't the end of the world, but it is irritating (and I don't get that problem on the BBC machine).

Secondly, you have to muck about with the plugs and wires. On most tape recorders, plugging computer output to tape input and tape output to computer input, at the same time, generates feedback when saving programs.

Third, you have to press buttons. I've been spoiled for this by several cheap systems which will turn the tape recorder motor off and on, and while I know it costs money, I feel it's worth the cash to have it. Obviously when the Microdrive is available, this will fade into insignificance.

2 The Basic

In alphabetic order, here are the new keywords, first the functions, then the statements.

ATTR

It finds out what character attributes are in force at that point of the screen. That means: is the character flashing, inverse video, coloured, etc.

BIN

Defines the next number as a binary number, so that 100 is 4, etc. You would normally use it for defining your own graphics character, with the "1's going where you wanted INK dots. The manual includes a nice version of this for turning the graphics version of P, N, R, K, Q, and P into chess pieces.

IN

The result of reading the input port (of interest to machine code games writers, mainly).

INKEY\$

Changed from the ZX81 version to allow the new upper and lower case input as well.

SCREEN\$ USR

See above on tape handling. As well as its normal meaning of invoking a machine code routine, USR followed by a string is used to program your own characters (in graphics mode) like chess pieces, and so on.

Presumably somebody thought this was necessary, but I can't see why.

BEEP

There ought to be a law against describing the component in the Spectrum which responds to BEEP as a "loud" speaker. I shall refer to it as the "mouse" which grotesquely exaggerates its power. In a totally quiet room, you can detect a faint tone, which sounds for a certain time (you set it) on a certain note (starting with Middle C as 0, BEEP 1, 0 would play a one-second middle C). You can go up or down by whole or fractional semitones. To hear the thing, you have to play it through your amplifier, and if your amplifier is plugged in, you can't save programs. Silly.

(Note: the mouse automatically clicks its claws against the computer case each time you press a key. It would be a great idea, if you could actually hear it.)

BORDER

A number from 1 to 7 which sets the colour of the border round the edge of the screen.

BRIGHT

Some people say they can see the difference between the dark and bright versions of the eight available colours. I must have the wrong television set.

CAT

Disk command.

CIRCLE

Specify the centre point and the radius of a circle, and watch it draw itself there.

CLEAR

When used with a number, moves RAMTOP to that address, giving room for machine code routines or whatever, above.

CLOSE#

Disk command.

CONTINUE

Same as old CONT, but

politer.

DATA

A new (conventional) way of storing data in a program rather than the old REM statement fiddle which users got accustomed to on the ZX81.

DEF FN

Probably the most useful single addition. It allows the user to define a new Basic instruction and say how it works, and what variables it needs when it is used. The BBC micro has this. The BBC micro also has a PROCedure function, just as useful, which shares some of the work of the Sinclair FN. It can make life a great deal easier for

somebody else who is trying to sort out the mess you made in a program, if they can look up functions like this, rather than having to trace subroutines, and if only the function could be given a name, rather than a single letter identifier, it could be very helpful indeed.

Disk command.

One of the new graphics commands. It draws a line or an arc. Unlike BBC micro graphics, however, you have to take great care that you don't draw over points which aren't on the screen, or the program will stop with an error message. And because this machine has no ON ERROR GOTO function, your error trapping routine has to be absolutely foolproof. Thoughtless.

Disk command.

Exactly what it sounds like — one character at a time.

Disk command.

One of the most powerful new colour commands, and a delightfully clear, easy way of inventing a new Basic word. The number that follows INK (or PAPER) is interpreted as follows:

0	Black
1	blue
2	red
3	magenta
4	green
5	cyan (light blue)
6	yellow
7	white

There is also the option of 8 (which says that the character is the same as its background (!) and 9, which declares that there shall be a maximum contrast.

The choice of numbers for colours may seem random, but in fact the ascending order is also the order of grey scale in which they appear on black-and-white (or green) screens.

Of course the ZX81 had INPUT! But this time, the difference is startling, because we have INPUT AT and INPUT "Hello, can I have your number"; number, and several complicated and powerful permutations of that. There is one small carp here.

(Continued on Page 57)

In many situations a more complicated data structure is required than either static arrays and matrices (Parts 1 and 2 of this series) or the ordered sequences of stacks and queues (Parts 3 and 4) can give. These situations include those where the size of the data collection is varying as processing proceeds, where there is a need to insert, delete or amend the present structure or where the relationships between items is complex.

A structure that meets these requirements is the LIST, in fact not a single structure but a family of related structures.

The basic unit of the list is the "cell" or "node". This consists of several consecutive bytes or several elements in arrays that between them provide two types of information.

1. DATA i.e. the value(s) held by the cell.

2. LINKAGE information.

The linkage information consists of either references to adjacent cells in the structure or coded information to special cases like the top or bottom of the list.

Lists may be categorised by the system of linkage used in each cell.

SINGLY LINKED LISTS

Each cell in a singly linked list contains one linkage word or byte which is the address or element number of the next cell in the list. The end of the list may be denoted by a coded value (e.g. -1) instead of an address.

Such a structure can represent an ordered set of items e.g. an alphabetical list of spare parts. Let us look at this.

Consider two arrays:

10 DIM P\$(50)

20 DIM L(50)

The array P\$ will hold the values in the list, in this case the values of up to 50 spare parts. The array L is a numeric array and will hold the linkage information for the list cells. The two arrays are related by their subscripts, i.e. L(1) is the LINKAGE value for cell 1 while P\$(1) is the value of Cell 1, etc.

The following diagram shows a small part of both the arrays.

L	P\$
23	23 "DIODE"
24	24 "SOCKET"
25	25 "TRANSISTOR"
26	26 "PLUG"
27	27 "CAPACITOR"
28	28 "RESISTOR"
29	29 "SWITCH"

Understanding data structures

PART 3

by N. K. Freestone

The numbers next to the boxes represents the subscript of that element, while the value inside the box represents the value of the cell or the value of the link.

Cell 27 contains the Capacitor (P\$(27) = "CAPACITOR") while the linkage value points to cell 23 (L(27) = 23), this being the next cell in order.

Cell 23 points to cell 26

Cell 26 points to cell 28

Cell 28 points to cell 24

Cell 24 points to cell 29

Cell 29 points to cell 25

Cell 25 points to cell 30

(not on the diagram)

Each cell has its corresponding description so the order of the items represented here is:

Capacitor

Diode

Plug

Resistor

Socket

Switch

Transistor

etc.

It can be seen that the cells occur in a particular order which is determined by the link values but that this order is not the order in which the elements occur in the arrays. Since it follows that the first cell is probably not in the first element of the array it is usual to have a separate variable (say T, the Top of the list) to point to the first cell. In our example T would equal 27.

Such a LIST structure enables us to gain access to the Nth cell simply by following the pointers. Once the required cell is found we can insert or delete cells from this point. Various operations can be carried out on the whole list, such as splitting it into two lists, counting the number of cells or copying all or some of it.

Manipulation of these structures may be carried out either by:

1. A specifically designed list processing language.
2. Direct addressing to the cells; e.g. in Assembler, or using Peek and Poke in BASIC, or with languages like CORAL which allow direct addressing to memory.

3. By references to array elements in languages like BASIC. This is the method to be used in the following examples.

Let us look at some examples of the operations mentioned earlier, as applied to our list of spare parts.

1. FOLLOWING THE POINTERS

This example routine will print all the spare parts in the list by following the pointers, starting at the top of the list. A working pointer (W) is used to point to the "current item" and the end of the list is marked by a pointer value of -1.

1000 LET W = T get pointer to first item

1010 IF W = -1 check for end of list
THEN GOTO 1050

1020 PRINT if not end then print
P\$(W) the item

1030 LET = L(W) set working pointer
to point to next
item in list

1040 GOTO 1010 go round again

1050 PRINT "END OF
LIST" end of list has been found

1060 RETURN continue

After each part is printed (Line 1030) the working pointer is set to the value of the link part of the cell so that it references the next cell.

Note that this routine can very easily be changed to perform a number of other functions e.g. to search a list for a particular value substitute an IF statement for the PRINT statement and test for the desired value and jump to an appropriate place when the item is found. In this case processing will continue from Line 1050 in the event of the list not containing the sought for value.

2. ADDING ITEMS TO THE LIST

In order that items may be added to a list it is obviously necessary to have some otherwise unused cells available into which new values can be placed.

FEATURE

Assuming that the whereabouts of these cells is known it is a straight forward matter to place the new value in the DATA area of the cell.

Some thought must be given however to maintaining the correct pattern of LINKS to the new cell.

Three cases arise here:

a) Adding the item to the end of the list. is the simplest case of the three. Since, in our example, the last item has a LINK value of -1 then the new cells link should be set to this value because it will be the last item in the list. Secondly the cell currently on the end of the list must have its link value changed from -1 to point to the new item. This establishes the proper links to the new cell.

b) Adding an item to the top of the list also requires two operations. The value of the variable T (which points to the top cell) must be entered in the LINK part of the new cell so that it points to the old top cell and the value of T must be changed to point to the new cell.

c) Adding an item into the middle of a singly linked list is slightly more complicated. A search is required to locate the two cells between which the new one will be placed. This is simplified if it is possible to locate the cell which will immediately precede the new one in the sequence. In this case the LINK value automatically identifies the cell that will follow the new one.

Usually however it is necessary to search down the list until a cell is found that has a value greater than the new one. The new cell is then inserted before the one found in the list. Since each cell has a pointer to the next cell, but not to the previous cell in sequence, it will be necessary to keep a "mental note" during the search of the number of the previous cell at each step through the list.

This can be done by adding the lines

**1005 LET P = -1
1025 LET P = W**

to the routine given earlier. Assuming that the new cell value to be added is in NS\$, and S is the number of a spare cell to put the new value in, the routine to add new cells becomes

```
1000 LET W = T
1005 LET P = -1
1010 IF W = -1 THEN GOTO 1050
1020 IF PS(W)/2 = NS THEN GOTO 1050
1025 LET P = W
1030 LET W = L(W)
1040 GOTO 1010
1050 LET PS(S) = NS
1060 LET L(S) = W
1070 IF P = -1 THEN GOTO 1100
1080 LET L(P) = S
1090 RETURN
1100 LET T = S
1110 RETURN
```

NOTES:

1005 Sets P so we can detect when to add the new cell to the top of the list, in conjunction with line 1070.
1010 Detects the end of the list.
1020 Check the values during the search.
1025-1040 Save the pointer value when the IF statement fails and go round again.
1050-1060 Set up the new cell when the IF Test is successful.
1070 Tests for the special case of adding the item to the top of the list.
1080 Adjusts the link of the cell before the new one to point to the new cell while . . .
1100 Adjusts the Top pointer(T) to point to the new cell when it is the first one in the list.

Some thought must also be given to removing an item from the list. Again, the same three possibilities exist depending on the items position in the list. In each case the item is removed by making the link of the cell before, equal to the link value of the cell to be removed. Since the link of the cell to be removed points to the next cell, placing this value in the previous cell will create a chain of pointers which bypasses the deleted cell.

Before:



After:



To remove the first cell the pointer(T) to the top cell must be changed to point to the second cell thus bypassing the deleted cell and to remove the last cell the end-of-list marker value (-1 in the example) must be placed in the second to last cell thus terminating the list there.

Amendment of a list is achieved either by altering the value of a cell without affecting the links or by deleting the cell from one position in the list and adding it again in another.

Having discussed this processing in some detail let us look at some other list structures the processing of which is very similar to that already described.

CIRCULAR LISTS

Sometimes it is convenient to make a list like the one described above circular. This can be achieved by using the LINK of the last cell to point back to the first cell. This can be useful where there is some relationship between the ends of the list as well as between adjacent items.

SPARE CELL LISTS

It was mentioned earlier while discussing the addition of a new cell to a list that it is necessary to know the location of a spare cell into which the data can be placed. It is common practice to compile all unused cells into a list with their own pointer say S (for spares). This allows easy access to spare cells for addition to other lists and cells deleted from other lists can be linked back into the Spare Cells List for later re-use.

DOUBLY LINKED LISTS

A single cell can be removed from a list if its "address" is known, but it does require a complete circuit around a circularly linked list in order to locate the neighbouring cells that must be linked together. It is necessary to read the whole list in order to locate the previous cell to the one being deleted. As this is a frequent operation on lists, which is particularly time consuming if the list is a long one, many lists maintain both forward and backward pointers from each cell. A doubly linked list:



Thus by following the first pointer in each cell the list may be read forwards in order, and by following the second pointer in each cell the list may be read backwards.

The extra linkage values do not necessarily involve much additional storage requirements as both pointers can sometimes share one word of store.

Now if we know the location of a cell it can be removed from its list without even knowing which list is involved because the two pointers identify the two cells which must be linked. Thus in a program that uses several doubly linked lists a single routine can perform all cell deletions when it receives a single parameter giving the address of the cell concerned.

All routines manipulating these lists must of course ensure that both sets of pointers are correctly adjusted in order to maintain correct cell linkage.

THREADED LISTS

When part of the data in a list is information that takes a limited range of values e.g. whether a person is male or female, it may be worthwhile setting up additional pointers in the list to the next cell of the same type. When a search of the list is performed for criterion which includes the fact that the person is (say) female, we can follow these additional pointers and so search only a subset of the whole list. A series of header pointers would give the first cell containing an item of each type.

Multi-thread lists can also save space by avoiding data duplication. In a list of (say) stock items it may be required to access the list in several different orders e.g. alphabetically on the description, numerically on the part number or by delivery date order. If a three sets of pointers are used to link the list in each order then duplicate copies of the list,


each in a different order, or the need to repeatedly sort a single list is avoided.

While we have lost some of the ease of inserting and deleting items from such a list, it can be analysed comparatively simply.

REPRESENTATION OF TREES BY LISTS

The various elements in a Tree Structure may be positioned in a List, but the links which should be maintained depend upon the application for which the tree is to be used. Any Tree Structure can be represented as a Binary Tree and this will be the only method described here.

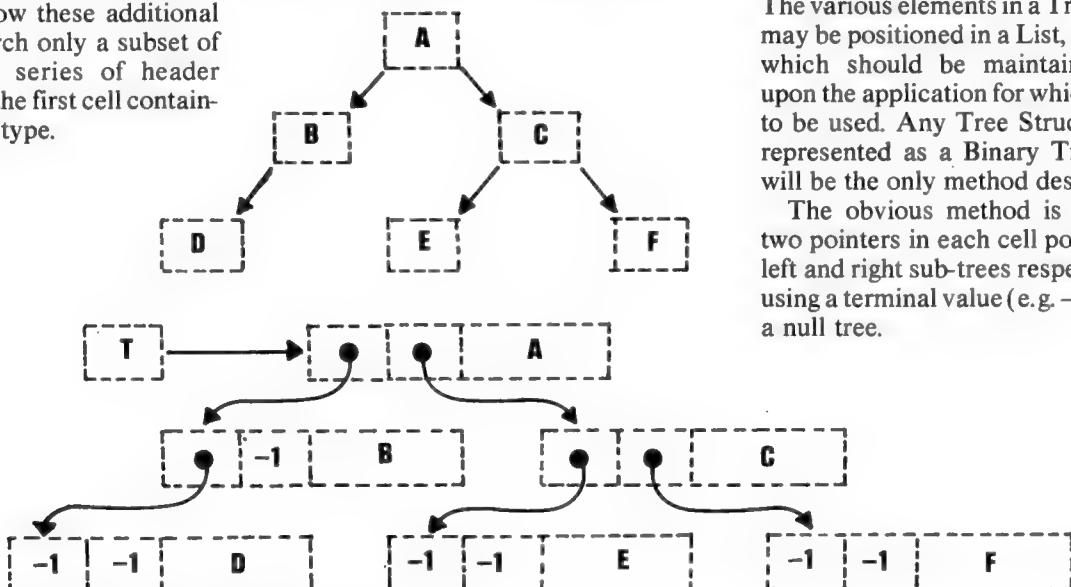The obvious method is to maintain two pointers in each cell pointing to the left and right sub-trees respectively, and using a terminal value (e.g. -1) to denote a null tree.



EG. A tree (T) and the corresponding data and links.



5HZ TO 100MHZ

TOMORROW'S TOOLS TODAY

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited Dept. 34D
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

Instant frequency indication from 5Hz to 100MHz; no range selection problems; a brilliant 8-digit LED display; mains or battery operation; an accuracy of 4 parts per million ± 1 count; and totally automatic operation — all this for only £85.00* with GSC's new Max-100 frequency counter.

Just take a look at our spec. Where else could you find anything similar at the price? *Frequency range 5Hz - 100 MHz *Input impedance 1M shunted by 10pF *Sensitivity 30mV from 1KHz up to 50MHz; 120mV r.m.s. over full frequency range *Timebase accuracy ± 4 parts in 10⁶ (from 5 to 45°C) *Maximum aging rate 10 parts in 10⁶ per year *Over-frequency indication *Low-battery-power alarm *Operates from dry or rechargeable cells, an external 7.5 to 10VDC supply, or a car battery (via an adaptor) *Dimensions: 45 x 187 x 143mm *Options: 12V adaptor; battery eliminator; r.f. antenna, low-loss r.f. tap, carrying case.

Fill in the coupon for further details . . .

*price excludes post, packing and VAT

G.S.C. (UK) Limited, Dept. 34D, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

MAX 100	FREQ. COUNTER	Unit price inc P & P 15% VAT £100.05	Qty _____	Read _____
---------	---------------	--------------------------------------	-----------	------------

Name _____
Address _____

I enclose cheque/P.O. for £ _____ or debit my Barclaycard/Access/
American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The G.S.C. 24 hour, 5 day a week service.
Telephone (0799) 21682 and give us your Barclaycard, Access, American
Express number and your order will be in the post immediately.

For Free
catalogue
tick box

Editorial/Circulation
67 High Street,
Daventry,
Northampton,
NN11 4BQ
Tel: 03272 71841

**Publisher/Editorial
Director**
David Raven

Production Editor
Glenn Price
Tel: 03272 76797

Group Sales Director
R.E. Pynegar

Advertising
(03272) 71702

Editorial
Ann Houghton
03272 76797

Subscription Control
Suzanne Gilbert

**Advertisement
Manager**
Diana Ward.

Distribution
Seymour Press Ltd
334 Brixton Road
London

Published by
Stagpark Limited
Russell Anderson House
18 Hamilton Road
Nottingham

Production
Newstead Publishing Ltd
Nottingham

Printed by
JSCG Lincoln

Computer Project 17

Programming a hand print terminal. Philip Barker takes you through the mechanisms of operation and types of transaction.

Taking the lid off The Spectrum 22

Guy Kewney takes a details look at the new release from Sinclair Research.

Understanding Data Structures 25

Part three of our series, on the alternatives, when you run out of games programs for your micro.

ZX81 Motherboard 30

Building a motherboard allows several different circuits to be connected at the same time, greatly increasing the scope of the system. This project will enable you to read temperatures, inside & out or for example, operate a central heating system.

Z80 Self Assembly 33

Ian Sinclair describes the unique features of using "Menta". A Z80 assembler which contains both hardware and software.

Nascom 'Micoed' Review 40

Interfacing the BBC Micro 44

If you are interested in using your BBC Micro to control things such as model railways or racing car circuits, this article will be of help.

Journey to the stars 51

Will it ever be possible to travel to the stars within a reasonable time period?

ZX81 Battery Back Up 54

A solution to the problems of mains failure with the resulting loss of memory.

Printerfacing The Atom 59

How to set up your own interface and replace the centronics routine with one that runs be it serial or parallel.

Computer Aided Design 65

The last in our series for defining the performance of a complete network from the component values entered. This month, 'Transformer & Line'.

International News	7
Computer Products News	10
Spotlight	12
Letters	16
Kids Corner	62
Talking Shop	69
Kit Review	71
Books Review	75

Electronics & Computing Monthly is normally published on the second Friday of each month.

© copyright Stagpark Limited, 1981. Reasonable care is taken to avoid errors in this magazine however, no liability is accepted for any mistakes which may occur. No material in this publication may be reproduced in any way without the written consent of the publishers. Subscription rates, UK £9.50 incl: post. For overseas rates apply to Circulation Control, 67 High Street, Daventry, Northants.

MicroValue

THE NEW


SHARP MZ80A

**£A75
+VAT**

**Electronic magnificence
from Sharp**

Z80A C.P.U. • 48K RAM • 4K ROM • Industry standard QWERTY keyboard with numeric pad • 9" GREEN C.R.T. • 1200 bd cassette • Music & sound • Real time clock • Enhanced BASIC • Full editing facilities • Internal expansion

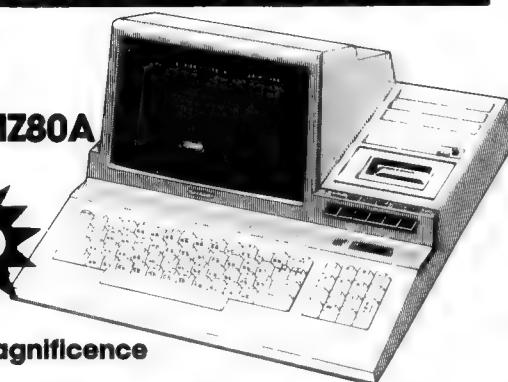FREE SOFTWARE! Home budget, bank reconciliation, SPACE INVADERS, STAR TREK, SCRABBLE, bank loan calculator, mortgage calculator + 7 other games.
Educational — Geography, Maths, Spelling + 4 part BASIC tutorial.



Quantum HI-RES FOR MZ80K

High resolution plotting on your MZ80K down to a resolution of a single dot within a character cell.

A new BASIC is supplied with the following additional commands:
LINE, WIPE, G SET, G RESET

**NEW FROM
Quantum**

Quantum HI-COPY FOR MZ80K

This combination of hardware & software not only allows printing of the full Sharp character set, but allows a full High Resolution print of the actual screen if used with the Hi-Res graphics option.

Available in 2 versions

QUANTUM GP100A HI-COPY

SEIKOSHA GP100A, Interface, ROMS & screen dump BASIC.

£300.00 + VAT
Including printer

QUANTUM EPSON HI-COPY


Interface & ROMS & screen dump BASIC suitable for use with any EPSON PRINTER.

£90.00 + VAT excluding printer

SPECIAL OFFER Quantum Hi-Res Only £70.00 if purchased with
Quantum GP100A Hi-Copy
Quantum MZ80K Games Packs 1-5 £5.00 + VAT each

EPSON PRINTERS

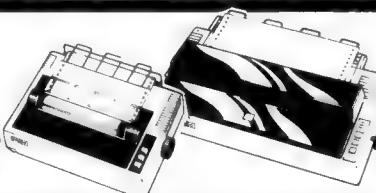Epson MX80T . . £395 + VAT
Epson MX80FT2 £465 + VAT
Epson MX100 . . £575 + VAT



YOUR LOCAL MicroValue DEALER

All the products on these two pages are available while stocks last from the MicroValue dealers listed on right (Mail order enquiries should telephone for delivery dates and post and packing costs.) Access and Barclaycard welcome



AMERSHAM, BUCKS.
Interface Components Ltd.,
Oakfield Corner,
Sycamore Road.
Tel: (02403) 22307. Tx: 837788.

Gemini GALAXY 1 CP/M COMPUTER SYSTEM

A Multiboard based 80-BUS computer

HARDWARE


- ★ Twin Z80A CP/M System.
- ★ 64K Dynamic RAM.
- ★ 800K Disk Storage (Formatted).
- ★ 80x25 Screen Format.
- ★ Inverse Video.
- ★ Prog Character Generator.
- ★ 160x75 Pixel Graphics.
- ★ Centronics Parallel I/O.
- ★ RS232 I/O.
- ★ Light pen interface.
- ★ 59-Key ASCII Keyboard.

SOFTWARE INCLUDED

- ★ Full 64K CP/M 2.2 with screen edit facility.
- ★ COMAL-80 structured BASIC.
- ★ GEM ZAP Assembler/Editor.
- ★ GEM PEN Text Editor.
- ★ GEM DEBUG debugging software.

**MicroValue price
£1,450
+VAT**

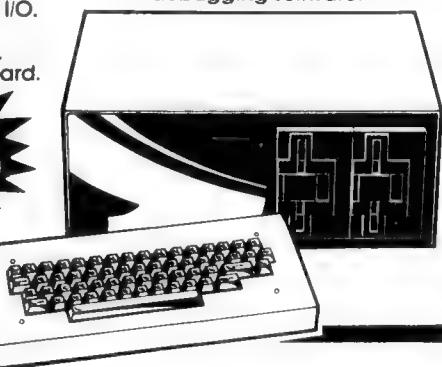Suggested monitor for use with the Galaxy: £150 + VAT



QUIBS-Quantum INTEGRATED BUSINESS SYSTEM

A business accounts package developed for the Galaxy, menu driven.

1. **SALES LEDGER** full VAT reports, statement, credit note + invoice facilities.
2. **PURCHASE LEDGER** full VAT reports, statements, remittances.
3. **NOMINAL LEDGER** 250 analysis heads, trial balances, accruals & repayments.
4. **STOCK CONTROL** costing reports, price lists, etc..

The system is fully integrated. Comprehensive audit trails are printed. Specially developed for Multiboard based systems.

£400 + VAT
Specify disk format when ordering

Quantum DATAFLOW

A Data base management and information retrieval package. Allows searching, sorting, report printing, file printing and label printing. Anything which is filed manually can be filed more efficiently with DATAFLOW.

£120 + VAT
Specify disk format when ordering


DAISY WHEELS ARE DOWN — ONLY £485 + VAT

For less than the price of some dot matrix printers, the Smith-Corona TP-1 brings the benefits of daisywheel printers within the reach of most micro users. Now letters, documents, forms, invoices, reports, price lists, etc., can be printed with the quality that until now was not readily affordable.

- ★ Simple reliable mechanism.
- ★ Serial or Parallel interface.
- ★ IEEE option.
- ★ Single sheet and fanfold paper.

FANFOLD PAPER

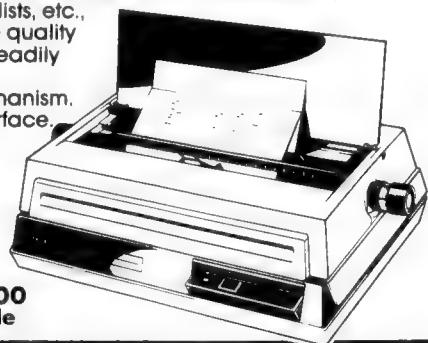2,000 SHEETS £16.00
Music Paper available



BRISTOL
Target Electronics,
16 Cherry Lane.
Tel: (0272) 421196

EDINBURGH
Computer Interfacing & Equipment Ltd.,
19 Roseburn Terrace.
Tel: (031) 337 5611

PART 3

by Owen Bishop

ZX81 MOTHERBOARD

The motherboard allows several different circuits to be connected to the ZX-81 at the same time, greatly increasing the scope of the system. For example, if you have the controller card which was described last month and then make the thermometer board (next month), the computer can read temperatures indoors and outdoors and operate the domestic heating system accordingly. With the addition of the real-time clock card, the computer knows the time of day, and what day of the week it is, and can run the heating system on different schedules at different times. In the field of model control, an assortment of sensors can provide input by way of a sensor card, and the controller card is made to take appropriate action.

This motherboard takes up to 3 cards. By setting it out on a wider board the design can be extended to include more cards than this. It allows the printer and 16K RAM pack to be plugged in at the same time as the cards, so you can assemble a really complicated system.

Another feature of the motherboard is its 5V regulated power supply. As can be seen from the pattern in Fig. 2, the 5V line from the ZX-81 continues across the board to the edge connector, but does not go to the sockets. The on-board 5V supply to the sockets comes from the regulator (IC1, Fig. 3). This avoids the risk of overloading the 5V regulator of the computer board. The on-board regulator derives its power from the unregulated 9V supply of the computer. There is the risk that if the printer, the extra RAM and three cards which require high current are all operating at once, the 9V transformer may be overloaded. This risk can be assessed only by adding together the requirements of each item connected to the system, not forgetting the requirements of the computer itself. The ZX Power Supply is rated at 700mA, which allows 600mA for the computer and 100mA for attached cards or 16K RAM, so there is little to spare. The controller card is probably one which requires more than average current. In the quiescent state it draws 25mA, but requires additional current for every switch that is turned on. Each relay takes 18mA when energised from the 9V supply. If more than 2 relays are to be used, it is essential to provide more

power. Adding the printer increases basic power requirements to 1.2A, not allowing anything for the cards. A total of about 2A should be sufficient for most systems which include the printer, the 16K RAM and three cards on the mother-board. This can be supplied from a single 2A power pack, or a 700mA Sinclair power pack can be used for the computer, with the mother-board being powered from a separate 1.2A (minimum) pack. The wiring is shown in Fig. 4.

SYSTEM BUS

As explained last month, the cards all have the same arrangement of lines at their edge-connectors so that they are fully compatible with each other and with the computer. This arrangement follows closely that of the ZX-81 edge-connector, so as to make interwiring as straightforward as possible. The ZX-PLUS system bus is listed in Table 1.

CONSTRUCTION

The mother board has been designed to fit on to a double-sided copper-clad board of standard size. Since the dimen-

sions of this board are exactly 8" by 3.75" and the edge connectors have 0.1" pitch, all dimensions are in inches instead of their metric equivalents. The ZX-81 board is double-sided so, to make the edge connector of the mother board compatible with the printer and 16K RAM, this board must be double-sided too. However, it is much simpler to construct the cards on single-sided stripboard, so the mother board provides a single-sided array at its sockets. There is just room for 3 sockets, and these can be added one at a time as the system grows.

With many close parallel lines to be etched, it is highly recommended that rub-down etch-resistant tracks be used. These are usually printed 0.1" apart, and they can be cut into blocks of parallel tracks of suitable length. Several tracks are rubbed down in one operation. Circular pads are recommended for the points where the terminal pins are to be soldered, and two 23-way edge-connector patterns are also needed.

The design occupies the full width of the standard board. The edge-connector lug is formed simply by cutting away the two rectangles of board to its left and right. Make a reference mark in pencil on

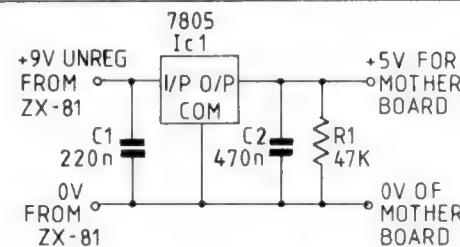


Figure 3 Circuit of the regulated 5v supply for the mother board


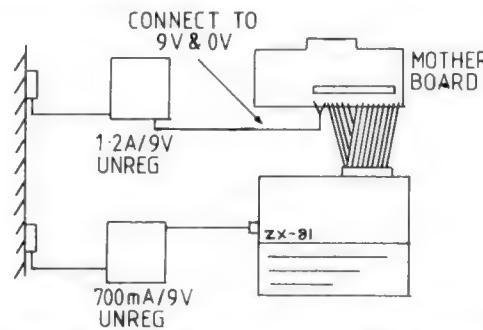


Figure 4 Using two power packs. The 9v line between the ZX81 and the mother board is omitted, but the OV Line and the 5v lines are retained.

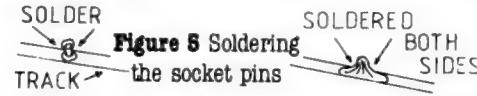

the edge of the edge-connector lug to coincide with the intended position of the RFSH and ROM C/S' tracks. The mark should be exactly 2.7" from the right-hand end of the board. This mark is essential if the two sides of the board are to be perfectly registered with one another. On both sides of the board scratch thin lines to mark the positions of the rows of holes to be drilled for the sockets. The first is 0.6" from the front edge, the next is 0.7" from this and the third is 0.7" from the second. A shorter fourth line is required 0.2" from the third line, to show where the connections between tracks on the opposite faces of the board are to be made.

Having marked these points which are especially critical for obtaining good registration, clean the board with Vim or whatever material is recommended for use with the particular etching method you are employing.

1. There is a gap at socket pin 37 for the key.
2. There is a gap in the edge-connector at the third position, for the keyway.
3. The 0V line is a double-width track, since this is likely to carry larger currents than other tracks.
4. The 5V supply to the sockets comes from the regulator, not from the 5V pin at the front of the board.
5. The track from the 5V pin at the front of the board by-passes the sockets.
6. The RFSH (dynamic memory refresh line) and the ROM C/S' (select line for the computer's ROM) also by-pass the sockets.


When the tracks and pads have been laid out, the vacant areas of the board are covered with Sellotape or similar material so as to leave these areas as copper. The board is then etched.

After etching, cut the key-way in the edge connector. Some patience is required in drilling the many holes and in soldering the sockets and terminal pins. Points to note are:

1. If you are not fitting all three sockets to begin with, do not drill the holes for them. Drilling the holes is very likely to cut the track completely, disconnecting the edge-connector. When the socket has been soldered in, the solder bridges the gaps in the tracks. When soldering the sockets, make sure that the near and far sides of all pins are properly soldered to the tracks (Fig. 5).
2. The 0V pin is soldered both above and below the board, to link the ground planes on both sides.

Continued overleaf ►

Top of the Mother Board

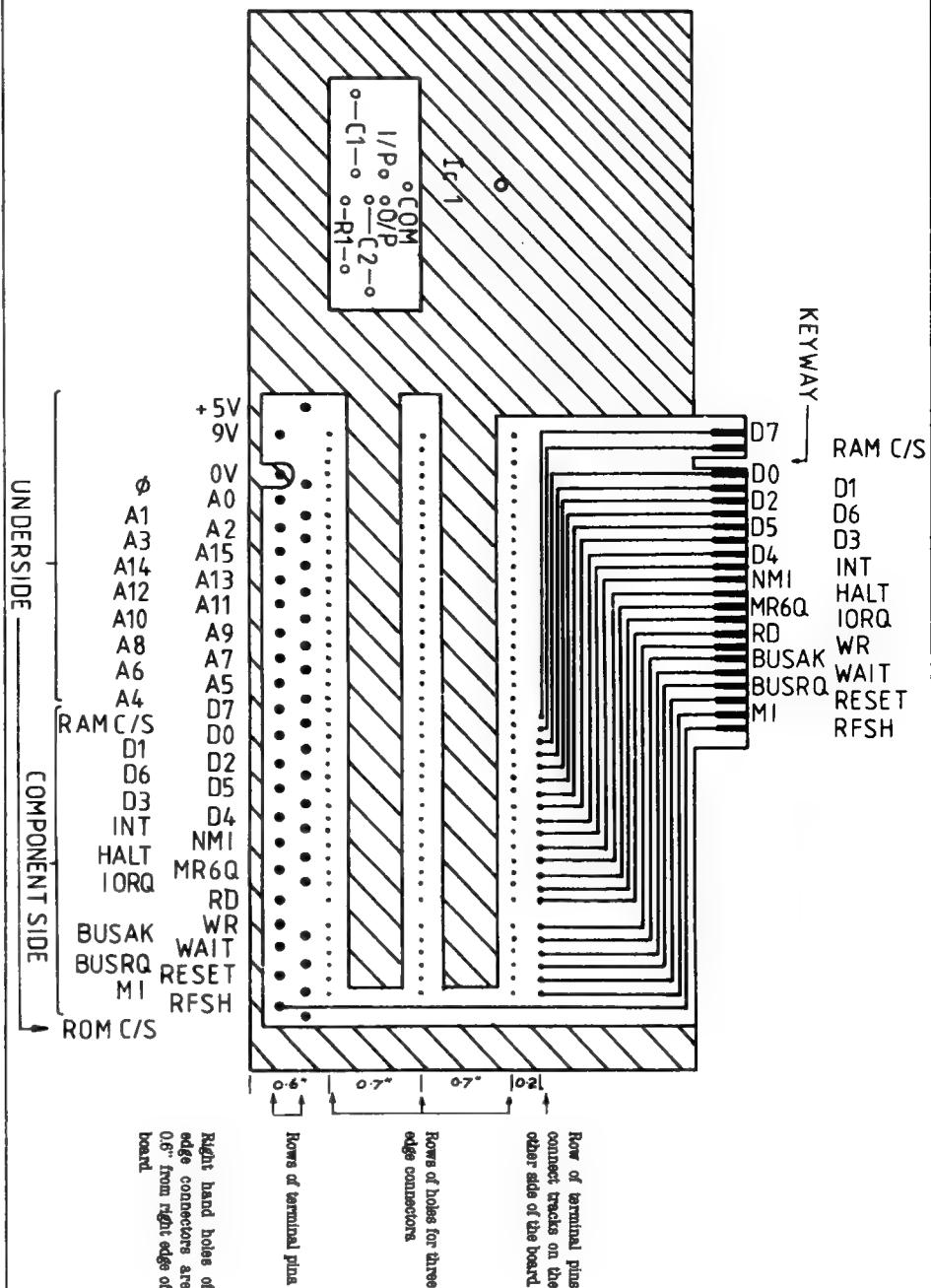

70% of original

ZX81 PROJECT

3. The RFSH pin must be soldered **above** the board, while all other pins are soldered below.
4. The lines to the upper side of the edge connector pass through the board by way of terminal pins, which are soldered both above and below the board.
5. Check all tracks carefully using a hand lens. If any are broken, repair them with soldered bridges.
6. Check that there are no short-circuits between tracks. Use an ohmmeter to confirm that every track is isolated from its immediate neighbours and from the 0V line.
7. When the regulator circuit is complete, check its action using a 9V rectified supply. 5V should appear on pin 1 of every socket and nowhere else. Similarly 9V should appear on pin 2, and at the correct pad of the edge-connector.

CONNECTION TO THE ZX-81

If you made up a cable for last months circuit, you will probably have already removed the single-sided socket to mount on the mother board. Trim the solder-covered ends of the wires neatly and solder them to the pins of the mother board.

If you have not already made a cable, first cut sections from both ends of the 43-way double-sided socket so that its key comes at position 3. The aperture in the rear of the ZX-81 case is only just wide enough to allow a 23-way connector to be inserted. File the cut ends of the socket so that it slips neatly into position onto the edge-connector of the ZX-81.

Remove the socket from the board. After checking which is the upper side, solder a length of 20-way ribbon cable to the pins on the upper side of the socket, from D7' to RESET (Fig. 6). Ribbon cable wires are usually multi-stranded. Twist the strands firmly together and coat with solder before soldering them to the pins. This makes it less likely that stray strands will cause short-circuits between adjacent pins. Solder an equal length of 20-way cable to pins on the lower side of the socket, from ϕ to ROM C/S'. This leaves two spare wires beyond ROM C/S', which are soldered to RFSH and M1 on the upper side at that end of the socket. Use flexible wire of rather heavier gauge (say, 10/0.1) for the 0V, 5V and 9V pins. The other ends of the ribbon cables and the power lines are then soldered to the terminal pins of the mother board.

TESTING


Before attaching the board to the computer thoroughly check all lines for:

1. Short circuits between adjacent lines (including lines on the opposite edge of the 2-way socket), and the power lines.
2. Continuity between the double-sided socket, and the socket(s) and the edge connector of the mother board.

CASING

Whether to house the mother-board in a case or whether to settle for the 'bare-board' look is a matter of personal preference. At the beginning it is certainly more convenient to have free access to the cards for testing them and for wiring external devices to them, so the latter is a more suitable choice. Stick-on plastic feet should be fixed at

Bottom of Mother Board.

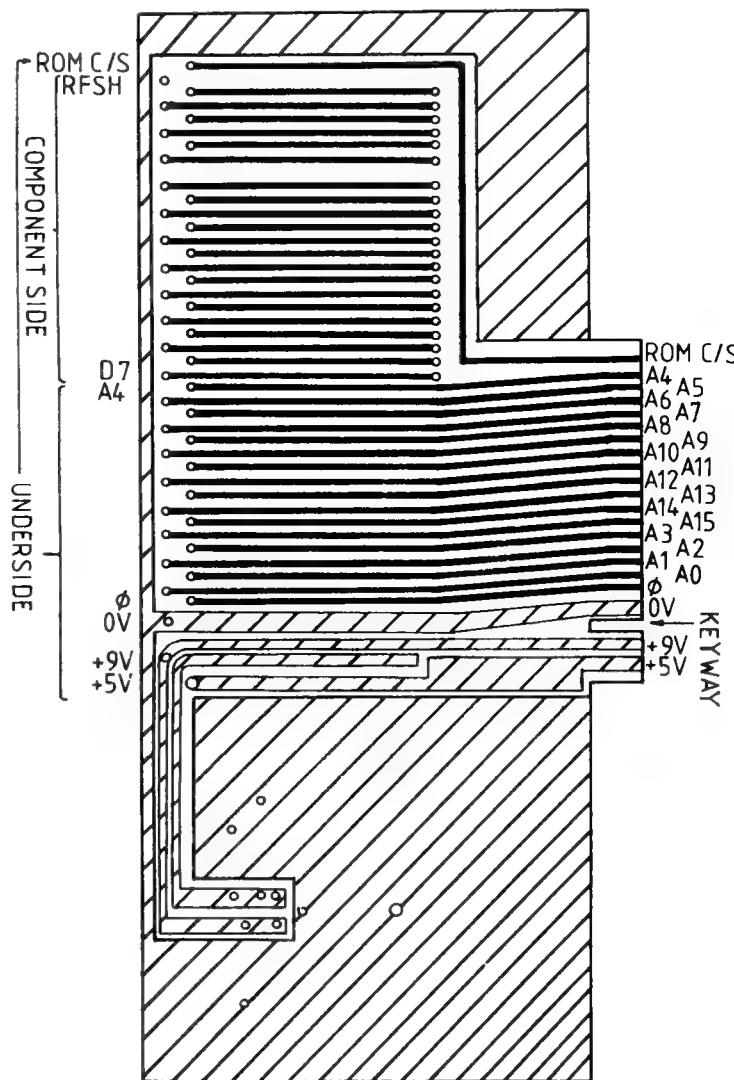

70% of original

Part 2

by Ian Sinclair

USING MENTA

the 4 corners of the board, with a fifth foot in the centre. This is to prevent the board from flexing unduly under the pressure caused by inserting a card in its socket.

The board is now ready for use. Hold the socket carefully as you push it on to the edge-connector of the computer. At this stage it is easy to bend some of the pins at the ends of the socket, so that they contact the pins next to them. Finally insert a card in a socket and switch on the computer. If the 'K' cursor does not appear on the screen, it is almost certain that a short-circuit exists despite all the testing. Switch off, unplug the cable socket from the computer and test again.

Table 1 The ZX PLUS system bus

Line Name	Function
1 SV	Regulated power supply
2 9V	Unregulated power supply
3 OV	System ground
4 OV	System ground
5 φ	System clock (6.5MHz, from the computer)
6 A0	
7 A1	
8 A2	
9 A3	
10 A15	
11 A14	
12 A13	
13 A12	
14 A11	
15 A10	
16 A9	
17 A8	
18 A7	
19 A6	
20 A5	
21 A4	
22 D7'	Data bus, via resistor
23 RAM C/S'	Chip select for the computer's RAM
24 D0'	
25 D1'	
26 D2'	
27 D6'	
28 D5'	
29 D3'	
30 D4'	
31 INT	Maskable interrupt
32 NMI	Non-maskable interrupt
33 HALT	Indicates that the Z80 has stopped action, awaiting an interrupt
34 MREQ	Z80 is ready to read or write to memory
35 IORQ	Z80 is ready to input or output data
36 RD	Z80 is reading (receiving) data
37 —	CONNECTOR KEY HERE
38 WR	Z80 is writing (sending) data
39 BUSAK	Z80 is handing over control of data and control busses to an external device
40 WAIT	Addressed memory or other device is not ready to receive or send data
41 BUSRQ	Requests Z80 to give control of data and control busses to an external device
42 RESET	Resets Z80 and other devices
43 MI	Machine Cycle One; indicates that the Z80 is fetching an instruction from memory

PARTS REQUIRED

R1 . 47kΩ, carbon, 0.25W, 10%

Capacitors

C1 220nF, polyester

C2 470nF, polyester

Integrated circuits

IC1 7805, 5V regulator

Miscellaneous

Double-sided epoxy glass copper-clad board,
203mm x 95mm (8" x 3.75")

43-way single-sided edge connector socket, 0.1" pitch (1 to 3 off, as required)

43-way double-sided edge connector socket,
0.1" pitch (1 off)

Terminal pins, 1mm, single-sided (43 off)

Stick-on plastic feet (5 off)

20-way ribbon cable (about 0.5m)

Connecting wire, solder, materials for etching.

Microprocessor programs are written in "assembler language", using the mnemonic codes for instructions, and with data or addresses written as label names or in hexadecimal code. Any assembler program, such as the excellent ZEN, available for the TRS-80 and the SHARP MZ-80K, will then permit these mnemonics and labels or hex numbers to be typed, one instruction per line, and assembled. Assembly means that the mnemonics are converted into the correct operating codes which will be shown on the screen of the computer as hex codes, but stored in the memory of the computer as binary code.

Computers which do not have an assembler program available have to make do with POKE instructions in BASIC to place the bytes of machine-code into memory. Since POKE instructions in BASIC are normally in denary (scale of ten), this is very tedious, because the hex equivalent of each instruction must be looked up in a list, then converted to denary, and written alongside the memory address at which it has to be poked.

MENTA is a unique Z-80 assembler which contains both hardware and software. It uses a Z-80, with 8255 programmable input/output port, 1K of RAM (static), along with character and display generators. The port connections are taken to a 26-pin plug to which a matching socket can be connected if the MENTA unit is to be interfaced to other circuits. There are also external sockets for a TV receiver aerial lead, a power supply (8V unstabilised), and for connection to and from a cassette recorder.

The unique features of MENTA start with the keyboard. Instead of using a purely hex keyboard, MENTA keys are labelled with Z-80 mnemonics, featuring all but the least-used instructions. By making use of these keys, a program can be keyed into MENTA in assembly language, needing no conversions, and will be viewable on a TV screen in hex. Even the normally awkward business of calculating jump addresses can be done automatically by using the ingenious MENTA operating system.

The program is displayed on the screen of any TV receiver, plugging the TV output lead of MENTA into the aerial socket and tuning to around Channel 35. The display shows the contents of a selectable 256 bytes of memory, starting with the first available address for writing programs. The display is in hex, with the cursor flashing, and the first byte of each instruction highlighted, so that the instruction bytes can be separated from the data bytes. The RAM of MENTA extends from F800 to FBFF (hex), so that each program will start at F800H unless some other address is chosen, and the screen will initially show the range of addresses between F800H and F8FFH. Other "pages", meaning blocks of 256 bytes can be chosen to be shown on the screen, but for our purposes in this series, the first page, page 0, will be used almost exclusively.

The program stored in the RAM of MENTA can be displayed, edited and altered as needed, and then run. A successful program can be recorded on cassette for future use, or if in a development stage, for future editing. The cassette saving and loading system is one of the best ever fitted to any unit of this type.

SWITCH-ON AND HEX DISPLAY

MENTA is connected to its power supply, using the jack connector on the extreme right-hand side at the rear of the unit (keyboard facing you). The TV connection is made to the adjacent phono socket, and MENTA can then be switched on by plugging its transformer directly into a 3-pin socket, and then pressing the RESET key twice. The output to the TV on or around Channel 35 should then be carefully tuned, altering the brightness and contrast controls if necessary, until the page of hex characters sent out by MENTA appears on the screen. A portable TV, such as the Ferguson 3810, will give the best results, colour TV receivers, in general, give poor results.

As usual, switching on gives a set of "garbage", meaningless bytes in the RAM. These can be cleared by pressing the CLEAR key of MENTA twice, with each keypress acknowledged by a short bleep from the built-in loudspeaker. The need to press certain critical keys twice is a safety feature of MENTA — anything that might call for second thoughts before a program is erased or run will require two key presses. The display should now show sixteen rows of hex bytes, sixteen bytes per row, all reset to zero, with a flashing cursor over the first byte at the top left-hand corner. This switch-on procedure results in the display of the first of four pages, page 0, corresponding to the memory addresses in RAM F800H to F8FFH inclusive. The rest of the 1K of MENTA's RAM can be displayed by using the PAGE key followed by the number of the required page (0 to 3) that is wanted. The page number is also displayed on the LED 7-segment display on the right of the keyboard. Though the CLEAR key (pressed twice) resets all of the memory, starting from the cursor position to the end of RAM, to zero, there is always a section of memory at the end of Page 3, from address FBC7H to FBFFH which is used by MENTA's operating system, and which will have bytes present, some changing as they are inspected. These addresses can be used to inspect the contents of registers and to make temporary alterations to the MENTA operating system if required.

THE CURSOR

The cursor is a square flashing block which is located on the screen at a position which corresponds to a memory address. The switch-on procedure will cause the cursor to be located at the HOME position in Page 0, which is the top left hand corner of the page, corresponding to the first available memory address, F800H. When the unit is used, the cursor will move from this HOME position, and it can be returned there by pressing (once) the HOME key. The HOME key does NOT change the Page number, however, so that if the cursor is in the middle of Page 2, then to home it on Page 0 requires the sequence of commands: PAGE 0 followed by HOME.

The cursor is used as a marker, to indicate where bytes are stored in memory, or programs started, and so it is essential to be able to move the cursor freely. The keys marked UP, DOWN, RIGHT and LEFT will move the cursor in the directions indicated, and the

movement will be repeated if these keys are held down, with wraparound. If RIGHT is pressed, for example, and held down, the cursor will travel right to the end of the current line then reappear at the lefthand side of the next line down, still moving to the right. Keeping the LEFT key pressed down will similarly move the cursor to the extreme lefthand side of a line, to reappear on the right hand side of the next line above. Using UP or DOWN in a similar way will cause the page number to change when the cursor reaches the top or the bottom of the screen.

If the STORE key is pressed, it will cause the RAM address corresponding to the cursor position to be stored. Pressing RECALL at some later stage will return the cursor to that stored address position, provided that another position has not been stored in the meantime. This simple position storage system is particularly useful for inserting jump addresses, as will be illustrated in a later Part of this series, dealing with jump instructions.

USING MENTA

At first sight, the MENTA keyboard looks rather complicated, but its operation is remarkably simple and well thought-out. When MENTA is not being used as an assembler, the markings on the keypads themselves are the relevant ones. The complete hexadecimal set, 0 to F, plus all the control functions are therefore available, using one keystroke each apart from CLEAR and RUN which, as already noted, need two keystrokes each.

MENTA can be used as a simple hex programmable machine by pressing the keys corresponding to each byte of a program — since each hex digit takes up half a byte, two digit keys have to be pressed to cause the entry of a byte at the current cursor position, and the cursor then moves to the next position. The program must terminate with FF, which will ensure an orderly return to the operating system. Note that the addresses used will be in the MENTA range of F800H to FBFFH, so that if the program is one containing addresses outside that range (because it was intended for another machine) then these addresses will have to be altered before the program can be run.

A particularly useful facility permits the insertion or deletion of code at any position in memory. If the cursor is positioned over a byte, and INSERT pressed, the byte under the cursor and all the code bytes to its right (unless there is

a gap of several zero bytes) are moved to the right, and the FF byte is inserted in the cursor position. This can be repeated to create as much inserted space as is needed for insertion of extra code, which can then be typed in to replace the FF bytes. Similarly, if the cursor is placed over an unwanted byte and the DELETE key is pressed, then that byte will be deleted, and the bytes following it in memory (right hand side) are moved up to fill the gap. This eliminates one of the objections to early assessment units that an insertion required re-entry of all the code from the insertion position onwards.


Having entered and checked the code — an easy task since most programs will fit on one page and can be inspected at a glance — the program can be run. Before running, however, it is prudent to save the program on cassette.

The recording system is unusual, because only one lead is needed, terminated by a 3.5 mm jack plug at each end. One plug is inserted into the remaining socket of MENTA, and for recording, the other plug is inserted into the MIC socket of a portable cassette recorder. The PLAY and RECORD keys of the recorder are pressed, and then the TRANSMIT key of MENTA. This causes the whole of the 1K of RAM to be saved on tape in a time of about 4 seconds, during which time the screen goes blank. When the display is restored, the recording is complete, and the recorder can be stopped.

Replay is equally simple. The jack-plug at the recorder is moved to the EAR socket of the recorder, from the MIC socket, and the tape is rewound to its start position. The RECEIVE key on MENTA is pressed, and the TV screen will go blank. The PLAY key of the recorder is pressed, and if the volume control setting is correct (try half-way), then a set of dots will appear on the screen when the program is about to load, and will break up into random dot arrays when the program is loading. Return of the normal display indicates once again that the program has loaded successfully. If the display does not reappear, the volume level will have to be increased on replay. The system is quite remarkably tolerant of volume control settings, and using my TROPHY CR100 recorder (Curry's), and setting between $\frac{1}{2}$ and full volume resulted in perfect replay of a program. I wish that makers of more pretentious machines would consult the designer of MENTA, Barry Savage, and learn how a good fast reliable cassette system can be designed!

RUNNING AND CHECKING

A program, once entered and recorded, can be run by replacing the cursor over the first byte of the program, and pressing the RUN key twice. If the program contains a closed loop, accidentally or deliberately, then the INT key can be used to recover control; if this is ineffective, the RESET will have to be used. If, however, the cursor proceeds in an orderly fashion to the last byte, the FF which is used as an end marker, the program has run successfully, and control has passed back to the operating system.

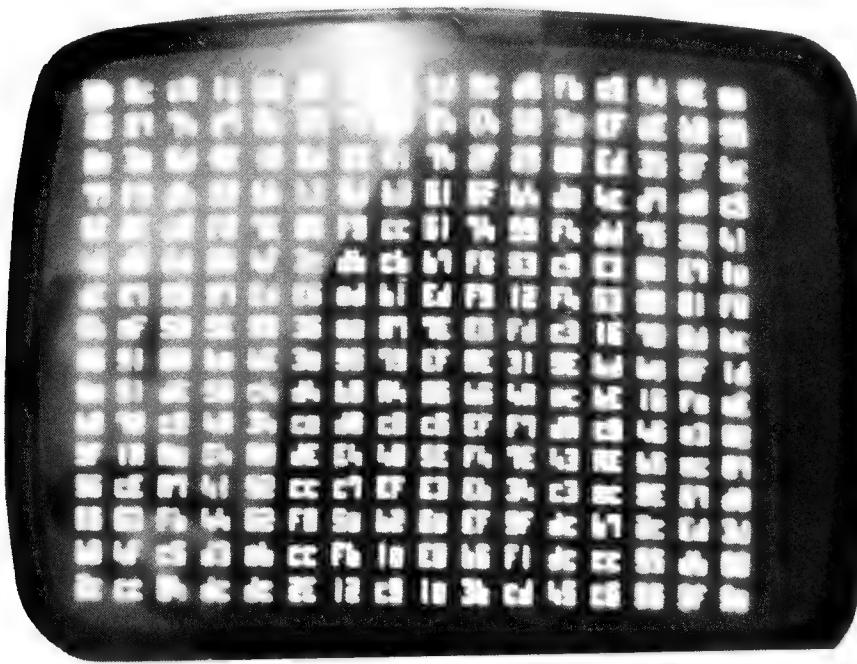

The screen display of MENTA. One complete "page" of data bytes is shown, in hex, on the screen, corresponding to 256 bytes in memory.

The keyboard of MENTA. Though this is of the touch-sensitive type, it is a well-designed one, with a beep from the loudspeaker indicating that a "key" has been correctly struck.

The effects of the program can now be analysed. Any memory address that was used can be inspected — its contents are displayed on the screen. It is particularly handy to arrange short programs on Page 0, with their data held at the end of the page, so that the results can be seen at a glance. In addition the state of the MENTA registers can be inspected by pressing the REG key. This places the cursor over the location in Page 3 where the contents of the status or flag (F)

register are stored. On the right of this byte are the contents, in order, of the A,C,B,E,D,L, and H registers. The arrangement follows the Z-80 convention of writing addresses into memory low byte first, then high byte.

The ability to inspect memory and register contents so easily is even more valuable when single stepping is used. When the cursor is placed at the start of a program, or over the first byte of any instruction (a highlighted byte), then pressing STEP will cause one single instruction to be carried out. This may cause the cursor to jump several bytes on, because an instruction byte may be followed by another instruction, or

ASSEMBLY LANGUAGE

What sets MENTA apart from all other microprocessor assessment units, however, is its ability to use Z-80 assembler mnemonics directly. Since machine-code programs are designed in assembly language, there is no need then to convert to hex codes, and in particular no need to calculate displacement values for relative jumps (see Part 7 for details). These features make the entry of code very much easier than has ever been possible on a unit at this price level before.

Assembly language entry starts with the cursor positioned over the place where the program is to start, the ASMBL key is then pressed, and this causes the top bar of the LED display to light. This is a reminder that the next keystroke will enter the code for one of the instructions shown in mnemonic form above the keys. When the key has been pressed, the LED display will change to light the bottom bar. This is now a reminder that the next byte must be selected from the register or flag references underneath the key positions. Any data (bytes or addresses) can also be entered in this way, looking at the symbols on the keys themselves, and the LED display will light the top bar again when all the data required for an instruction has been entered — this signals the need for a new instruction byte.

The screen does not show the code until the instruction is completely entered with all of its data, and any attempt to enter an impossible combination of instructions, registers or data will result in a protest from the loudspeaker. Once an instruction has been entered, it is shown in its entirety on the screen, with the first byte (the op-code) highlighted. The highlighting feature is extremely useful in tracing the steps of a program through for debugging purposes, but if necessary, the highlights can be removed by pressing the TIDY key, after which only the cursor is highlighted.

The assembler will cope with all but the least used of Z-80 assembly language instructions (mainly the block-shift instructions), which amounts to about 94% of all Z-80 codes being available in assembly language form. These unusual instructions are mainly single byte instruction, and can be entered in hex, so that the lack of assembly facilities is not a disaster.

alternatively be several bytes of data which have to be read in order to complete the instruction. MENTA will carry out all the necessary steps, ending with the cursor over the next instruction byte. After a single step, the contents of registers and memory can be checked to see if the instruction has had the desired effect, making debugging particularly easy. After inspecting registers, pressing RECALL will place the cursor over the next instruction byte.

The assembler use of MENTA is so useful that an example of the use of the keys to enter a piece of simple assembler language is needed. Suppose we wish to enter at the start of Page 0 the assembly language program shown in Fig. 1.

Starting with the cursor at its HOME position on Page 0, press ASMBL. The top bar of the LED display then lights to indicate that a function printed above the keys must be entered, and the one we need is LD. When this has been pressed, the bottom LED bar lights to indicate that we need to choose a function printed under a key, in this case the rA key (under the CLEAR key). The LED bottom bar indicates that more is needed, so that the hex number keys 0 and 6 can be pressed. The data entry terminates when the 6-key is pressed, and the complete code (3E 06) will then appear on the screen. At the same time, the appearance of the top bar of the LED display again indicates that the next instruction can be entered. This is LD again, and the bottom bar of the LED prompts once again for a register, rC this time, followed by rA. This completes this single-byte instruction, and the LD key can be pressed again, prompted by the top bar of the LED, followed by the HL (under DELETE) and the four keys that are needed to enter F8FF. Note that the commas which are used in assembly language (for the computer program to separate the parts of the instruction) are not needed for MENTA. The fourth instruction starts with LD again, but since the contents of register C are to be stored at the address held in the H1 registers, the next keys are the (HL) and the rC keys. The program entry is then terminated by touching the ASMBL key again to return to normal entry, and pressing the F key twice so as to enter FF, the code byte which returns control to the operating system.

In this state, the cursor is located over the next unused position, and the program is marked out by the highlights on the opcodes, the instruction code portions of the program. A more elaborate program would at this stage be checked for mistakes and then recorded, but for the purposes of this simple illustration, all that needs to be done is a quick check — the error detecting system of MENTA will have caught any attempt to enter impossible commands. The cursor can then be returned to the start of the program using LEFT (which will remove highlights) or HOME, depending on the starting position, and RUN pressed (twice). The time needed is negligible, so that only a faint flicker

can be seen on the screen, and the cursor appears over the blank space following the FF command. Looking at the last memory byte on Page 0, however, shows that this has changed to 06 as a result of transferring the contents of the C register to the address held in the HL pair, which is the address of the last byte in Page 0, F8FFH.

Using REG to inspect the register contents will now reveal that the byte 06 is stored in both the A and C registers, as you would expect. Looking further along shows that the HL pair contains F8FF (remember the inverted order) again as expected.

A useful exercise at this stage is to press RESET, which will clear the

the screen display while it is running the program. When a counting loop has to be tested, the most convenient method is to single step round the loop once or twice to check that the loop actions are correct, and then to alter the count to 01. If the count numbers are held in registers (usually BC), press REG, move the cursor along to the register position, and enter the new value from the hex keys. For example, if a count started with BC set to FFFF, the B register could be set to zero, and the C register to 01, than RECALL used to place the cursor back at the program step where it was interrupted. The end of the loop can then be tested without the need to go round 65534 more times!

Figure 1

Code	Assembler	Menta
3E 06	LD A, 06 ASMBL LD rA 06
4F	LD C, A	LD rC rA
21 FF F8	LD HL, F8FF	LD HL F 8 F F
71	LD (HL), C	LD (HL) rC
FF	HALT ASMBL FF

A sample program, showing the hex codes, the assembly language version, and the MENTA keystrokes.

registers and return the cursor to the HOME position on Page 0. Pressing STEP will now cause the first command, coded as 3E 06, to be executed, which loads 06H into the accumulator. To check that this has been done, press REG, which will transfer the display to Page 3 with the cursor over the F-register byte. The next byte on the right of this position is the accumulator content, 06 as expected. You can now return to exactly the correct position in the program by pressing RECALL — this is automatic; there is no need to have used STORE first. This makes it unusually easy to flick between viewing registers and stepping through a program, and is one of the lesser-known advantages of using MENTA. Very few assembler programs, apart from the latest versions of ZEN for TRS-80 and VIDEO GENIE, allow for this quick and easy testing system, which makes MANTA an automatic choice for those of us who write Z-80 code as a matter of routine.

When longer programs, particularly programs which contain a counting loop, are run, the screen will go blank until the program ends, because the single Z-80 microprocessor cannot continue to serve

USING YOUR OWN ASSEMBLER

If you already own a Z-80 based computer along with an assembler program, you should be able to assemble and run the short examples which are contained in this series, but the ease with which you can do so depends very much on the assembler. Not all assemblers, for example, will permit code to be assembled directly into memory and tested there, and very few will allow single-stepping. The methods that you use will depend very much on what is available for your computer. It may be necessary, for example, to use an assembler program to create the code, and then record the code, load in a monitor program, then reload the assembler code so that it can be tested. This is a very clumsy procedure, and if you possess neither assembler nor monitor programs and have a keen interest in interfacing, then it may well be cheaper to buy MENTA than to buy the programs for your existing computer. If your computer uses a 6502 and you, very reasonably, want to learn Z-80 code, then buying MENTA is the only way out of the problem.

ZX 81 OWNERS & 80



NEW

ACCESS THE OUTSIDE WORLD!

EXPAND AND IMPROVE YOUR ZX — PIECE BY PIECE WITH OUR SPECIALISED PRODUCTS

TE10 INPUT/OUTPUT PORT — Easy to use. Fits between ZX & RAM PACK/PRINTER (if required). No skill required to connect. Can be used for such things as:— motor control; sound/music generators, connection to printers/floppy discs/light/pens/other computers, temperature monitoring, square wave generating, control of rotating aerials, even train sets etc. Port has 16 programmable I/O lines and may be used without any electronics knowledge to connect other add-ons. Motherboard required ONLY when two or more add-ons are used at any one time.

FULL ASSEMBLED £17.95

KIT (without case) £14.95

TE12 4 CHANNEL RELAY BOX — To suit Port Contact rating:— 240v AC/1.5A — 24DC or 110v AC/3A. Up to 4 units i.e. 16 relays can be operated — £14.95.

TE15 8 WAY TRANSISTOR DRIVER — £9.95

TE17 8 WAY SWITCH UNIT (EDUCATIONAL) — £12.95

TE18 8 WAY INDICATOR UNIT (EDUCATIONAL) — £12.95

TE20 JOYSTICK & FREE GAME — (2 Joysticks may be connected via Motherboard) — £12.95

TE30 MOTHERBOARD — Allows multiples/combinations of add-ons — up to 16 I/O lines may be used — £15.95

TE126 POWER SUPPLY — 6/7.5/9v DC at 300MA — Required for use with add-ons TE12/15 & 18 — £4.95

23 + 23 WAY ZX Edge Con. — £2.85 Contact Cleaner — £2.30

16 WAY SINGLE SIDED EGE CON. — £1.95

EXTENDED PIO NOTES — £1.00

ALL PRICES INCLUDE VAT

Receipts always provided — Delivery normally ex-stock. ADD 50p towards p&p on all orders under £20.00, with the exception of accessories, e.g. Edge con. Full instructions and examples with all products.

SEND S.A.E. FOR CATALOGUE
POSTAL OR TELEPHONE ORDERS ACCEPTED



THURNALL (ELECTRONICS) ENG.
DEPT. E. 85 LIVERPOOL ROAD,
CADISHEAD, MANCHESTER M30 5BG
TEL: 061-775 4461



AUDIO SOUND
MULTI LED DISPLAY
ZX81 PLUG IN P-I-O TRAINER
WITH PROJECTS FOR:

SOUND FLASHING ARRAY


NIGHT BE THE CAT
GIVE IT A SLEEP

BURGLAR ALARM

G-M-S
ELECTRONICS

KIT £15.95
£00-75 P&P

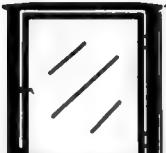PROXIMITY HEAD £1.85
PRESSURE PAD £2.75
SOUND ELEMENT £3.25



plexo
alarm

G-M-S ELECTRONICS.
PART KIT

£ 24.95
£ 02.00 P&P


BUILT £ 59.95
£ 02.50 P&P

: 8 INPUTS
: 8 OUTPUTS WITH
POWER DRIVERS &
INTERNAL POWER
PACK.

16k SYSTEM

UNIT 5,
GRANBOURNE
CLOSE,
HORBDURY SW16 4NG.
TEL: 01-679-5205

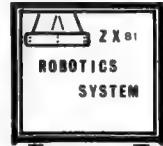THE
ROBOTIC DRIVER FOR YOUR
SINCLAIR WHICH BRINGS THE
WORLD OF PROCESS CONTROL
TO YOUR FINGER TIPS!



Zeta Computers

nascom
authorized stockist

66 high street, stonehouse, glos. gl10 2na

telephone: stonehouse (045 382) 2444

NORTHERN IRELAND

Stockist for
NASCOM — GEMINI — ACORN
Computer Peripherals & Components

NEWBURN ELECTRONICS

58 MANSE ROAD, BALLYCARRY,
COUNTY ANTRIM. Tel: Whitehead 78330

DEAR DESIGNER OF OUR FUTURE,

Computer programmers are already ten-a-penny. The future is for ENGINEERS who can design microprocessor based products. What is stopping YOU designing with micros? If you can claim better than average intelligence and determination the answer should be — nothing! Times have never been better for the man who likes to tinker and find things out for himself. This is based on personal experience. I have designed a dozen micro-based products which are still selling — and I have no higher education or electronics background (I was nearly forty when I learned Ohm's Law).

UNDERSTANDING THE LANGUAGE.

Microtechnology seems a black art to the newcomer, mostly because of the terminology. But nine times out of ten the concepts which go with the unknown terms are already familiar to you or self-evident truths. It's a fact that each step of system design and programming is essentially simple because the micro itself is simple. The micro is a painstaking device which relies on perfect short-term memory and speed to perform complex tasks in easy steps.

GETTING STARTED

There is no secret to starting. What I did was to buy microprocessor and memory chips and find out how to wire them up (No problem. All the pins are labelled, there is only one way to do it) However I do not recommend you to start from scratch because you will come up against the same problem that I did: how do you put the program into memory in a way that lets you see it and edit it? And how do you store it and make it permanent?

AVOIDING WASTED TIME.

This caused me a long detour but I can save YOU the trip because I came back with a solution. At the time I was working there was no cheap development system on the market. The first to appear was the Sinclair MK14, a useful device which got a lot of people started. Development systems have a keyboard and display — and a program in ROM which allows you to enter and edit code. But the trouble with buying a ready made kit is that you are committed to the circuit and the processor. Your imagination is restricted. You are treading the same path as everyone else. I designed SOFTY to solve these problems when building my Chess Player's Visual Recorder (TOLINKA)

A UNIVERSAL DEVELOPMENT SYSTEM.

The funny thing is that I never intended SOFTY to be a commercial product! I built SOFTY because I needed one. I did not realize then that the development tool was the more important product. SOFTY has gained acceptance in industry and education at all levels. Our customer list reads like a Who's Who in Electronics. There is even a SOFTY on display in the Science Museum

TV DISPLAY

SOFTY uses your TV set to display the contents of data memory. This is like having a window into the working memory of the micro. SOFTY has this unique method of converting memory directly into visible hexadecimal code. SOFTY is ROM-emulator for ROMULATOR) which just plugs into the system you're developing where the EPROM goes. You can shift code around without overwriting, do insertions, deletions and hex arithmetic to calculate relative jumps. There are parallel and serial inputs to link up a computer and similar outputs to print the data on a standard printer. SOFTY converts Hex to ASCII and has routines for 110, 300, 600, 1200 and 2400 baud rates. The CASSETTE

RECORDER interface permits code to be stored on tape. SOFTY is an EPROM programmer too. SOFTY1 is an open-board device which programs 3-rail 2708 and 2716 EPROMS. SOFTY2 has a sleek black case and its programs single-rail 2716, 2732 and 2532 EPROMS. For small system development and manufacture SOFTY is the only tool you will need.

Customers often tell me that SOFTY is the most useful tool in the lab — and that SOFTY is underpriced. That must be true because companies are now selling remarkably similar equipment for three times the price. Before buying a copy which is oversized and overpriced do look at a real SOFTY first.

LEARNING MICRO TECHNIQUES

Teachers appointed by the Schools Council to teach microprocessor control as a project (Modular Courses in Technology) looked at all the available hardware. The only thing they liked was SOFTY. The personal computers were out because they gave no INSIGHT. I was invited to a meeting and a specification was written for the ideal device: a product like SOFTY intended to provide insight into the workings of the micro and for experiments in control. I was given an order for a quantity of Micro Electronic Mnemonic Teaching Aids - called MENTAnow

MENTA — AN IDEAL MICRO TUTOR?

MENTA uses the power of the Z80 type microprocessor to make a TV picture mainly by software. MENTA has the advantage of permitting program entry in both HEX and ASSEMBLY LANGUAGE with STEP-BY-STEP EXECUTION which lets you see your program in

MICRODOCTOR — A DIAGNOSTIC AID.

DATAMAN will have another new product soon. MICRODOCTOR is a diagnostic tool for sick microsystems. I see a need for a tester which will look around in addressing space and report what it finds there, check the ROM and RAM, work the peripherals etc.

MICRODOCTOR will save lots of time spent troubleshooting bad systems both on the production line and in the repair shop. The output device is a small PRINTER. You program MICRODOCTOR with a test made of these instructions. CHECKSUM, RAMTEST, HEX DUMP, ASCII DUMP, DISASSEMBLE, WRITE, READ, INPUT, OUTPUT, DELAY. All the instructions have parameters like where to start and where to finish. Each test can have up to eight instructions and you can have up to fifteen tests. Battery backup retains the programs when the power is off. For many purposes MICRODOCTOR is better than a Logic Analyser because it gives an instant printed report and it can be used by a non-technical operator. A FREE Z80 DISASSEMBLER will be included. Disassemblers for other micros will be available at around £35 extra cost. The price will be around £300 but I can't give you a delivery date

OLIVETTI TYPEWRITER INTERFACES

We make interfaces for Olivetti's of the ET121 and ET221 kinds, which permit the machines to be used as printers from standard busses (RS232, IEEE-48, Centronics Parallel). Use of the typewriter with any computer is possible. These interfaces are offered only to dealers who can fit them

PRODUCT	PRICE EX. VAT
SOFTY1	£120
SOFTY1 PSU	£20
SOFTY2	£169
MENTA	£115
ET1211	CALL
ET2211	CALL
MICRODOCTOR	CALL

action. BREAKPOINTS can be inserted and deleted by a single keystroke. The contents of the REGISTERS and the STACK can be seen. There is a CASSETTE RECORDER interface too. MENTA could be called a super-sophisticated development system. There is no other piece of equipment on the market which gives the same INSIGHT that MENTA does.

Menta comes with a fair-sized manual which includes suggestions for use of the 24 available input/output lines to control MACHINERY, ROBOTS etc. Learning with MENTA is not at all boring because you can quickly progress to controlling things. Some fun-and-games like BATTLESHIPS and MUSIC BOX programs are included (which have a serious tutorial purpose I hasten to add). COURSE MATERIAL and plug-in control boards will be available through the SCHOOLS COUNCIL in BROMLEY, Kent.

Quantity prices are available. Dealer and export enquiries are invited

MONEY BACK GUARANTEE.

Don't worry about being disappointed with the goods. You can have your money back promptly if you return the product within 30 days. I am quite happy for you to order the goods for approval in this way rather than ask for literature. I know you don't want to wait — most orders go out Securicor or First-Class Post the same day we get them. My home address and phone number appears on all invoices

ALL PRODUCTS ARE EX-STOCK
at time of writing (except

MICRODOCTOR). Jim Bennett, who manages the business, is available on Dorchester 68066 (STD code is 0305) to answer your enquiries.

Yours sincerely, (Barry Savage).

DATAMAN DESIGNS, LOMBARD HOUSE, CORNWALL ROAD, DORCHESTER, DORSET.

nascom MEANS SOLUTIONS **nascom** MEANS PERFORMANCE

Nascom have come a long way since their acquisition by Lucas. With the knowledge of over 30,000 units already in the field you can buy with confidence from NASCOM.

PRODUCTS:

We have kits, built and tested boards, and our fully assembled and tested NASCOM 3 system with a full choice of configuration either cassette or disc based. Alternative operating systems include NAS DOS and CP/M.



Learn more about
NASCOM now.
Complete the
coupon for further
information and a
full list of dealers

SOFTWARE:

We have a team of programmers who are writing software and courseware especially for UK educational business and domestic users.

FREE ADVICE:

We have appointed experts to advise on the specialist use of micro computers in U.K. schools, homes or businesses.

BACK-UP:

We have a nationwide dealer network giving full sales back-up and after sales service. From our head office we have a service line to sort out any problems.

SYSTEM EXPANSION:

NASCOM machines are designed to grow with users. Easily and simply NASCOM systems can be expanded by adding extra modules to the basic system.

LUCAS LOGIC LIMITED
NASCOM MICROCOMPUTERS DIVISION,
Welton Road, Wedgnock Industrial Estate,
Warwick CV34 5PZ, England.


Have you a
NASCOM programme?
If so send for an
application form for
inclusion in our
programme book

Dealer Enquiries
Welcome

£1,548 + VAT

A typical system as shown
consisting of a Nascom 3 (48K),
dual disks, monitor, and printer is
available from your dealer now.

authorized stockists

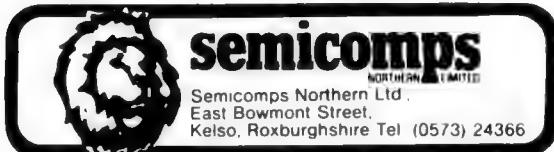

Eley Electronics

Eley Electronics, 100/104 Beatrice Road,
(off Fosse Road North), Leicester. Tel: 0533 871522

MID-SHIRE'S COMPUTER CENTRE

68 Nantwich Road, Crewe, Cheshire
Tel: (0270) 211086

ELECTRICAL ELECTRONIC & MICROCOMPUTING
RETAIL & REPAIR
18 Station Road Lower Parkstone
Poole Dorset BH14 8UB
Tel: Parkstone (0202) 746555



MicroComms

Amateur radio C.B. radio
Electronics Computers
372-374 George Street Aberdeen
Telephone: 0224 633385

JPS

9 East Street, Colne,
Nr. Huntingdon, Cambs.
Tel: Ramsey (0487) 840710
Contact Paul Jephcott



SRS MICROSYSTEMS
161 Bramley Road, Oakwood,
London N14
Telephone: 01-363 8060

58 Battersea Rise,
Clapham Junction
London SW11 1HH
Tel: 01-674 1205
01-675 4557

**OFF
Records**

SKYTRONICS LTD.

2 NORTH ROAD, THE PARK, NOTTINGHAM NG7 1AG
TELEPHONE (0602) 45053



In the heart
of the Nascom
country lies
Business & Leisure

Business & Leisure Micro Computers
We specialise in tailoring systems to your specific requirements.

16 The Square, Kenilworth, CV8 1EB.
Tel: Kenilworth (0926) 512127



Stationstraat,
6241 CL,
Bunde (L),
Netherlands.
Tel: 043 641147

CHRISALID for **nascom**
systems & software
tel 74569
13 High Street BERKHAMSTED

MICRO-PRINT LTD

59 Church Street, Stoke-on-Trent, ST4 1DQ.
Tel: (0782) 48348

OTHER NASCOM PRODUCTS

Kits from £125 + VAT

Built from £285 + VAT

Systems from £399 + VAT

New Products

- ★ **Micro-Ed** — The Education Computer £399 + VAT
- ★ **AVC** — Advanced Video Controller with Colour Graphics and 80x24 Text £155 + VAT
- ★ **M Basic** — A compiled Basic for use under CP/M £150 + VAT
- ★ **Monitor Display** — 12" Green Screen in Cream Metal Case £120 + VAT
- ★ **Monitor Display** — 12" Green Screen in Cream Plastic Case £99 + VAT

To Lucas Logic Ltd., Nascom Microcomputers Division, Welton Road, Wedgnock Industrial Estate, Warwick CV34 5PZ, England

Please send:

Literature Dealer List Prog. Book Form

Name

Position

Establishment

Address

Tel. No.

ELC I

Lucas Logic

When I was first asked to review a machine called the MicroEd, from NASCOM, I imagined that this must be one of the machines designed for the notorious BBC Microcomputer contract, and therefore intended to compete for Government subsidy and Educational Authority support with the "standard" machine which is the RML 380-Z. The present policy of the Dept. of Education & Science is to support two machines, the RML and the BBC MICRO-COMPUTER.

Schools and Colleges which choose these machines have very strong inducements offered in the form of enormous discounts — 50% for first time buyers, which makes even the RML machine seem reasonably-priced — and extensive hardware and software support for establishments which re-equip or extend their computing facilities. Any assessment of the NASCOM contended for this lucrative market must therefore be in comparison with these two models.

We can assume at once that the NASCOM is not competing in the high-price world of the RML-380-Z. The 380-Z is a mainly-RAM machine which has its BASIC or other languages loaded from disc or tape, and its mainstay version is a very pleasant unit with 56K of RAM, and twin double-sided discs running CP/M. This makes up into a very powerful system (or will, when they sort out their network) capable of dealing with tasks which range from elementary BASIC tuition to full-scale data processing in COBOL. The NASCOM simply isn't in this class. This puts it into direct competition with the BBC machine, which is the pace-maker for the machines which are on offer at the moment and for those which will appear over the rest of this year. It's important to remember in this respect that Educational users do not pay VAT, so that the BBC machine costs them just over £200 even with no discounts or subsidies.

A photocopied sheet which was enclosed in the very provisional manual for the MicroEd seemed to declare the intention of the machine — to break away from the old image of NASCOM as a home-constructed spaghetti-special and be regarded seriously by educationalists. As a user of computers for educational purposes (including RML and BBC machines).

I shall judge the NASCOM accordingly. In doing so I have to bear in mind that this is a machine with a long pedigree, a reputation for excellent reliability, lots of good software, and a wide range of add-ons available. It is also supported by what must be the most enthusiastic and dedicated User Group in the country and was at one time the flagship of British-made computers.

First impressions were anything but favourable. The NASCOM is a very large (21" x 17½" x 5¼") and heavy machine by modern standards, housed in a black case which looks like a chunk carved out of a vinyl car roof. The keyboard set in this expanse looks rather list, and though the flat deck would be useful for sitting a video monitor, a cassette recorder and several ZX-81's, it does take up rather a lot of space. Presumably all the expansion can be done within the existing case, as is true of the RML machines, and the case was certainly sturdy enough for school use, something which can't be said for some of its rivals.

The provisional manual was basically that of the NASCOM-2, which appeared to indicate that the MICROED was a NASCOM-2 with a different sticker on the front. The manual was very much aligned to the old NASCOM image, partly dot-matrix printed, part daisywheel, partly typewritten, and partly typeset. It dealt in detail with construction from kit form, with the circuit, with the machine-code monitor, and it also mentioned BASIC. There was an index, but not a very helpful one — there was no entry for MEMORY MAP, for example, and this was typical of the frustration that the user would find in trying to dig information from the manual. The RML manual, incidentally, is worse; and only the BBC manual sets really high standards in manual production, reflecting the educational experience of its author, John Coll. NASCOM would certainly have to pay considerable attention to this point.

Taking the manual at face value indicated that the MICROED was a machine using 8K ROM and 8K RAM, and the screen message on the BASIC carried the 1978 MICROSOFT copyright notice. There are a large number of potential interfacing points on the back of the case, though on the review machine most of these were blanked off, leaving the cassette socket (a DIN-style socket with centre-pin for which I could not find a plug in time to test the cassette

system), a serial-printer connector (now that most schools use the OKI microline with parallel interfaces), a video monitor output, using the BNC socket favoured by the BBC machine, and a UHF modulated output. I hooked in my video monitor and switched on.

First impressions were once again unfavourable. There was nothing to be seen on the monitor, and after pressing ENTER (not RETURN), I saw only SYS-3. This should have been NAS-SYS-3, indicating that the video monitor signal was designed for an under-scanning monitor. I can't change the scan width on my monitor, which functions well on the RML and the BBC machines, and it's unlikely that School or College users would want to try such adjustments. I changed over to the UHF modulated output. This gave better results, though the lines still filled the screen to an uncomfortable extent. Nascom should be aware, however, that the use of TV receivers in Schools is subject to considerable restrictions on safety grounds, and many authorities insist that all school TV receivers should use a double-wound mains transformer and have an earthed chassis. This makes them expensive and rare items, so that the use of cheap video monitors is quite widespread.

BY IAN
SINCLAIR

NAS


Moving on, the next question was — why should it start up in the monitor? There's no reason for the RML doing so, because only the monitor is in the ROM of the RML machine, but there seems no reason for a machine which has BASIC in ROM to start up in monitor — it's just another chore for whoever switches the machines on. The manual suggested that switches or links inside the case could be altered to make the initial switch-on produce BASIC, and this would presumably be already done on production models — you can't expect school users to want to start getting acquainted with a machine by taking the lid off it. In any case, the application of the Health & Safety at Work Act has discouraged experiments, since any subsequent mishap can be pinned on whoever took the lid off, and teachers have enough to worry about as it is. The days when the school computer fell into the hands of a knowledgeable enthusiast are over — computers are increasingly being set up and used by teachers with no previous

experience; that, after all, is what it's all about. The monitor startup looked like a hangover from the "constructor's paradise" days of the old NASCOM, and made me wonder if this was a serious attempt to get into the educational market or just a way of reducing stocks of the NASCOM-2 before a new model could be designed. The whole prospect stands or falls by one simple proposition — if you are Head of a School which by a year's efforts of Fêtes and Jumble Sales has raised about £399, how are you going to spend it? Do you buy a half-

BASIC is well known. Any class learning NASIC will nowadays concentrate on the data processing and problem-solving aspects of the language, and the string handling of MICROSOFT BASIC is good, well known, easy to understand and generally available on other machines. Unfortunately, the cassette filing system of the MICROED is not exactly suited to data processing work. You will look in vain for commands like OPEN and CLOSE, PRINT and INPUT, used in data filing. All you have is a version of CLOAD and

keys have auto-repeat, but the ENTER key (it's not big enough to print RETURN on!) is not sufficiently distinguished by size, shape, colour or position to emphasise its importance to the beginner — it's also very easy to hit in place of the backspace. Though lower case could be obtained by using the SHIFT key along with letter keys, there was no SHIFT LOCK key. The manual advocated the use of the monitor K1 command to achieve shift lock, the alternative being a POKE from BASIC. The appearance of the characters on the screen was good, and the line layout of 48 characters per line and 16 lines per screen was clear, though the characters, oddly enough, looked larger than a 48-character line might suggest. This is a good compromise for UHF modulation, clear without being too large.

NASCOM has now been under new management, after the spectacular crash, for about a year, and if this is all they can come up with in the way of a computer for the fastest-growing market of all, then the year has not been well spent. This is still a computer for the home constructor who doesn't mind paying a lot of money for an unsophisticated machine just to get some experience of construction. There's nothing wrong with that, and a few schools with well-heeled electronics clubs might still be prepared to buy the NASCOM as a super test-bed for accessories. It simply cannot compete on any other grounds, however, either as a home computer, where it's up against the BBC machine, SPECTRUM, VIC, ATOM, ZX-81 and many more on the horizon, nor can it compete as an educational machine for which purpose it simply isn't adequate. The pioneering days are over. Educational users nowadays are not working with machine-code entered in hex (though the superb ZEN assembler is available — a point not even mentioned by NASCOM), they are not interested in taking the machine apart now and again to make minor changes. The main purpose of a computer in a School is to teach the use of a computer to solve problems, and quick and easy use without the mumbo-jumbo of "front-panels" and machine code monitors is essential, along with low prices and plenty of support from the local educational authority. With the greatest of respect for NASCOM, and the many enthusiasts who have had much enjoyment from their machines in the past, this is not a machine which can possibly hope to compete in today's marketplace.

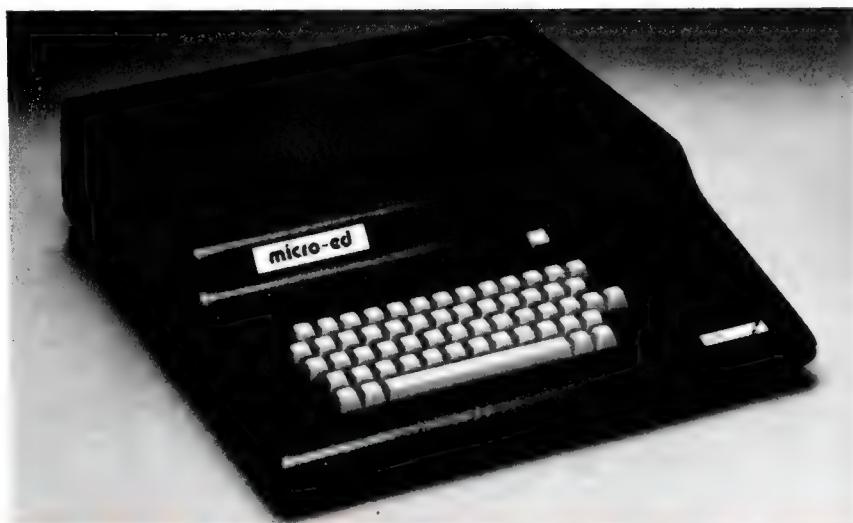

COM "MICROED"

price BBC machine plus a printer and other extras, or a full-price BBC machine (no VAT, remember) and some extras, or on ten ZX-81's (unsupported by the authority but on special offer) or on this machine (with nothing left over for even one cassette). Which gives you the greatest amount of computing now, and the greatest scope for expansion?

Much, of course, depends on the price level at which a computer can be sold. If the price is substantially below that of the BBC MICROCOMPUTER, then there may be a few buyers for an 8K ROM, 8K RAM machine which is capable of considerable expansion and is available now. In 1977, I would have thought the specification of the NASCOM excellent, but times have moved on since then, and the hardware which is on offer here is 1978 style, no U.L.A.'s, no switch-mode power supplies hence the massive size.

The BASIC... well, unless it is a very new design of BASIC there's not much to say. The 1978 MICROSOFT

CSAVE (the program load and dump commands) which can be used to file variables, but NOT string arrays. This is very poor by 1982 standards, and though the manual mentions that the cassette system can operate at several baud rates, trying to find instructions for this is like the proverbial search for the needle in the haystack. This point once again raises serious doubts about the purpose of this machine. An enthusiast who already has a NASCOM can put up with all kinds of patching on inadequate systems, just to keep a solid and reliable machine running — I did the same for my TRS-80. We can't, however, expect to buy a machine which lacks today's fundamental requirements, particularly when the competition has much more advanced specifications at lower prices.

How does the machine shape up to everyday use. On the review machine, the RESET key had become detached, and there was no obvious way of securing it. The keyboard is pleasant to use from the touch point of view, and the

NASCOM USERS

Take a look at the NASCOM APPROVED HS-IN STORAGE SYSTEM. Where else can you get features like these . . .

A full on screen instant display of the catalogue
Auto verification of each file as it is written.
CRC error checking.
Link selectable 2Mhz or 4Mhz option.
Fast data transfer rate of 6000 bps.
Powered from NASBUS.
8" sq NASBUS compatible PCB.
Far more reliable than any floppy disk system.
112K on-line storage with 2 drive system.

The HS-IN has a Command Set which makes it a floppy-disk "look-alike". It can load an 8K program in under 11 seconds and can store up to 56K (28 files) on each side of tape. Why spend £700 on a floppy disk system when the less expensive HS-IN system has a command set like this . . .

OFFER NO1

ALL RAM B boards supplied until April 30th come with an **EXTRA 32K FREE** on board.

OFFER NO2

NASCOM 2 built, 48K RAM B board built, 3A PSU **ONLY £360 + VAT. SAVE £37.50 SEE OFFER 1**

OFFER NO3

NASCOM 2 built, 48K RAM B board built, 3A PSU, HS-IN SINGLE DRIVE SYSTEM **ONLY £530 + VAT. SAVE £66.50 SEE OFFER 1**

ALL OFFERS END APRIL 30TH 1982

BRIDGE THE GAP BETWEEN EXPENSIVE FLOPPY DISK SYSTEMS AND UNRELIABLE CASSETTES.

- B — Write a Basic file
- C — Instant display of catalogue.
- D — Delete file.
- J — Jump to Basic.
- N — Jump to NAS-SYS.
- Q — Warm start to NASPEN text editor
- R — Read a file.
- T — Transfer file to another drive.
- W — Write a file.
- X — Exit and rewind cassettes.
- Z — Warm start to Basic.

Call us for details of the **NASCOM ED**

This Mini-Cassette Storage System is technologically far ahead of anything like it on the market and is extremely reliable into the bargain. **AND THE COST?**

Single Drive System built and tested **£199**

Double Drive System built and tested **£279**

Carriage **£3.50**.

OFFER NO4

NASCOM 2 built, 48K RAM B board built, 3A PSU, HS-IN single drive system, EPSON MX80FT-1, NASPEN & ALL CABLES ONLY £900 + VAT. **SAVE £125.50 SEE OFFER 1**

OFFER NO5

NASCOM 3, 48K RAM B built, Gemini Intelligent Video Card (IVC) **ONLY £540 + VAT. SAVE £65 SEE OFFER 1**

OFFER NO6

SHARP MZ80K WITH SUPER GRAPHICS +5 GAMES, EPSON MX80FT-1 WITH PAPER. **ONLY £825 + VAT. SAVE £229**

MICRO-SPARES JOIN MICROVALUE GROUP

QUALITY MEMORIES

AT PRICES THAT CANNOT BE BEATEN IN THE U.K.. MICRO-SPARES can supply these memories in quantities from 1 to 10,000+. Parts delivery is fast - orders received by 4.30pm are shipped same day.

All memories are guaranteed for 1 year from date of purchase. Memories supplied are good quality but should you have a faulty part a replacement will be sent as soon as the part is received - without question.

Thousands of memories have already been supplied to Manufacturers Computer Traders, Government Bodies and Individuals all over the U.K. and the continent. If you are buying in large quantities please telephone for price. Official orders welcome!

	1-49	50-249
2114L (200ns & 300ns) low power	96p	93p
Suitable for Acorn Atoms		
2114N (200ns & 300ns)	96p	93p
4116 (250ns)	63p	63p
(200ns)	65p	63p
(150ns)	75p	73p
2708 (450ns)	1.40p	1.34p
2716	2.05p	1.92p

MICRO-SPARES have now become the MICROVALUE GROUP member supplying Scotland and now add super new products like the Gemini, Sharp & Epson to the MICRO-SPARES range. SEE MICROVALUE AD IN THIS MAG. On pages 24 & 25

Buy an EPSON PRINTER- Get a COMPUTER



YES - YOU WILL RECEIVE A FREE SINCLAIR ZX81 WITH EVERY ONE OF THE MODELS BELOW. EVEN THOUGH THE PRICE IS GOOD - BUT HURRY - THIS OFFER LASTS AS LONG AS THE ZX81's ARE IN STOCK

EPSON MX80T	£359 + VAT
EPSON MX80FT1	£399 + VAT
EPSON MX80FT2 (new type)	£465 + VAT
EPSON MX100	£575 + VAT

PAYMENT AND DELIVERY

Payment is by Cheque, Postal Order, ACCESS, VISA etc. PLEASE add postage and VAT. Postage on component orders under £30 is 50p. All in stock items sent same day. All none Kit items have a 1 year guarantee. Official orders welcome. Discount on large orders by arrangement.

SUPPLIERS TO TRADE
LOCAL GOVERNMENT
EDUCATION
INDIVIDUALS
INDUSTRY

EDINBURGH



Micro-Spares

19 Roseburn Terrace, Edinburgh EH12 5NG
Tel: 031-337 5611



SCOTLAND

COMPUTERS
PERIPHERALS
COMPONENTS
& NATIONWIDE
MAINTENANCE

SUPERBRAIN

BEST VALUE IN THE U.K.

SUPERBRAIN

(64K · 350K DISKS)

£1,599

SUPERBRAIN 'QD'

(64K · 700K DISKS)


£1,799



MICROLINE 80
80 cps uni-directional
Matrix printer £295

MICROLINE 82A
120 cps
bi-directional logic
seeking Matrix
printer £399

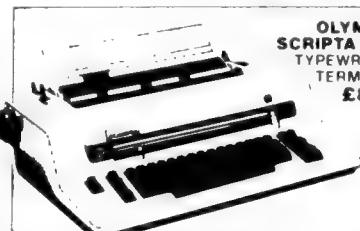MICROLINE 83A
120 cps bi-directional
logic seeking
Matrix printer £690



OLYMPIA
SCRIPTA KSR
TYPEWRITER
TERMINAL
£850



RICOH 1600S
Highspeed daisy
wheel printer
Special interfaces
available £1450

ALL EQUIPMENT CARRIES A 90 DAY WARRANTY - MAINTENANCE AVAILABLE

SOFTWARE

WORDSTAR
MAILMERGE
DATASTAR
T MAKER
DATAFLOW

£225
£70
£155
£150
£99

PAYROLL
INVOICING AND STOCK
CONTROL
SALES LEDGER
PURCHASE LEDGER
NOMINAL LEDGER

£250
£245
£225
£225
£265

VERBATIM DISKETTES
LISTING PAPER
PRINTER RIBBONS
COMPUTER LABELS

**DISCOUNT
PRICES**

(ALL PRICES EXCLUDE VAT)

051-263 5783 - 5738

BUSINESS EQUIPMENT CENTRE, 35 EDGE LANE, LIVERPOOL L7 2PA

TALK TO
BEC

DEALER AND
QUANTITY ORDER
ENQUIRIES
WELCOME



PROFESSIONAL GRADE KEYBOARD AND CASE AT UNBEATABLE PRICES

- ★ Our case takes the ZX81 printed board.
- ★ Keyboard supplied fitted to case
- ★ Your RAM Pack plugs into rear of case
- ★ Assembled keyboard and case price £36.00
- ★ Keyboard complete with ribbon cable & connectors
- ★ No soldering required
- ★ Large keys are used with changeable keymarkers
- ★ Keyboard Ready Assembled price £24.00

SINCLAIR MAKES THE BEST HOME COMPUTERS AND WE MAKE THE BEST KEYBOARDS

Full money back guarantee if you are not fully satisfied.
Prices include VAT

MAIL ORDER ADDRESS:

GORDON ELECTRONICS 76 Mountbatten Road,
Braintree, Essex, CM7 6TP Telephone: (0376) 26048
Please add £1.50 P&P. Make cheques payable to: GORDON ELECTRONICS

V. GENIE UPGRADES

Internal memory upgrade 16-32K, £44.95 (kit)
Ditto: 32K-48K (factory fitted only) £49.95+ £12.00 carr.

Lowcase conv. £28.00 TAB/CLEAR Keys £3.45

New ROM with keyboard debounce and personalised power up message (15 chars max), supports lowercase (with our L/C upgrade kit), 1 ROM £8.95

Any kit fitted for £7.50 plus £12.00 carriage.
AY3-8910 sound generator on PCB with demo tape - just plugs in to expansion con. £49.95

Eight input A/D converter to add on to sound generator board £23.00

Eproms, 2708 £2.95, 2716 £3.47, 2532 £5.25 (All single rail)

Eeprom blowing service ring for details. Erasing 50p/chip
C15 cassettes 65p each + 10p each carr.

We can supply most hardware at competitive prices e.g.:

V. Genie printer interface with cable £39.95

Microline 80 £335.00 Microline 82A £435.00

Epson MX80FT £435.00 Epson MX82T £430.00

V. Genie Disk drives £5.25 inch boxed with PSU and all cables, examples:

Twin 40 track £508.00 Twin 80 track £654.95

Ring for a quote on your requirements.

Repair service for Genie, TRS80, Superboard & VIC 20

ALL PRICES INCLUDE VAT, AND P&P ON ORDERS
OVER £10.00 Otherwise add 75p towards cost.

*Ring your order through on Barclaycard
for immediate despatch.*

ARC Electronics

54 Heron Drive, Sandal, Wakefield, W. Yorks.
Telephone: Wakefield (0924) 253145

If you are interested in getting your B.B.C. microcomputer to control things, for example a model railway or a model racing car circuit then this and successive articles should be of help to you. However I'm going to start right from scratch so that even if you have never done any interfacing before, you should at least be able to get started once you've absorbed this article. What I will be assuming though is that you have some knowledge of binary and hexadecimal. If you haven't, then pop along to your local library and find a book which explains it. (Any suggestions, Ed?). You cannot get far with digital interfacing unless you understand the number system used by the computer, i.e. binary, and since binary is so cumbersome — all those 1's and 0's — we use hexadecimal (base 16) which is simply looking at four bits at a time, 2 to the power 4 being equal to 16. So to specify an 8 bit byte requires just two hexadecimal numbers.

What I shall do is to look at the whole idea of memory-mapped input/output which may well be a new idea even to those who have done some interfacing on Z80 based machines. Then I shall give a little bit of explanation about the 6522 versatile interface adapter which, to explain it fully would need a complete series all to itself, and then finally I shall give you a few circuits so that you can get started with a few simple experiments yourself, then as the series goes on I'll go into more detail so that you can go on to more advanced projects.

MEMORY-MAPPED INPUT/OUTPUT

In most microcomputers the information is stored in the form of 8 bit binary numbers, each of which is stored at a specific numbered location. This number is known as the address. At some of these addresses the information is stored in permanent form i.e. it cannot be changed. This is what is called read-only-memory (r.o.m.). Other information needs to continually up-dated and moved around and therefore has to be stored in read/write or random access memory (r.a.m.).

SIMPLE DIGITAL INPUT-OUTPUT

by Paul Beverley, Norwich City College.

Within a r.a.m. chip are effectively vast arrays of transistors, the state of each transistor, on or off, representing one bit of one of the binary numbers stored in it. In memory-mapped input/output, what we do is to have a circuit which, as far as the computer is concerned, acts like ordinary r.a.m., but in fact, each of the transistors which represents one bit of memory has got a circuit attached to it so that its state can be looked at electrically from outside the computer, or so that its state can actually be changed by some external logic level. But unlike r.a.m., these memory locations can only either be written to or read from, but not both at the same time. Thus we talk about input and output ports. i.e. windows through which the computer can talk to the outside world and vice versa.

An output port then is a set of eight lines coming out from the computer, and each line will either be at logic 0 (0 volts) or logic 1 (+ 5 volts) depending on what number has been written to it by the computer. Each of these lines could then be used to switch on or off some electrical circuit such as a light or an electrical heater, or to operate some mechanical device such as a flow valve. Alternatively you could feed all eight lines into a device called a digit to analogue converter which would give you a single voltage out which was proportional to the binary number stored at the port.

As far as input ports are concerned what we have is eight lines which can be used to sense the states, logic 0 or 1, of each of eight different circuits. So when the computer reads the input port, the number it gets is made up of the individual on/off states of each of the lines, and it would then have to be programmed to interpret the number in terms of events in the circuits to which it was attached.

Just as the output port can be used to produce a single voltage, so the input port, if used with an analogue to digital converter, can be used to read the value of a voltage in an external circuit. The

B.B.C. microcomputer actually has four of these circuits each of which uses 12 bits rather than 8 giving greater accuracy, and I dealt with how to use these from within BASIC in my article last month.

THE 6522 V.I.A.

The B.B.C. microcomputer has many different types of port — too many to deal with here, but the one I will look at is the 6522 versatile interface adaptor. This has sixteen 8 bit registers in it which

Address	Register
FE60	PB port - User port
FE61	PA port - Printer port
FE62	DDRB - Data direction register B
FE63	DDRA - Data direction register A

Figure 1 — Four of the registers of the 6522 v.i.a.

can perform various functions, and their addresses are &FE60 to &FE6F. Of these, only two are actually ports which can be connected to the outside world, but the other registers can affect what happens at these ports in various ways. Also, both these ports are "bit-programmable", in other words each line can be individually programmed to be either an input or an output. The 6522 itself therefore can be used to provide 16 output lines or 16 input lines or any other combination in between. However on the B.B.C. machine, one of the ports has been provided with a buffer in order to make it suitable to drive a parallel printer and so those eight lines can only be used as outputs. So if you need more than eight inputs you will have to use one of the other ports. For example, there are two spare digital inputs on the connector for the paddles.

Interfacing the BBC Micro

DATA DIRECTION REGISTERS

In order to set each bit of each of the two ports as either input or output, there are two registers called data direction registers, DDRA and DDRB. Each bit of these two registers corresponds to a bit in port A or port B, and each bit acts like a toggle switch. If the bit is set (logic 1) then the corresponding bit in the port is set as an output, and if it is reset (logic

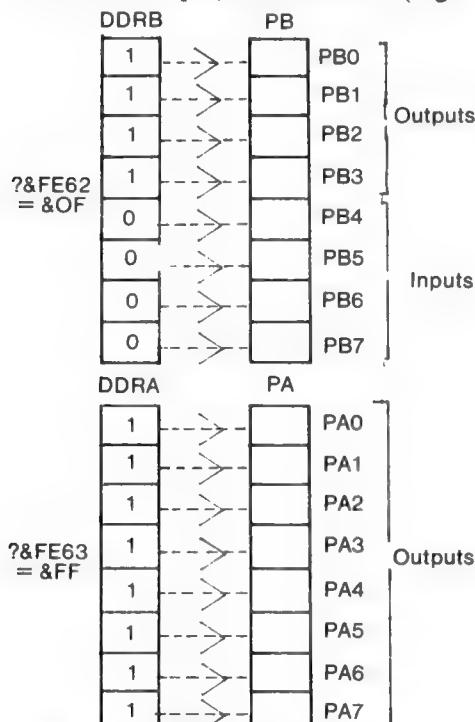


Figure 2 - An example of the use of the data direction registers

0) then the corresponding bit is an input. In the example given in figure 3, all of PA is being used for output, as of course in this machine it has to be, and this is done by putting 255 (&FF or binary 11111111) into DDRA. That is, all the bits of DDRA are set to 1, and this can be done from BASIC by saying

?&FE63=&FF

The “?” is the “byte indirection” familiar to Atom users and is equivalent to the more common POKE. i.e. POKE &FE63, &FF.

PB on the other hand is split into two halves — four input lines and four output. For this, DDRB has to be loaded with 15 (00001111 in binary) so that the four 0's correspond to the four upper bits being inputs and the four 1's, the four lower bits being outputs.

OUTPUT CIRCUITS

When you are using the computer to switch things on and off, you have to be aware of the amount of current which each output device in the computer is capable of providing. It is also worth noting that the amount of current is different depending on whether you are trying to “source” or “sink” current. i.e. it depends, as can be seen from figure 4, on whether the load through which the current is to be passed is connected to OV or +5V. Connecting it to OV is perhaps the more obvious way of doing it so that when the output is logic 0, no current flows, but when it is logic 1, current flows out of the port and down

into the port — hence the term “sinking”. Admittedly it is a little bit confusing that although the port is an OUTPUT, never-the-less current flows INTO the computer, but the computer IS still acting as an output because it is controlling whether or not the current should flow.

As you can see from figure 4, both the ports have a greater capability for sinking current than for sourcing it. Indeed it is quite possible to drive L.E.D.'s directly from the PA port as shown in figure 5. However this means that the L.E.D. will be ON when the output is logic 0 which might be a little confusing. But if you use a transistor as shown in figure 5 then it works more as you might expect, that the L.E.D. is ON for logic 1 and OFF for logic 0. The circuit shown can be used on either of the ports, provided that the transistor has a gain of at least 50 which is well within the capabilities of most general purpose NPN silicon transistors e.g. BC182, BC108, ZTX300 etc.

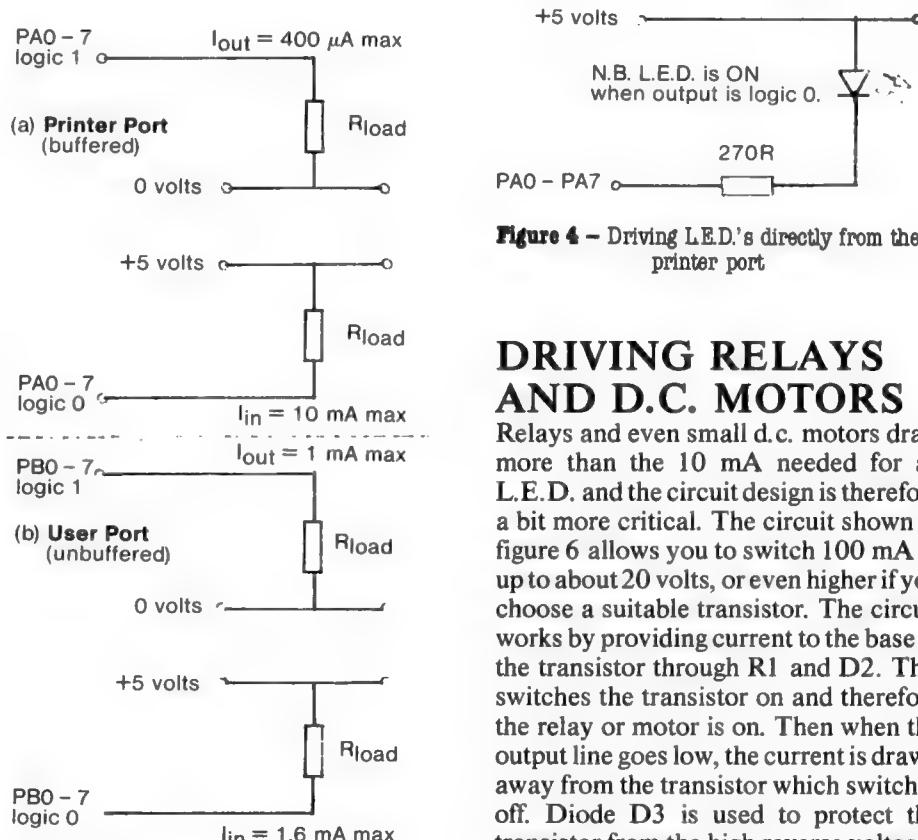


Figure 3 - Current capabilities of the printer and user ports

through the load resistor. That is, the port is acting as a source of current. If you connect to +5V however then when the output is logic 1, no current flows, but when it goes to logic 0 then current will flow down through the resistor and

DRIVING RELAYS AND D.C. MOTORS

Relays and even small d.c. motors draw more than the 10 mA needed for an L.E.D. and the circuit design is therefore a bit more critical. The circuit shown in figure 6 allows you to switch 100 mA at up to about 20 volts, or even higher if you choose a suitable transistor. The circuit works by providing current to the base of the transistor through R1 and D2. This switches the transistor on and therefore the relay or motor is on. Then when the output line goes low, the current is drawn away from the transistor which switches off. Diode D3 is used to protect the transistor from the high reverse voltages which are generated when the current through the coil is switched off suddenly.

In order to switch even higher currents you will need to use two transistors in the so-called darlington pair configuration as shown in figure 7. This circuit should cope with more like 1 amp at up to about 60 volts, again depending on the transistors used.

But as a general rule it is worthwhile allowing for more current than you think you need, simply because if you cut it a bit fine, you may find your transistors getting rather hot. The point about using transistors as switches is this. When they are switched off then no current flows, so no power is dissipated. Then when it is fully switched on, the voltage drop across it is very small so the power dissipated is also small. But if you do not provide enough base current, then the transistor may not be fully switched on, in which case there may be an appreciable voltage drop across it which, with the current that is flowing, may represent an appreciable amount of power dissipation.

As far as motors are concerned, the only thing you have to beware of is that when they are stalled they tend to draw rather large currents, so you have to be sure that your circuit is capable of handling that maximum current.

USING THE PORTS AS INPUTS

The most important thing to be sure of when using the ports as inputs is that you have actually programmed them into the input mode. If you have programmed them as outputs and then try to use them as inputs you may well blow them up. Also, as I have said, PA has output buffer circuits on it and can therefore not be used as inputs at all. It is worth noting at this point that when you first switch the machine on, or press the BREAK key, PA is automatically set in the output mode, and PB in the input mode.

Simple inputs can be provided by using mechanical switches or reed switches which can be operated by bringing magnets near them. The switch can be connected directly between the input port and 0 volts so that when it is pressed the computer registers a logic 0. Unfortunately you can't get it to work the other way round by connecting between the port and +5 volts since inside the input port is a resistor pulling it up to +5V so that if left unconnected it registers logic 1.

READING AN INPUT PORT

In order to read an input port, you can again use byte indirection, though this time it appears on the other side of the assignment, viz:-

value + ?&FE60

This is equivalent to "value = PEEK(&FE60).

But what if you want to look at one particular line and are not interested in,

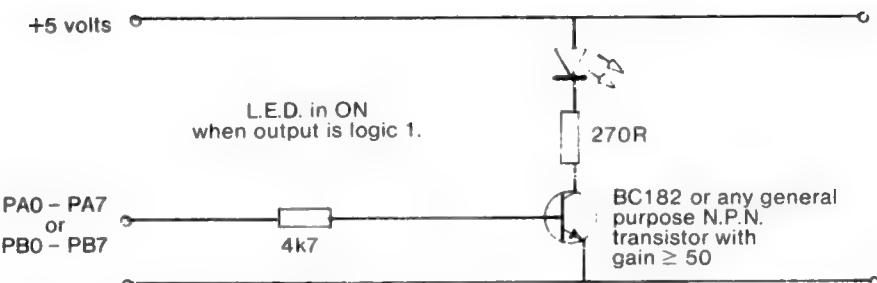


Figure 5 – Using a transistor to switch an LED.

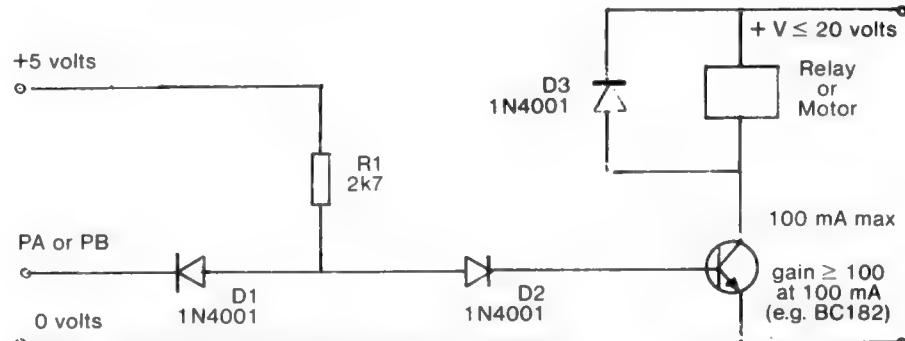


Figure 6 – Single transistor relay or motor driving circuit

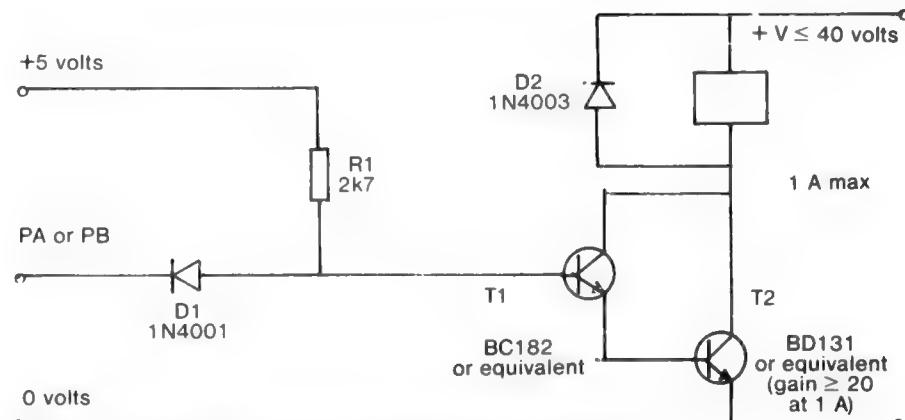


Figure 7 – Darlington pair circuit for higher current switching

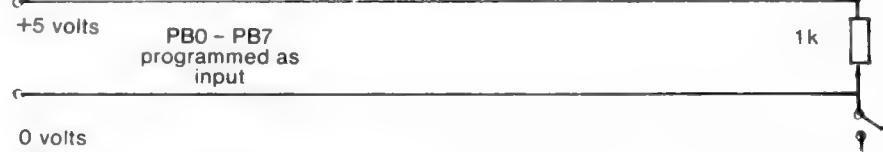


Figure 8 – Simple switch input to user port

or don't know the value of the other lines? For this we can use the logical operator, AND. For example, to check on the state of PB3, we could say:-

```
IF(?&FE60 AND 8) = 8 THEN
    PRINT "ON" ELSE PRINT
    "OFF"
```

or, to wait for PB1 to go to logic 0 we could say:-

```
REPEAT
    UNTIL ?&FE60 AND 2 = 0
```

APPLICATIONS

I hope you now feel that you could go away and start connecting up to say a model railway or model car racing set. You have enough information to be able to switch motors on and off and also to look at reed switches or mechanical switches to sense the presence of a car or a train. We haven't thought about how to actually control the speed of a motor yet, only how to switch it on and off, but first things first!

SHARP MZ-80K/MZ-80A /MZ-80B

Functional cassette software by Dale Hubbard

Buy 2 at £19.95 - take 1 at £5.95 FREE!!!

All programs in Standard Sharp Basic for 48k RAM upwards.

All programs supplied with exhaustive and attractively bound documentation.

DATABASE

The program that everyone needs. Facilities include sort, search, list, delete, change, totals, save file, line print if required, etc. etc. Can be used in place of any card index application.

£19.95

STOCK CONTROL

All the necessary for keeping a control of stock. Routines include stock set up, user reference no., minimum stock level, financial summary, line print records, quick stock summary, add stock, delete/change record, and more.

£19.95

MAILING LIST

A superb dedicated database to allow for manipulation of names & addresses & other data, with selective printing to line printer. Features include the facility to find a name or detail when only part of that detail is known. Will print labels in a variety of user-specified formats.

£19.95

DECISION MAKER

A serious program that enables the computer to make a sound decision for you based on various criteria. If you want to buy a car, hi-fi, house, etc., or you don't know which woman to marry then you need this one.

£5.95

INVOICES AND STATEMENTS

Ideal for the small business. A complete suite of programs together with generated customer file for producing crisp and efficient business invoices and monthly statements on your line printer. All calculations including VAT automatic and provision for your own messages on the form produced.

£19.95

RUBIK SOLVER

It's not our policy to offer games but we make an exception here for a program to solve the cube from ANY position. Shorthand notation makes learning the solution by heart possible for most active brains.

£12.95

THE CATALOGUER

This dedicated database is ideal for use in any situation where a catalogue could be utilised. E.g. stamp collection, coins, photos, slides, books, records etc.

£19.95

COMMERCIAL ACCOUNTS

A gem of a program, all for cassette, with the following features:-

Daily Journal
Credit Sales
Cash Sales
Credit Purchases
Purchases - other

Sales Ledger
Purchase Ledger
Bank Account
Year to Date Summary

A fully interactive program suitable for all businesses. Files can be saved and loaded and totals from one file carried forward to another on cassette. Particularly useful from a cash flow point of view, with an immediate accessibility to totals for debtors and creditors. Bank totally supported with entries for cheque numbers, credits and, of course, running balance.

£19.95

HOME ACCOUNTS

£19.95

Runs a complete home finance package for you with every facility necessary for keeping a track of regular and other expenses, bank account, mortgage, H.P. etc etc etc!! You'll wonder how you ever managed without it.

CHOPIN - LES ETUDES

£19.95

Six beautiful studies from Opus 10 and 25 performed for you live by Mr. Sharp - Spellbinding!!!

£5.95

MOTOR ACCOUNTANT

£19.95

Find out exactly what that car is costing you and keep a data file with all your expenses therein!

£5.95

RECIPE FILE

Let all those computer widows have a bash! The wives will really enjoy the fun of this program designed to keep all her recipes. Will even suggest a menu for a day/ week! Excellent value.

£19.95



Access Welcome

Send cheque or P.O. or Cash (registered) or Credit Card no. to:

Gemini Marketing Ltd

Dept PCW(3) Quay House Quay Road | Newton Abbot Devon TQ12 2BU
Or telephone us with your credit card order on (0626) 62869

All orders despatched by return - no waiting.

All prices include VAT and post & packing except Hardware. Full range of Sharp peripherals available - please 'phone for quotations.

Please state machine type (A.K. or B) when ordering software.

ECMZ

HARDWARE OFFER!
MAIL ORDER ONLY
MZ-80A PLUS ANY 3
PROGRAMS
£477 + VAT
LIMITED STOCKS -
HURRY!!!

COMMENT

A question I am frequently asked is, "Which segment of the electronics and computing market does our magazine appeal to?" By arranging readers into neat categories, media analysts hope to be able to divide markets into segments. This quite normal practise works fine when dealing with traditional industries such as mechanical and electrical engineering. It is not usual to find a mechanical workshop technician or machine operator with a full-blown lathe or milling machine in his back kitchen.

In the case of a computer service or electronics technician, we are not surprised to learn that after leaving his computer system at work he returns home to a lavish and possibly better computer in his own lounge. A recent example which illustrates this point arose from a telephone conversation I had recently with an E&CM reader, who phoned from his office to discuss a product review. The item we discussed would clearly be defined as "business use" however, the link between the professional and private interest of this reader were inseparable. He went on to tell me how at home he has a dustbin lid covered with silver paper on his garage roof which forms part of a satellite base station.

Since I know from our survey that this particular gentleman is by no means untypical of E&CM readers you can imagine the headaches we have trying to explain our reader profile to professional media agencies.

In an effort to try to put computer users into slots, computer manufacturers are now placing different emphasis on the words 'personal' and 'home' computer. When Sharp first introduced their MZ80B Personal Computer, I thought they were mad restricting its use by the title to personal computer users, when the specification clearly made it suitable for professional users. It soon became obvious however, that Sharp were aiming at the managers, engineers and decision makers who could

justify a personal computer on their desks.

The distinction then, between different levels of micros would appear to be 'home computers' which fall into the price bank of up to say £500. Followed by 'Personal Computers' which normally cost between £500 and £3000 and finally 'Business Computer Systems' which carry a price tag anywhere between £3000 and £20,000 depending on the software requirements.

Survey 82

During the past month I've been wading through the surveys kindly completed by readers and they reveal some surprising results. In particular was the amount of cash many of our readers earn which has prompted a memo from me to our Chairman asking for a 300% pay increase to bring me into line with the lowest paid readers. "I didn't know we were paying you anything". Chairman. According to your figures and a slight bit of extrapolation E & CM readers will be spending a massive 14½ million pounds on electronics and computing equipment during the next twelve months. In addition 34% of you influence capital equipment purchasing and 20% have a budget to spend at work. An estimated 37% of our readers plan to buy another computer shortly and 62% use computers at work.

One of the less predictable areas of the survey was readers alternative interests to electronics and computing. I won't dwell on this since its a personal matter and what people do in their spare time is their own business. If I tell you in some confidence however, gardening, sex, home brewing and amateur radio are in some way linked in the minds of some of our readers then perhaps you will know what to make of it.

My conclusion to date is that we are reaching probably the most influential, technical sector of the electronics and computing market and with the information you have provided I hope we can now plot a course for an editorial balance which continues to meet the requirements of a great many electronics and computing enthusiasts.

NEXT MONTH

In Britain's first electronics & computer applications magazine

Introducing CP/M

The role of a computer operating system is outlined in this special feature by Dr. Philip Barker. A complete overview of the CP/M operating system for 8-bit microcomputers is then given and the use of this operating system on a PET via a SOFTBOX is described.

Extra Memory for the ZX80/81

This project describes how the 80/81 can be easily expanded beyond the addition of a 16K RAM pack.

Atomic Frequency Meter Project

Turn your Atom into a frequency meter with a range of 10Hz to 400KHz and an accuracy of better than 0.03%.

Other regular features include Ann Houghton's software reviews — ZX81 KIDS CORNER — ZX80 Addressing Methods by Ian Sinclair. Plus lots of software — readers letters and ideas on how to get the best from your computer.

All in BRITAIN'S FIRST and BEST electronics and computer applications magazine AUGUST issue on sale at all leading newsagents from 9th JULY.

JOSEPH SPENCER & PARTNERS LTD + SHARP

NEW



48K

MZ-
80A

CASH PRICE

£ 475

PLUS VAT

YOURS FOR ONLY 24 PAYMENTS OF

£ 28 - 95
PER
MONTH


MZ-
80B

CASH PRICE

£ 1095

PLUS VAT

RAVE
REVIEWS

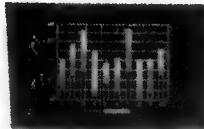

64K

YOURS FOR ONLY 24 PAYMENTS OF

£ 66 - 75
PER
MONTH

MZ-80SFD SINGLE DISC DRIVE FOR 'A' OR 'B'



INCLUDES:
★ EXPANSION UNIT
★ MASTER DISKETTE
★ OPERATIONS MANUAL

24 PAYMENTS OF

£ 38 - 50

CASH PRICE
£630+VAT

MZ-80P6 PRINTER FOR EITHER 'A' OR 'B'

24 PAYMENTS OF

£ 33 - 50

CASH PRICE
£550+VAT



WITH:
★ FRICTION & TRACTOR FEED
★ FULL GRAPHICS + 80 CPS
★ BIDIRECTIONAL & LOGIC SEEKING

HOW TO ORDER

Cash Customers

Tick box/boxes for goods required.
Enter name and address. Send with cheque.
Allow 28 days for delivery.

Credit Customers

Order as for cash customers. Send cheque for 1st monthly payment as deposit. We send you simple Musters Finance loan form. You complete and return it, we despatch.

Other Sharp Kit

If you want dual disks, P4 or P5 printer, machine languages etc., phone Nottm. 607395 for cash prices and monthly payment terms.

Mail Order Form

GOODS REQUIRED	TICK HERE	CASH PRICE	24 MONTH CREDIT CHARGE	TOTAL CREDIT PRICE
MZ-80A	<input type="checkbox"/>	£546.25	£148.55	£649.80
MZ-80B	<input type="checkbox"/>	£1259.25	£342.75	£1602.00
MZ-80SFD	<input type="checkbox"/>	£724.50	£199.50	£924.00
MZ-80P6	<input type="checkbox"/>	£632.50	£171.50	£804.00

MAX A.P.R. 30.5%

Name Tel (day)

Address

MAIL TO: JSP COMPUTERS, 18 HAMILTON RD., NOTTINGHAM

**AMERICAN
SOFTWARE
FOR YOUR
VIC**

Great VIC Software
New Programs for your VIC Computer
On Cassette
COLOUR & SOUND

**All prices
include VAT
at 15% and
P. & P.**

Lunar Lander
Wrap
Breakout
Blackjack
Pong
Slots
Alien Raiders
Bombs Away

**£10.25
EACH**

Adventure
Head On
Target
Hang In
Chase

**ANY 3
FOR
£28.50**

Home Finance
Math Drill
Hangman
Yahtze
Othello
Target Moon
Shooting Gallery
Capture

Cattle Roundup
Artillery Shoot
Micro Maze
Snake Out
Trapper

EGG ATTACK

This seemingly innocent electronic game of catch turns gradually into a harried race of joystick control. The player must manoeuvre a nuclear reactor in order to catch radioactive eggs as they are dropped from advancing "monsters". If the player misses three eggs, the Earth is no longer habitable and their turn to play is over — **£12.95**

TUNNEL PATROL

The player is required in this arcade game to manoeuvre an android through a maze in order to harvest "Energy Crystals" and score points. As an obstacle the program randomly throws the android into the fourth dimension where it must battle the dreaded "Batwing" in order to survive — **£12.95**

JOYSTICK

SEND 75p FOR FULL CATALOGUE (Refundable against purchase).
DEALERS ENQUIRIES WELCOME.

ANGLO AMERICAN SOFTWARE
138a Stratford Road, Birmingham B11 1AG
Tel: 021-771 2995/2736

ALL PRICES INCLUDE VAT & POSTAGE
24 Hour answering service
on 021-771 2995 for Access orders.

PLEASE SUPPLY

In enclose a cheque/PO for £ made payable to ANGLO AMERICAN or debit my

Access card number

Signature

NAME

ADDRESS

ZX81 16K

ANNOUNCING OUR NEW RANGE OF APPLICATION PROGRAMMES
WRITTEN BY THE DISCERNING — FOR THE DISCERNING

ZX81

1K

AS SEEN AT THE MICROFAIR

MICRO-MUSIC

A superb programme which turns your keyboard into a musically in tune instrument. Just load the programme and press the start key. The sound can be heard through the monitor of your cassette recorder or, if you wish, through an amplifier. The sound produced is crystal clear and can be recorded with ease.

NOTE

All the 16K programmes are menu driven and have extensive error traps built in which makes an error virtually impossible. The approximate running time for each programme is 7 minutes.

555 TIMER AND 741 OP AMP

Both of these programmes were written by full time electronics engineers and only the highest standards can be expected from these programmes. It may be noted that only a few of the many capabilities of these programmes are mentioned. For full details of the programmes mentioned in this advertisement, please write to: Dept. PI — SAE not necessary.

DATA DISCOUNT CLUB

On application for club membership you will receive: membership card and number, 10% discount on this and/or any future order, and you will also be included on our "latest release" bulletin list.

To join send a cheque/postal order for £4.00 to the address below.

PRICES

Bank	£6.95
Freezer	£6.95
Names	£6.95
Dates	£6.95
Timer (555)	£7.95
OP Amp (741)	£7.95
Micro-Music	£4.95

All prices include P & P

Trade prices on request.

Quantity and educational discounts available.

Please make cheques/postal orders payable to:

ZX MICRO-PRO. (BCM) MICRO-PRO, LONDON WC1 3XX

Telephone: (01) 404 5011 (24 hour message service)

ZX MICRO-PRO®

Director: K Haynes

THE TRS80 MODEL III SYSTEM

TRS80 MODEL III

The Radio Shack TRS-80™ Model III is a ROM-based computer system consisting of:
 • A 12-inch screen to display results and other information
 • A 65-key console keyboard for inputting programs and data to the Computer
 • A Z-80 Microprocessor, the "brains" of the system
 • A Real-Time Clock
 • Read Only Memory (ROM) containing the Model III BASIC Language (fully compatible with most Model I BASIC programs)
 • Random Access Memory (RAM) for storage of programs and data while the Computer is on
 • A Cassette Interface for long-term storage of programs and data (requires a separate cassette recorder)
 • A Printer Interface for hard-copy output of programs and data (requires a separate line printer, optional extra)
 • Expansion area for upgrading to a disk-based system (optional/extra)
 • Expansion area for an RS-232-C serial communications interface (optional/extra)



48K
£599
+ VAT

EXTENDED
GUARANTEE BY
COMPACARD

All these components are contained in a single moulded case, and all are powered via one power cord.

MICROLINE 80

£289 + VAT

• 80 cps Uni-directional • Small size: 342 (W) x 254 (D) x 108 (H) mm. • 160 Characters, 96 ASCII and 64 graphics • 3 Character sizes: 40, 80 or 132 chars./line • Friction and Pin Feed • Low noise: 65 dB • Low weight: 6.5 kg

MICROLINE 82A

£449 + VAT

• 80 cps Bi-directional logic seeking • Small size: 360 (W) x 326 (D) x 130 (H) mm. • 160 characters, 96 ASCII and 64 graphics, with 10 National character-set Variants. • 4 Character sizes: 40, 60, 80 or 132 chars./line • Built-in parallel and serial interfaces. • Friction and Pin Feed • Low noise: 65dB • Low weight: 8kg

MICROLINE 83

£649 + VAT

• 120 cps bi-directional logic seeking • 136 column printing up to 15in forms • Small size: 512 (W) x 328 (D) x 130 (H) mm. • 160 characters, 96 ASCII and 64 graphics with 10 National character-set variants • 3 Character spacings: 5, 10 and 16.5 Chars/in. • Built-in parallel and serial Interfaces • Friction and Pin Feed • Low noise 65dB • Low weight: 13 kg

CENTRONICS DOT MATRIX PRINTERS

737 £369 }
739 £469 } VAT

Standard Features

- Proportional Spacing
- Right Margin Justification
- 3 way paper handling
- Upper and lower case
- True Descenders
- Bi-directional Paper Mode
- Underlining capability
- Condensed/Expanded Print
- Sub-Scripts and Super Scripts
- Pin and Friction Feed
- 80/132 Column

739 as above with special feature of Dot Resolution Graphics.

HITACHI PROFESSIONAL MONITORS

9" - £129 £99.95 }
12" - £199 £149 } VAT

• Reliability Solid state circuitry using an IC and silicon transistors ensures high reliability. • 500 Lines horizontal resolution Horizontal resolution in excess of 500 lines is achieved in picture center. • Stable picture Even played back pictures of VTR can be displayed without jittering. • Looping video input Video input can be looped through with built-in termination switch. • External sync operation (available as option for U and C types). • Compact construction Two monitors are mountable side by side in a standard 19-inch rack.

THE NEW SHARP MZ-80A

A COMPACT READY TO RUN COMPUTER FOR ONLY £449 VAT

- 280 CPU
- 48K RAM
- 40 Character x 25 line Display
- Built in 9" High Focus Green Display
- Built in Audio Cassette Deck : Data Transfer 1200 bits/sec
- ASCII Keyboard, Upper & Lower Case, Graphic Symbols, Numeric Keypad • Editing, Cursor Control (Up, Down, Left, Right, Home, Clear, Deletion Keys) • Built in Clock & Music

We give a full one year's guarantee on all our products, which normally only carry 3 months guarantee.

EXTENDED
GUARANTEE BY
COMPACARD

INTERNAL DUAL DISC DRIVES

FD50A

• 40 Track • Double Density • 5½" Drives £589 + VAT
• 184320 Bytes per Disks

FD50E

• 80 Track • Double Density • 5½" Drives £679 + VAT
• 368640 Bytes per Drive

SUMMER SPECIAL OFFERS

Model 3 + Dual 40T Drives + MX80F/T	£1555
Model 3 + Dual 40T Drives + 737 Centronics	£1539
Model 3 + Dual 80T Drives + MX80F/T	£1657
Model 3 + Dual 80T Drives + 737 Centronics	£1649

THE GENIE SYSTEM

Ideal for small businesses, schools, colleges, homes, etc Suitable for the experienced, inexperienced, hobbyist, teacher, etc

GENIE I



STILL ONLY
£279
+ VAT

NOW INCLUDED: Sound, Upper and lower case, Extended BASIC and Machine Code enabling the Writing and Execution of Machine Codes Programming direct from Keyboard.

16K RAM, 12K Microsoft BASIC Extensive Software Range Self Contained PSU UHF Modulator Cassette. External Cassette Interface. Simply plugs into TV or Monitor Complete and Ready to Go Display is 16 lines by 32 or 64 Characters Switchable. 3 Manuals included, Users Guide, Beginners Programming and BASIC Reference Manual. BASIC Program Tape Supplied. Pixel Graphics

GENIE II



£299 + VAT

The NEW GENIE II an ideal Business Machine. 13K Microsoft BASIC in ROM. 71 Keyboard Numeric Keypad. Upper & Lower Case. Standard Flashing Cursor. Cassette Interface 16K RAM Expanded externally to 48K

GENIE I & II EXPANSION UNIT WITH 32K RAM £199 + VAT

PARALLEL PRINTER INTERFACE CARD £36.00 + VAT

All prices quoted are exclusive of VAT. Delivery is added at cost. Please make cheques and postal orders payable to COMP SHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS number



CREDIT FACILITIES AVAILABLE - send S.A.E. for application form.

MAIL ORDER SHOP

14 Station Road, New Barnet, Hertfordshire, EN5 1QW
 (Close to New Barnet BR Station - Moorgate Line)
 Telephone: 01-441 2922 (Sales) 01-449 6596
 Telex: 298755 TELCOM G
 OPEN (BARNET) - 10am - 7pm - Monday to Saturday

311 Edgware Road, London W2

Telephone: 01-262 0387

OPEN (LONDON) - 10am - 6pm - Monday to Saturday




"Europe's Largest Discount Personal Computer Stores"

TELEPHONE SALES

OPEN 24 hrs. 7 days a week

01-449 6596

A Journey to the STARS

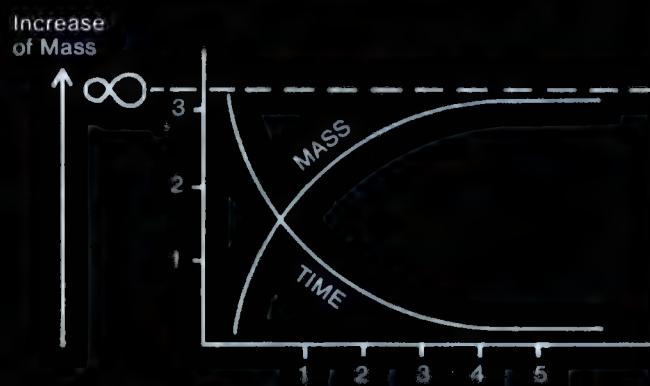

By ROGER DAVIS

Will it ever be possible to travel to the stars within a tolerable period of time?

On the face of it the answer would appear to be no.

The nearest star to our sun is Alpha Proxima which is a mere 4.2 light years distant. A light year is the distance that a light wave will travel in one year, and this puts our closest neighbour a staggering 24.636 Trillion (10^{12}) miles from us. The fastest a space vehicle has managed so far is 80,000 mph for the Voyager spacecraft on its way from Jupiter to Saturn last year.

Even if we could accelerate up to 1 million miles an hour it would still take 2,810 years to reach Alpha Proxima.

There have been futuristic proposals of astronauts put into suspended animation, or of self replicating colonies which would travel on for generations until the fiftieth or sixtieth grandchild would arrive at the star. It doesn't seem at all realistic and the people who have suggested it cannot have seriously thought such a scheme through. In any case we are interested in more stars than the handful which are just a few light years from us. What about the ones 50, 100 or even more away. Our own milky

way galaxy has 10,000 million stars in it, and is 100,000 light years in diameter.

If we are ever going to visit the stars there has to be another way.

And there just may be.

The answer could lie in Elbert Einstein's Theory of Relativity and its effect on matter which is travelling at very high speeds relative to an observer.

It has now been shown by numerous observations, and repeatable experiments that the 'Time Dilation' effect revealed in the equations of the 'Special Theory of Relativity', would appear to indeed be a reality.

For example:-

- ★ When two previously synchronised atomic clocks are compared after one of them has been taken for a ride in a jet aeroplane at 600 mph there is a measurable difference between their two times as accurately predicted by the theory.

- ★ Time as measured in a satellite, orbiting the earth at 10,000 mph slows down by a measurable amount relative to the time on earth.

- ★ Atomic particles which decay into other forms in a precise interval of time have their lifetimes extended when travelling at speeds close to the speed of light.

To test out the time dilation effects of the theory of relativity we have devised a fairly simple computer program to calculate the effects on an interstellar journey which we imagine future space explorers will be able to undertake.

The results should give a valuable insight into what our great great grandchildren will be capable of and also reveal some of the astonishing consequences inherent in Einstein's equations.

The year is 2182.

The solar system has been colonised by earth people and there are now settled communities living on Mars and the Moon. Orbiting around the earth there are huge space islands and it is from here that interstellar expeditions are planned and launched.

Technology has advanced in the 200 years since our time by at least as much as ours has from 1782. In particular rocket motors have been developed out of all recognition to anything we know today. We can only guess at their means of propulsion, perhaps it is an atomic rocket, perhaps an ion rocket. We only know that the power to weight ratio and the ability to generate a constant thrust for very long periods of time is far in advance of anything we can achieve today.

It is planned to launch an expedition to a nearby star and in order to do this we must first of all calculate:

(1) The life support systems to sustain the crew over the period of the expedition, in their reference time frame.

(2) The period away from earth, in earth's reference time frame.

(3) The power requirements for the rocket.

LET: K = Distance to the star. In Light Years.

J = Seconds per year. i.e. 31.536×10^6 .

L = Time on board the rocket. In years.

t_e = Time back on the earth. In years.

v = Velocity in metres per second.

c = Velocity of light. i.e. 3×10^8 metres per second.

From the Lorentz transformations as adapted by Einstein:

$\frac{L}{J}$

Time away fro earth (t_e) = $\sqrt{1 - v^2/c^2}$ seconds

Where the Lorenz transformation (G) is the term $/1 - v^2/c^2$

Therefore, $t_e = GLJ$

The distance travelled by the spacecraft must therefore be: $t_e v = GLJv$ metres.

But the distance from the earth to the star is: KJc metres.

Therefore, $KJc = GLJv$.

$\frac{L}{J}v$
Hence, $Kc = \sqrt{1 - v^2/c^2}$

$\frac{L^2 v^2}{K^2 c^2} = \sqrt{1 - V^2/c^2}$

From this equation we can extract the spacecraft velocity v.

$\frac{K}{L}$

Thus, $v = \sqrt{L^2 + K^2} \times c$ metres per second.

To calculate the time away from earth (in earth time) we now simply divide the distance to the destination by the velocity and add on the time we spend there.

Time away from earth = $K/v + M$ years. Where M = time at destination.

One important consequence of travelling close to the speed of light (and incidentally a severe limitation on our present technology to achieve these speeds) is the exponential increase of mass the faster we go.

This is calculated by multiplying the inertial mass of the spacecraft by the Lorentz transformation, G.

Mass increase due to relativity = $W \times G$ tons. Where W = inertial mass.

The computer program listed here is called STARTRIP and works out all the above equations.

It was written in MicroSoft Basic and so should be easily adaptable to most other Basic dialects. It is very 'user friendly', and also quite amenable to added refinements, such as calculating more precisely the effects of the four periods of acceleration and deceleration.

The program, as it is currently written, only calculates relativistic effects during the long cruise periods at speeds close to the speed of light. The periods of accelerate, decelerate on the outward journey and accelerate, decelerate on the homeward journey have not been worked on for relativistic effects. Time during these periods is assumed to be earth time and since the speeds during most of them will be well below the speed of light this is a reasonable assumption.

The graph showing the exponential nature of time dilation and mass increase further illustrates this point.

Another possible refinement is to calculate the effect of different amounts of accelerating force.

A constant, uniform acceleration, of 15 metres/sec² (i.e. approximately 1.5g) was assumed as being the highest level the astronauts could tolerate over a period of a few months. At this level it takes 7.61 months to reach speeds close to the speed of light and a similar period to slow down again to the speed of the star system to be visited, or to earth-bound levels on the return journey. At 1.5g everything would weigh 50% more to the astronauts so it must come as a welcome relief when the required speed

is reached and the rocket motors are switched off. The spacecraft will then cruise along with a constant momentum at this speed, (for ever if necessary) and the astronauts will experience the joys of weightlessness. 7.61 months from their destination they must switch the motors on again, this time pointing in the reverse direction, in order to synchronise their speed with that of the star system they are visiting.

Since the stars in our Milky Way Galaxy are not speeding away from each other, in the same way as the galaxies themselves are thought to be doing, it seems a fair assumption to make, that both our earth and the star system to be visited are moving at about the same speed. However, simple refinements to the program could take into account any relative movements between source and destination.

The minimum memory required is about 8K, but again it could easily be tailored to less by cutting down on the verbiage somewhat.

Double precision calculation has had to be used to achieve the fine accuracies necessary as the speed of light is approached, but even so the explorers are limited by the accuracy of the computer to our own Milky Way Galaxy. The machine cannot cope with distances greater than 99,999 light years from earth. If your computer cannot handle double precision calculations you will probably be confined to star systems around 40 to 50 light years away.

```

10 PRINT LCHR$(4)
20 PRINT TAB(20) "A JOURNEY TO THE STARS"
30 PRINT:PRINT
40 INPUT "WHAT IS THE DISTANCE TO THE STAR IN LIGHT YEARS, PLEASE.... .",K
50 INPUT "NUMBER OF YEARS THE ASTRONAUTS WANT TO SPEND ON THE ROUND TRIP ???",L
60 INPUT "HOW MANY MONTHS WILL THE EXPEDITION REMAIN AT THE DESTINATION...?",M
70 N = L - (M + 30.44)/12
80 REM 30.44 MONTHS IS 1 ACCELERATION PERIODS AND 2 DECELERATION PERIODS.
90 V = K/SQR(N*N + K*K)
100 PRINT:PRINT
110 PRINT "THE RESULTS OF THE CALCULATIONS ARE AS FOLLOWS:--"
120 PRINT
130 PRINT "TO ACCOMPLISH THE JOURNEY IN" L "YEARS"
140 PRINT "A CONSTANT VELOCITY OF" V & ".1 MILLION MILLS PER HOUR"
150 PRINT "MUST BE MAINTAINED FOR" N "YEARS."
160 PRINT "THIS REPRESENTS A SPEED OF" CDBL(V)/C METRES/SECOND,"
170 PRINT "OR" CDBL(V)*100 "% OF THE SPEED OF LIGHT."
180 G = 1/SQR(1 - V*V)
190 PRINT "TOTAL DURATION, IN EARTH TIME =" (2*N/V) + M/12 "YEARS"
200 PRINT:PRINT
210 INPUT "DO YOU WISH TO INVESTIGATE THE ROCKET POWER REQUIRED? Y/YES/N/NO...",N$
220 PRINT
230 IF N$ = "YES" THEN 40 ELSE 350
240 PRINT "THANKYOU"
250 PRINT "WHAT IS THE MASS OF YOUR SPACECRAFT AT ZERO SPEED ?"
260 INPUT "CHOOSE BETWEEN 1 AND 10 TONS... ",W
270 PRINT
280 PRINT "With a Physically tolerable, constant acceleration"
290 PRINT "of 1.5g the spacecraft will reach a velocity close to c"
300 PRINT "in 7.61 months, earth time."
310 F = W * 5280 * 48 INITIAL THRUST
320 PRINT "INITIAL THRUST = F " lbs.
330 PRINT "THIS RISES TO -" F * 6 "lbs. AT THE MAXIMUM VELOCITY."
335 PRINT "THE MASS OF THE SPACECRAFT INCREASES TO" G*W "TONS."
340 PRINT
350 PRINT "THANKYOU.....AND BON VOYAGE."
360 END

```

(Continued from Page 24)

INPUT AT, on most civilised systems, stops the cursor at the point on the screen specified. So when the user of the program starts typing, the answer appears at the point where the question was asked. Not on this one. INPUT always produces a prompt on the bottom line, whether INPUT AT or not.

Like the colours, INVERSE is a bit tricky to manage — it switches the INK and PAPER status round. The problem is to work out how much of the screen will be affected. Sometimes, it is just the character blob; other times, it's the whole graphics area.

See tape handling, above.

MERGE More tape handling, above.

MOVE Disk command.

OPEN# Disk command.

OUT Gives direct control over the wires at the back of the computer. Anybody designing a machine control system will be glad of this. Should somebody one day put the language APL on the Spectrum, he will be glad of this, because APL uses overprinting — one character on top of another — and this will allow it. Put a double quote on top of an O and you get an Umlaut, says the manual. I got a wonky rabbit, but I'm sure my German friends wouldn't mind.

See INK.

Before buying a Spectrum, it would be a good idea to see somebody do some Plotting. As long as you stick to monochrome plotting — that is, without changing paper and ink colours throughout the operation, Sinclair's claim is quite true.

Sinclair says that his machine is superior to the BBC micro, because his hi-resolution graphics use less memory. So, he says, when you use high resolution graphics, on a BBC Model A, you only have 3 Kbytes of memory left for your program. This is true enough — but it implies that his hi-res graphics are the same as the BBC graphics, and they certainly are not.

INVERSE

LOAD

MERGE

MOVE

OPEN#

OUT

OVER

PAPER

PLOT

PRINT

READ

RESTORE

SAVE

VERIFY

Apart from the problem of going "off the screen" mentioned above, there is the question of how versatile they are. And the Spectrum graphics have an inherent limitation, in that there can be only two colours in any character square — the ink colour, and the paper colour.

Any square can have any individual pixel set to the paper or ink, so the fine detail possible is good. But take a red line, and cross it over a black line, and the square where they cross will become confused. Draw several intersecting lines, and you end up with blobs instead of pixels. With care, the attentive screen designer can get around these — but on the BBC machine and on the Commodore VIC, the attentive designer doesn't have to bother.

Yes, there was a PRINT on the ZX81, but there are significant differences in this new Basic. Mainly, these are due to the fact that the new machine doesn't use the unique codes of the ZX81, and uses American Standard Code for Information Interchange (Ascii) instead. So there are "control" characters, which have control effects on the screen. A single quotation mark produces a line feed and carriage return. And colour items produce colour changes.

This, like the next keyword, goes with the DATA statement.

With a number, starts READING at the numbered item. Otherwise, works as in all ordinary Basics.

See tape handling notes, above.

See tape handling.

key as the PRINT command. The often needed semicolon is right next to it. Similarly LET and = are on the same key, THEN and GOTO are on the G key, FOR and TO on the F key with STEP next to them on the D key.

To say that the keyboard is "typewriter pitch" is to mislead. Yes, it is, but the space bar is missing, the ENTER key is where you expect a semicolon, comma and full stop are SHIFT characters on N and M, and anyway, you have to press the keys in the middle to be sure that they register. It's a great improvement on the ZX81, but that's all I can really say for it.

Display

Prototypes, says Clive Sinclair, are not as good as the production models — the fault which made the colours shift and shimmer like a mirage in the Sahara will be cured by reducing the bandwidth of the colour. In fact, this will reduce, not eliminate, the "dot crawl" problem, and the colour will never be capable of display on a high quality monitor to ultra-high resolution like the BBC micro. Then again, for £125 what do you expect?

Basic

It's a noticeable improvement on ZX81 Basic. That was pretty good. I don't think the speed of Basic matters too much to most people, which is just as well for the Spectrum. The only thing slower is a Casio pocket Basic calculator, or the ZXC81 in SLOW mode. In FAST mode, the ZX81 beats it comfortably. And any model BBC micro is between four and ten times faster, judged on the standard benchmarks originally published in Kilobaud. I wouldn't mention this, but Clive did say his machine was "more powerful" than the BBC.

The BBC micro has a built-in assembler. It runs slowly, but it runs. This machine has no assembler.

The Manual

Better than average despite some excruciating puns by Steven Vickers, which escaped the censor. Some were quite nice — comparing strings, for example, Vickers asks "Which of these is the lesser? EVIL or evil?"

It certainly is better than the BBC manual was, though the new BBC manual will be out by the time you read this, and it may even include all the functions of the machine.

General

It is terrific value for money. At the moment, there is so much more software available for the Commodore VIC that I think the non-curious customer might prefer that machine — but within six months, that will change and the Spectrum will (I think) have the edge.

Once it has its diskette drives, however, there won't be anything in the world to touch it. And somebody will put CP/M on it, you'll see.

User impressions

The new keyboard is made of rubber, and it squishes. Whatever colour the keys eventually are, I think you will need good light and good eyesight to read the characters in red on the keys themselves. They are little, fiddly characters like the equals sign, the commas, colons, multiplier, minus, <> and so on. The layout is logical enough. Start a command like PRINT, and you will find the quote makes on the same

The MICRO PROFESSOR solves the 'mystery' of micro-processors.

Micro-Professor is a low-cost Z80A based microcomputer which provides you with an interesting and inexpensive way to understand the world of microprocessors.

Micro-Professor is a microprocessor learning tool for students, hobbyists and engineers. It is also an ideal educational tool for teaching in schools and universities.

The main object of **Micro-Professor** is for the user to understand the software and hardware of a microcomputer easily and conveniently. Besides the complete hardware/software system you have the users experimental manual. It includes self-learning text with 20 experiments which range from simple, software

programming to designing a complex electronic game. Completed programmes can be stored and re-read via the cassette interface. 2K bytes of monitor source program with documentation is also provided in the manual.

Micro-Professor provides a wide range of other applications: Low cost prototyping tool • Low

cost development tool • Process controller • Electronic music box • Timer • Noise generator • Home appliance control • Burglar alarm • System control simulation Tester ... and much more!

New
Add on products
Speech synthesiser
board
EPROM programmer
board

TECHNICAL SPECIFICATION

CPU Z80A CPU high performance microprocessor with 158 instructions

SOFTWARE COMPATIBILITY Capable of executing Z80/8080/8085 machine language programs

RAM 2K bytes expandable to 4K bytes

ROM 2K bytes of sophisticated monitor expandable to 8K bytes

INPUT/OUTPUT 24 system I/O lines

DISPLAY 6 digit 0.5" red LED display

AUDIO CASSETTE INTERFACE 165 bit per second average rate for data transfer between memory and cassette tape

EXTENSION CONNECTORS Provides all buses of CPU, channel signals of CTC and I/O port bus of PIO for user's expansion

COUNTER TIMER CIRCUITS Socket is provided. Z80-CTC IC extra

PARALLEL I/O CIRCUITS Socket is provided. Z80-PIO IC extra

SPEAKER AND SPEAKER DRIVER CIRCUITS A 2.25" - diameter speaker is provided for user's applications

USER'S AND EXPERIMENT MANUAL Complete self-learning text with experiments and applications.

OPTIONS (Prices on application) Z80-CTC. EPROM programmer board. Prototyping Board Z80-PIO Speech synthesiser board. Audio Cassette 2K Ram

KEYBOARD 36 keys including 19 function keys, 16 hex-digit keys and 1 user defined key

A 9V, 0.5A adaptor and 350 page manual is provided.

Formal orders requiring

Acc & 30 days credit.


Please ask for price list.

New
"BASIC"
EPROM &
Keyboard Overlay
£9.95

Complete the coupon today!
MICRO-PROFESSOR(S)
(+ £2.95 p & p)

Please allow 28 days for delivery
Flight Electronics Ltd, Flight House
Quayside Road, Southampton
Hants SO2 4AD
Tel: (0703) 34003/27721
Telex: 477793
E&C

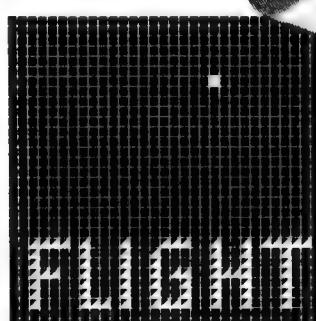Use the unique
Micro-Computer to truly
understand the inside
workings of microprocessors,
or simply use as a Z80A
evaluation system



Flight Electronics Ltd.

£69.95*
+ p&p
* Mail Order only

MICRO-PROFESSOR is a trade mark of Multitech Industrial Corporation. Z80 is a trade mark of Zilog Inc.

To receive your MICRO-PROFESSOR
Please send me
I enclose cheque/P.O. for £.....
Name
Address

PRINTERFACING THE ATOM

by Tim Edwards

If you were buying a printer specifically for the Atom then you would obviously choose one with a Centronics parallel interface, but supposing you have access to a different type of printer how would you link it up to the Atom? In this, the first of two articles, I shall look at the general principles of how to set up your own interface and replace the Centronics routine with a suitable routine to run that interface, be it serial or parallel. The example given in this article, to illustrate these principles, is the Qume Sprint 5. Then in next month's article I shall describe the more complex system necessary to link up to a Commodore printer which uses the I.E.E.E.488 interface.

OUTPUTTING CHARACTERS

Whenever you write a character on the screen and/or to a printer, either in direct mode from the keyboard or in a program, the Atom executes a JMP(WRCVEC). In other words it looks at locations #208 and #209 to find the WRite Character VECtor, which is the start address of the routine to which this character should be sent. This is illustrated in figure 1. If you wish therefore to add your own routine, you need first to change WRCVEC to point to the start of your routine, and then at the end of your routine, jump back into the Atom's own routine.

It is worth mentioning at this point that normally WRCVEC points to #FE52, but if you are using the Wordpack r.o.m. then a different routine is used for outputting characters, which starts at #ACCE. Therefore the best thing to do is to have an initialisation routine which removes the present value of WRCVEC and stores it for later use and replace it with your own WRCVEC. Then at the end of your own routine you execute a JMP(OLD WRCVEC). This is illustrated in figure 2.

What has to go into your special printer routine?

The sample routine, which is for the Qume Sprint 5, is given in Appendix A and will be referred to in the following explanation by using the BASIC line numbers.

1) Initialisation (lines 40 – 80)

Remove the old WRCVEC and replace it with a pointer to the start of your routine, set up the VIA appropriately at output, and send out a carriage return to check that the printer is responding.

2) Write a character routine (lines 90 – 280)

Lines 90 to 180 is the routine used to output a single character to the printer. The main part of the routine consists basically of saving all the registers (line 190), dealing with the individual character, first checking to see if it is a control code (lines 220 – 280), and then restoring the registers before jumping back into the Atom's own routine (line 210). The way in which the individual character is dealt with is shown in the form of a flow chart in figure 3. If a control B or C is detected, it must not be sent on to the Atom routine or it will think that there is a Centronics printer attached and wait for the appropriate response which will not of course be

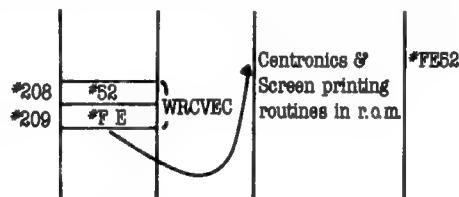


Figure One Illustration of JMP (WRCVEC)

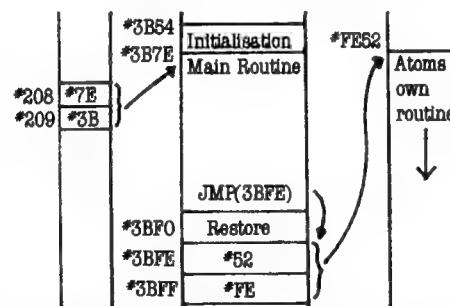


Figure Two How new printer routine is fitted into existing routine

forthcoming. Therefore these control codes are replaced with either a null (0) or an ESC (27) before passing on to the Atom routine.

Another point to note is that some printers have an auto-linefeed. In other words they respond to a carriage return (13) by executing a carriage return and a line feed. To cope with this the Atom uses memory location #FE to store a "character not sent to the printer", and on BREAK this is initialised to a linefeed character (10). So all you have to do is to compare the character with the contents of #FE and, if equal, not output it to the printer (line 270). This then suppresses all linefeed characters as far as the printer is concerned, but if you should want to send out a linefeed character, all you have to do is to alter the contents of #FE, send out the linefeed and then restore #FE to a linefeed character.

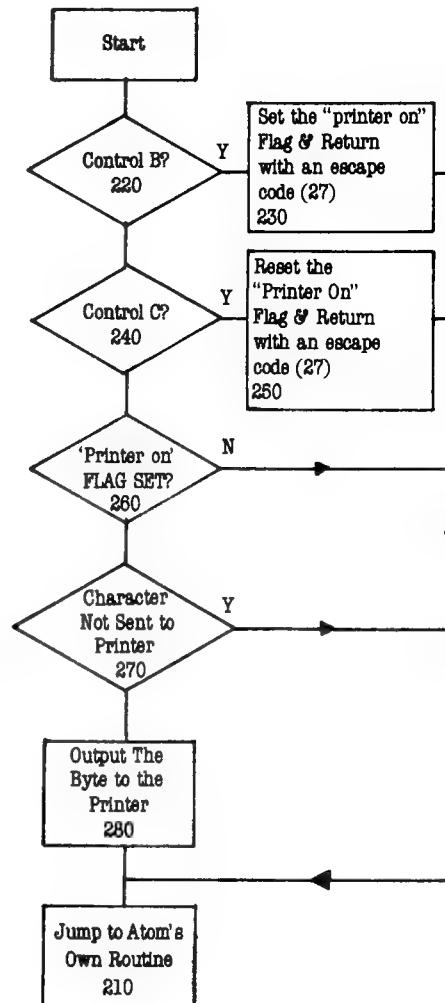


Figure Three Flow Diagram of Characters Handling Routines

DOT-BY-DOT SCREEN DUMP

The routine for producing a dot-by-dot screen dump of the high resolution graphics screen is given in Appendix B. It sends out spaces or full stops according to whether each bit in the video ram is clear or set. If a whole byte is zero then instead of sending out eight individual space characters, it sends out the control codes which make the printer spacing eight times what it was previously, and then just sends out one space character. Since it takes three characters to change the print spacing this is not much of a saving for a single zero byte, but in practice large areas of the screen may well be clear, in which case you get a succession of zero bytes and only need to change back to the narrow spacing when you come to the first non-zero byte.

To run the routine use LINK #3B0B from within a BASIC program, or JSR #3B0B from a machine code program. A routine is also provided so that you can initiate the screen dump with an interrupt. To set this up, you have to do a LINK or JSR #3B00 which sets the interrupt vector to point to the interrupt routine at LL14. Then when you momentarily ground the IRQ line, all the registers are saved, the screen dump routine is run, and the registers are restored. Therefore when the screen dump is finished, the program continues as if nothing had happened. It would be a good idea when using this routine to run the interface at the full 1200 baud, because even at this speed it can take 5 minutes or so to do a full screen dump. A sample dump is shown in figure 5.

INTERFACING TO THE QUUME SPRINT 5

In order to drive the Quume Sprint 5 using the routine in Appendix A, you will need an MC1488 or SN75188 to produce the RS232 drive requirements. This chip uses dual supplies, but the voltages are not too critical. Anywhere between 9V and 12V will do, so you could use a couple of 9V dry batteries. The connections are shown in figure 4. The "data terminal ready" line is sensed by the Atom to check whether the Quume's input buffer is full, and is only really necessary if you are using the full speed of 1200 baud. The baud rate is set to 1200 baud by the LDX@14 at LL13. For 600 baud use LDX@33, 300 baud would be 65, and 110 baud would be 180.

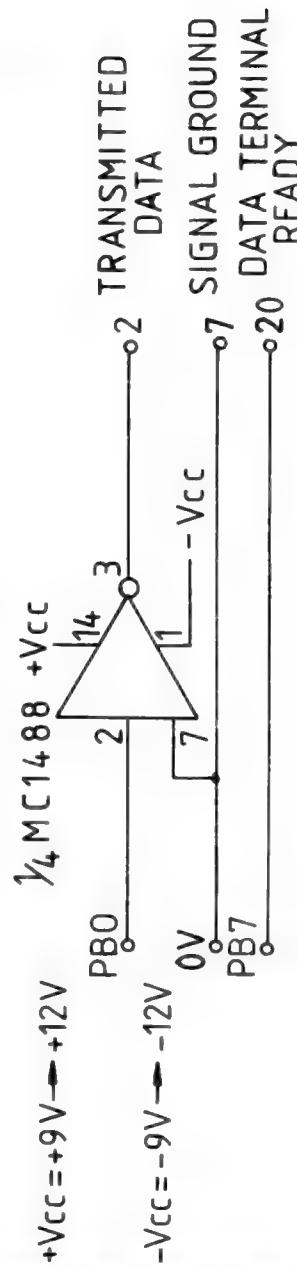


Figure Four RS 232 Interface

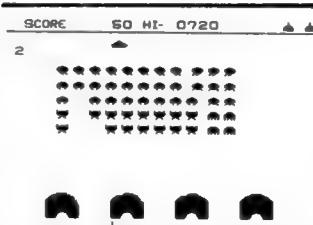


Figure Five Example of a dot-by-dot printout of the Atom's high resolution screen

NEXT MONTH:

How to interface
the Atom
to a Commodore
Pet printer.

Appendix B Dot-By-Dot Screen Dump Routine

```

10 I = #3B54; M = #3BFC; B = #B800; V = #208
20 DIMLL8; FORN = 0TO9; LLN = #FFFF; N.
30 P. $21; FORN = 1TO2; P = I; [
40 :LL0 LDAV; STAM+2; LDAV+1; STAM+3
50 LDA@ (LL5%256); STAV
60 LDA@ (LL5/256%256); STAV+1
70 LDX@1; STXB+2; DEX; STXM+1
80 LDA@13; STAM; JSRLLI; RTS
90 :LL1 LDX@0; STXB
100 LDAM; ORA@#80; LDX@10
110 :LL2 JSRLL3\delay routine
120 SEC; RORA; ROLB
130 DEX; BNELL2
140 RTS
150 :LL3 PHA; TXA; LDY@10
160 :LL4 LDX@14; DEX; BNEP-1
170 DEY; BNELL4
180 TAX; PLA; RTS
190 :LL5 PHP; STAM; TXA; PHA; TYA; PHA
200 BITB; BPLP-3; JSRLL6
210 PLA; TAY; PLA; TAX; LDAM; PLP; JMP(M+2)
220 :LL6 LDAM; CMP@2; BNELL7
230 LDA@128; STAM+1; LDA@27; STAM; RTS
240 :LL7 LDAM; CMP@3; BNELL8
250 LDA@27; STAM; LDA@0; STAM+1; RTS
260 :LL8 BITM+1; BMIP+3; RTS\printer on?
270 CMP@FE; BEQP+5
280 JSRLLI; RTS
290 ]; N.; LINK I
300 P. $6$2"INITIALISE"&I'"BYTE 0/P"&LL1"
310 @=5; P. $3" *SAVE QUME"&I,&P,&I
320 END

```

Appendix A Printer routine for a Quume Sprint 5

```

10 L=14; M=#80; Q=#80
20 V=1; H=2; REM vert. & horiz. spacing
30 V=V+1; N=H+1; W=8*H+1; B=#B800
40 DIMLLL; FORC=0TO1; LLC=#FFFF; N.
50 P.$21; FORC=1TO2; S=#3B00; P=S; [
60 LDA@ (LL14%256); STA#204
70 LDA@ (LL14/256%256); STA#205
80 RTS
90 :LL0 LDX@192; LDY@1; STYB+2
100 DEY; STYQ+2; LDA@#80; STAQ+3
110 LDA@32; STAQ; LDA@27; JSRLL8
120 LDA@30; JSRLL8; LDA@V; JSRLL8
130 LDA@N; STAQ+4; JSRLL7
140 :LL1 LDA(Q+2), Y; STAQ+1
150 CMP@0; BNELL3
160 LDA@W; CMPQ+4; BEQLL2
170 STAQ+4; JSRLL7
180 :LL2 LDA@32; JSRLL8; JMLLL5
190 :LL3 LDA@N; CMPQ+4; BEQP+7
200 STAQ+4; JSRLL7
210 TXA; PHA; LDX@8
220 LDAQ+1; PHP
230 :LL4 LDA@32; PLP; BPLP+4
240 LDA@46; JSRLL8
250 ASLQ+1; PHP
260 DEX; BNELL4
270 PLP; PLA; TAX
280 :LL5 INY; PHP; DECQ; BNELL6
290 LDA@13; JSRLL8; LDA@32; STAQ; DEX
300 :LL6 PLP; BNEP+4; INCQ+3
310 TXA; BNELL1
320 LDA@27; JSRLL9; LDA@26; JSRLL9
325 LDA@73; JSRLL9; RTS
330 :LL7 TXA; PHA; TYA; PHA
340 LDA@27; JSRLL9; LDA@31; JSRLL9
350 LDAQ+6; JSRLL9
360 PLA; TAY; PLA; TAX; RTS
370 :LL8 STAM; TXA; PHA; TYA; PHA
380 JSRLL10; PLA; TAY; PLA; TAX; RTS
390 :LL9 STAM
400 :LL10 BITB; BPLP-3; LDX@0; STXB
410 LDAM; ORA@#80; LDX@10
420 :LL11 JSRLL12\delay routine
430 SEC; RORA; ROLB
440 DEX; BNELL11
450 RTS
460 :LL12 PHA; TXA; LDY@10
470 :LL13 LDX@14; DEX; BNEP-1
480 DEY; BNELL13
490 TAX; PLA; RTS
500 :LL14 TXA; PHA; TYA; PHA
510 JSR#FD1A; JSRLL0
520 PLA; TAY; PLA; TAX; PLA; RTI
530 ]; N.; @=5; P. $6"ROUTINE STARTS AT #&LL0"
540 P. " *SAVE SDUMP"&S, &P, &LL0"
550 END

```

Transformer & Line

The transformer is often used in networks of the types covered, and it seemed highly desirable to include such a section. To completely define a transformer would require a complicated circuit due to the effect of stray inductance and capacitance. These factors however are very difficult to measure in isolation, and in any case are likely to vary from unit to unit wound from the same design. It is fortunate therefore that they only seriously affect results at the top end of the frequency band covered, and because of production variations in their values, it is good practice to design the physical lay-out so that the major effect lies just outside of the band covered and may normally be ignored.

In Fig. 5.1 is shown the major equivalent used to account for copper losses, winding self-inductance, and leakage inductance between the two. In Fig. 5.1(a) the location of these values, both in the physical unit and in the Z array are shown. The schematic circuit shows the equivalent circuit used for computation of the matrix. In (b) is shown the Z matrix for this equivalent which is a single tee circuit such as was used in the previous article. The Z matrix is used here because memory space is minimised for computation, and in (c) is shown the standard conversion formula between Z and A together with the resulting equations for computing the matrix shown for use in the program.

In the listing shown lines 2200 through 2245 compute the values and assemble them into a matrix for return to the calling program. This matrix will cover only the major portion of the transformer, but the iron losses and self capacitance of each winding must be covered by a second matrix of the 'CR' type 7 added as second matrix across the windings by matrix multiplication as already covered in earlier articles. Unless the upper edge of the frequency range is important, a single additional matrix of this type will suffice, but if the edge of the range is vital, where the value of the coupling factor begins to give a drooping characteristic, then two matrices of type 7 should be added, one at the input covering the primary self capacitance and the iron losses, and a second at the output covering secondary self-capacitance and any stray ohmic losses which can be measured on a few production items.

The only secondary factor not covered will be the capacitance between the two windings, and if this is vitally important, then it can be covered, providing equipment is available to measure it, by use of an unsymmetrical form of bridged tee

By Ralph Lovelock

filter adapted from the symmetrical form in the last article, together with two type 7 sections added on either side of the main matrix. If there were to be a desire for this expressed by readers, such an additional section could be published involving an expansion of the Y array, and addition to some other portions of the program.

The normal transmission line is often used as a filter, as a matching unit, and as a delay line, as well as the normal method of conveying communication from one location to another. It comprises a complete ladder network in its own right, and can be simulated over a limited frequency range by a set of sections comprised of normal impedance nets in series. The line itself has a distributed impedance instead of a succession of local ones, and where the coverage of a wide frequency range is required it is essential that the whole length shall be of uniform distributed values. This is usually catered for by fairly expensive cables manufactured to very close tolerance.

Since there are some uses where a line is inserted as a part of a series of ladder networks, it was thought desirable to include it in this suite. It should be realised however that all the values used in the computation should be the 'effective' values as measured on a high accuracy bridge, and not the approximate calculated ones. This applies particularly to the length, which in most cases will be different from the physical length of the cable used.

The computation involves a new type of complex trigonometrical functions, called 'hyperbolic' because they were first used for calculations involved with the hyperbola.

Fig. 5.2 shows the complete details of the line computation used here, and (c) covers the relationships used for calculation. This is listed as a small separate subroutine, since although tables are readily available for the functions of real values, they are inconvenient to use for functions of the 'complex' values involved in electrical circuits, and it may be desired for other purposes to have available a quick and easy way of obtaining such values. The listing of this sub-routine is contained in lines 1600 through 1650.

In the figure (a) shows the data values required and their location within the Z array, while (b) shows the formulae for calculating the 'characteristics' which are required for computation. These characteristics are the values normally used for quality control of production. A second subroutine, in lines 1700 through 1750 gives a straight-forward routine for obtaining them, and is given here as a separate routine since it might well be desired to obtain them for other purposes.

The matrix for the line is given in (e) while (d) covers the question of the 'signs' to be used for the A and B arrays when using these relationships. The non-mathematical reader need not bother about these details, since the program automatically sorts this out, but they are given for those who wish to follow exactly what the listing is doing. It commences by calling up the routine to

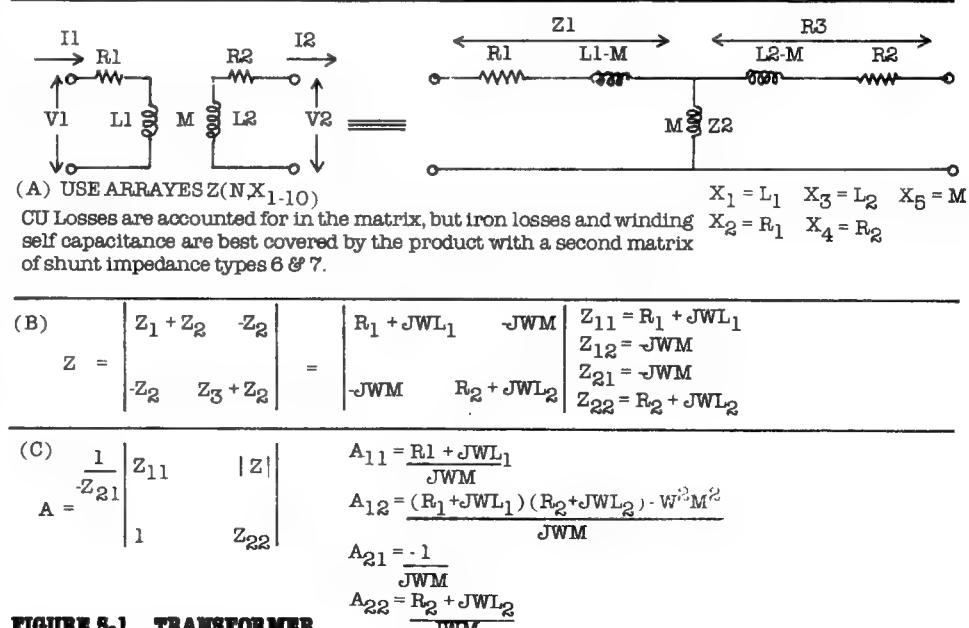


FIGURE 5-1 TRANSFORMER

WATFORD ELECTRONICS

33-35, CARDIFF ROAD, WATFORD, HERTS WD1 8ED, ENGLAND
Tel: Watford (0923) 40588, Telex: 8956095 WAELEC

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. & P ADD 5% TO ALL ORDERS. OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders no VAT. U.K. customers please add 15% VAT to total cost incl. p&p.
We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Open Monday to Saturday, 9.00 am to 6.00 pm. Ample FREE Car parking space available.

POLYESTER CAPACITORS: (Axial Lead) 400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8 11p; 10n, 15n, 18n, 22n 12p; 33n, 47n, 68n 18p; 100n, 150n 20p; 220n 30p; 33n 42p; 47n 52p; 68n 60p; 1μF 68p; 2μ2, 4μF 85p. 1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n, 100n 50p.

POLYESTER LEADLESS CAPACITORS: 250V: 10n, 15n, 22n, 27n 8p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 13p; 680n 18p; 1μF 24p.

ELECTROLYTIC CAPACITORS (Values in μF) 500V: 10μF 52p; 47 78p; 63V: 0.47-1.0 1.5 2.2 3.3 3.8; 8.47 10 10p; 15, 22, 12p; 33 15p; 47 68 16p; 100 19p; 220 26p; 1000 70p; 2200 90p; 25V: 5, 47, 10, 22, 47 80p; 150 120p; 300 150p; 600 300p; 1000 400p; 2500 1000p; 3200 1500p; 6800 3000p; 10000 4000p; 15000 7000p.

TAG-END TYPE: 84V: 4700 24p; 3300 19p; 2200 16p; 135p; 50V: 3300 15p; 2200 11p; 40V: 4700 160p; 25V: 10000 32p; 15000 34p.

TANTALUM BEAD CAPACITORS: 35V: 0.1μF 22, 0.33 18p; 0.47 68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 28p; 16V: 2.2, 3.3, 16p; 4.7, 6.8, 10, 18p; 15 36p; 22 30p; 33, 47 40p; 100 75p; 220 88p; 10V: 15 22 26p; 33, 47 35p; 100 55p.

SILVER MICA (pF) **SIEMENS** multilayer miniature capacitors: 2.3, 3.4, 6.8, 8.2, 10, 12, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180, 15p each 220, 250, 270, 330, 360, 390, 470, 600, 800 & 820pF 21p each 1000, 1200, 1800 30p each 3300, 4700 60p each.

MYLAR Film CAPACITORS 100V: 1nF, 2n, 4n, 47, 10 6p 15nF, 22, 30, 40, 47n 7p 56nF, 100, 200n 9p

CERAMIC Capacitors: 50V Range 1pF to 6800pF 4p 10nF, 15n, 22, 33, 47nF 5p 100nF/30V 7p; 220n/6V 8p.

Sound Generator IC AY-3-8910 £6

Special Booklet for above £2.50

100+ price applies to Resistors of each type not mixed values

RESISTORS - Hi-stab, Miniature, 5% Carbon, RANGE Val. 1-99 100+ 0.25W 0.2-4 M7 E24 2p 1p 0.5W 0.2-4 M7 E12 2p 1p 1W 0.2-10M E12 5p 3p 2% Metal Film 10Q-1M 8p 4p 1% Metal Film 51Q-1M 8p 6p

LINEAR IC's LC7130 340 NE531 140 TL072CP 50 6802 400 7441 68 74173 80 LS47 38 LS253 35 4023 18 4435 850 LF347 150 NE543 225 TL074CN 100 6803 850 7442 32 74174 80 LS48 45 LS257 35 4024 33 4440 999 702 75 NE544 210 TL081CK 25 6804 160 7443 32 74174 80 LS49 50 LS258 35 4025 16 4450 360 LF351 48 NE555 18 TL082CP 45 6805 670 7444 90 74175 40 LS51 14 LS259 75 4026 80 4451 350 709C 8 pin 35 LF353 95 NE555 16 TL083CK 75 6806 520 7445 55 74177 45 LS55 14 LS260 22 4027 24 4490 350 710 48 LF355 85 NE556DB 45 TL084CP 95 6809 895 7446 55 74178 80 LS63 14 LS261 138 4028 50 4500 675 LF356 44 NE560 325 TL085CP 55 6810 120 7447 55 74179 80 LS64 14 LS262 60 4029 60 4501 675 747C 14 pin 65 LF357 110 NE561 398 TL086CP 55 6821 125 7448 46 74180 80 LS73 14 LS263 22 4030 30 4502 675 748C 8 pin 36 LF398 475 NE562B 398 TL087CP 55 6821 125 7449 55 74181 115 LS74 14 LS264 22 4031 30 4503 675 752 8 pin 185 LM10 360 NE564 420 UA2240 120 6840 412 7450 38 74182 115 LS75 14 LS265 22 4032 30 4504 675 810 159 LM301A 26 NE565A 120 UA78450 230 6843 £12 7451 38 74183 115 LS76 14 LS266 20 4033 16 4505 675 9400CJ 350 LM307 00 NE566 155 UA78540 230 6843 £12 7452 38 74184 115 LS77 14 LS267 20 4034 16 4506 675 709C 8 pin 35 LF353 95 NE567 140 UA810 170 6847 850 7453 38 74185 115 LS78 14 LS268 20 4035 16 4507 675 711 48 LF355 85 NE568 140 UA810 170 6847 850 7454 38 74186 115 LS79 14 LS269 20 4036 16 4508 675 712 48 LF356 85 NE569 140 UA810 170 6847 850 7455 38 74187 115 LS80 14 LS270 20 4037 16 4509 675 713 48 LF357 85 NE570 140 UA810 170 6847 850 7456 38 74188 115 LS81 14 LS271 20 4038 16 4510 675 714 48 LF358 85 NE571 140 UA810 170 6847 850 7457 38 74189 115 LS82 14 LS272 20 4039 16 4511 675 715 48 LF359 85 NE572 140 UA810 170 6847 850 7458 38 74190 115 LS83 14 LS273 20 4040 16 4512 675 716 48 LF360 85 NE573 140 UA810 170 6847 850 7459 38 74191 115 LS84 14 LS274 20 4041 16 4513 675 717 48 LF361 85 NE574 140 UA810 170 6847 850 7460 38 74192 115 LS85 14 LS275 20 4042 16 4514 675 718 48 LF362 85 NE575 140 UA810 170 6847 850 7461 38 74193 115 LS86 14 LS276 20 4043 16 4515 675 719 48 LF363 85 NE576 140 UA810 170 6847 850 7462 38 74194 115 LS87 14 LS277 20 4044 16 4516 675 720 48 LF364 85 NE577 140 UA810 170 6847 850 7463 38 74195 115 LS88 14 LS278 20 4045 16 4517 675 721 48 LF365 85 NE578 140 UA810 170 6847 850 7464 38 74196 115 LS89 14 LS279 20 4046 16 4518 675 722 48 LF366 85 NE579 140 UA810 170 6847 850 7465 38 74197 115 LS90 14 LS280 20 4047 16 4519 675 723 48 LF367 85 NE580 140 UA810 170 6847 850 7466 38 74198 115 LS91 14 LS281 20 4048 16 4520 675 724 48 LF368 85 NE581 140 UA810 170 6847 850 7467 38 74199 115 LS92 14 LS282 20 4049 16 4521 675 725 48 LF369 85 NE582 140 UA810 170 6847 850 7468 38 74200 115 LS93 14 LS283 20 4050 16 4522 675 726 48 LF370 85 NE583 140 UA810 170 6847 850 7469 38 74201 115 LS94 14 LS284 20 4051 16 4523 675 727 48 LF371 85 NE584 140 UA810 170 6847 850 7470 38 74202 115 LS95 14 LS285 20 4052 16 4524 675 728 48 LF372 85 NE585 140 UA810 170 6847 850 7471 38 74203 115 LS96 14 LS286 20 4053 16 4525 675 729 48 LF373 85 NE586 140 UA810 170 6847 850 7472 38 74204 115 LS97 14 LS287 20 4054 16 4526 675 730 48 LF374 85 NE587 140 UA810 170 6847 850 7473 38 74205 115 LS98 14 LS288 20 4055 16 4527 675 731 48 LF375 85 NE588 140 UA810 170 6847 850 7474 38 74206 115 LS99 14 LS289 20 4056 16 4528 675 732 48 LF376 85 NE589 140 UA810 170 6847 850 7475 38 74207 115 LS100 14 LS290 20 4057 16 4529 675 733 48 LF377 85 NE590 140 UA810 170 6847 850 7476 38 74208 115 LS101 14 LS291 20 4058 16 4530 675 734 48 LF378 85 NE591 140 UA810 170 6847 850 7477 38 74209 115 LS102 14 LS292 20 4059 16 4531 675 735 48 LF379 85 NE592 140 UA810 170 6847 850 7478 38 74210 115 LS103 14 LS293 20 4060 16 4532 675 736 48 LF380 85 NE593 140 UA810 170 6847 850 7479 38 74211 115 LS104 14 LS294 20 4061 16 4533 675 737 48 LF381 85 NE594 140 UA810 170 6847 850 7480 38 74212 115 LS105 14 LS295 20 4062 16 4534 675 738 48 LF382 85 NE595 140 UA810 170 6847 850 7481 38 74213 115 LS106 14 LS296 20 4063 16 4535 675 739 48 LF383 85 NE596 140 UA810 170 6847 850 7482 38 74214 115 LS107 14 LS297 20 4064 16 4536 675 740 48 LF384 85 NE597 140 UA810 170 6847 850 7483 38 74215 115 LS108 14 LS298 20 4065 16 4537 675 741 48 LF385 85 NE598 140 UA810 170 6847 850 7484 38 74216 115 LS109 14 LS299 20 4066 16 4538 675 742 48 LF386 85 NE599 140 UA810 170 6847 850 7485 38 74217 115 LS110 14 LS300 20 4067 16 4539 675 743 48 LF387 85 NE600 140 UA810 170 6847 850 7486 38 74218 115 LS111 14 LS301 20 4068 16 4540 675 744 48 LF388 85 NE601 140 UA810 170 6847 850 7487 38 74219 115 LS112 14 LS302 20 4069 16 4541 675 745 48 LF389 85 NE602 140 UA810 170 6847 850 7488 38 74220 115 LS113 14 LS303 20 4070 16 4542 675 746 48 LF390 85 NE603 140 UA810 170 6847 850 7489 38 74221 115 LS114 14 LS304 20 4071 16 4543 675 747 48 LF391 85 NE604 140 UA810 170 6847 850 7490 38 74222 115 LS115 14 LS305 20 4072 16 4544 675 748 48 LF392 85 NE605 140 UA810 170 6847 850 7491 38 74223 115 LS116 14 LS306 20 4073 16 4545 675 749 48 LF393 85 NE606 140 UA810 170 6847 850 7492 38 74224 115 LS117 14 LS307 20 4074 16 4546 675 750 48 LF394 85 NE607 140 UA810 170 6847 850 7493 38 74225 115 LS118 14 LS308 20 4075 16 4547 675 751 48 LF395 85 NE608 140 UA810 170 6847 850 7494 38 74226 115 LS119 14 LS309 20 4076 16 4548 675 752 48 LF396 85 NE609 140 UA810 170 6847 850 7495 38 74227 115 LS120 14 LS310 20 4077 16 4549 675 753 48 LF397 85 NE610 140 UA810 170 6847 850 7496 38 74228 115 LS121 14 LS311 20 4078 16 4550 675 754 48 LF398 85 NE611 140 UA810 170 6847 850 7497 38 74229 115 LS122 14 LS312 20 4079 16 4551 675 755 48 LF399 85 NE612 140 UA810 170 6847 850 7498 38 74230 115 LS123 14 LS313 20 4080 16 4552 675 756 48 LF400 85 NE613 140 UA810 170 6847 850 7499 38 74231 115 LS124 14 LS314 20 4081 16 4553 675 757 48 LF401 85 NE614 140 UA810 170 6847 850 7500 38 74232 115 LS125 14 LS315 20 4082 16 4554 675 758 48 LF402 85 NE615 140 UA810 170 6847 850 7501 38 74233 115 LS126 14 LS316 20 4083 16 4555 675 759 48 LF403 85 NE616 140 UA810 170 6847 850 7502 38 74234 115 LS127 14 LS317 20 4084 16 4556 675 760 48 LF404 85 NE617 140 UA810 170 6847 850 7503 38 74235 115 LS128 14 LS318 20 4085 16 4557 675 761 48 LF405 85 NE618 140 UA810 170 6847 850 7504 38 74236 115 LS129 14 LS319 20 4086 16 4558 675 762 48 LF406 85 NE619 140 UA810 170 6847 850 7505 38 74237 115 LS130 14 LS320 20 4087 16 4559 675 763 48 LF407 85 NE620 140 UA810 170 6847 850 7506 38 74238 115 LS131 14 LS321 20 4088 16 4560 675 764 48 LF408 85 NE621 140 UA810 170 6847 850 7507 38 74239 115 LS132 14 LS322 20 4089 16 4561 675 765 48 LF409 85 NE622 140 UA810 170 6847 850 7508 38 74240 115 LS133 14 LS323 20 4090 16 4562 675 766 48 LF410 85 NE623 140 UA810 170 6847 850 7509 38 74241 115 LS134 14 LS324 20 4091 16 4563 675 767 48 LF411 85 NE624 140 UA810 170 6847 850 7510 38 74242 115 LS135 14 LS325 20 4092 16 4564 675 768 48 LF412 85 NE625 140 UA810 170 6847 850 7511 38 74243 115 LS136 14 LS326 20 4093 16 4565 675 769 48 LF413 85 NE626 140 UA810 170 6847 850 7512 38 74244 115 LS137 14 LS327 20 4094 16 4566 675 770 48 LF414 85 NE627 140 UA810 170 6847 850 7513 38 74245 115 LS138 14 LS328 20 4095 16 4567 675 771 48 LF415 85 NE628 140 UA810 170 6847 850 7514 38 74246 115 LS139 14 LS329 20 4096 16 4568 675 772 48 LF416 85 NE629 140 UA810 170 6847 850 7515 38 74247 115 LS140 14 LS330 20 4097 16 4569 675 773 48 LF417 85 NE630 140 UA810 170 6847 850 7516 38 74248 115 LS141 14 LS331 20 4098 16 4570 675 774 48 LF418 85 NE631 140 UA810 170 6847 850 7517 38 74249 115 LS142 14 LS332 20 4099 16 4571 675 775 48 LF419 85 NE632 140 UA810 170 6847 850 7518 38 74250 115 LS143 14 LS333 20 4100 16 4572 675 776 48 LF420 85 NE633 140 UA810 170 6847 850 7519 38 74251 115 LS144 14 LS334 20 4101 16 4573 675 777 48 LF421 85 NE634 140 UA810 170 6847 850 7520 38 74252 115 LS145 14 LS335 20 4102 16 4574 675 778 48 LF422 85 NE635 140 UA810 170 6847 850 7521 38 74253 115 LS146 14 LS336 20 4103 16 4575 675 779 48 LF423 85 NE636 140 UA810 170 6847 850 7522 38 74254 115 LS147 14 LS337 20 4104 16 4576 675 780 48 LF424 85 NE637 140 UA810 170 6847 850 7523 38 74255 115 LS148 14 LS338 20 4105 16 4577 675 781 48 LF425 85 NE638 140 UA810 170 6847 850 7524 38 74256 115 LS149 14 LS339 20 4106 16 4578 675 782 48 LF426 85 NE639 140 UA810 170 6847 850 7525 38 74257 115 LS150 14 LS340 20 4107 16 4579 675 783 48 LF427 85 NE640 140 UA810 170 6847 850 7526 38 74258 115 LS151 14 LS341 20 4108 16 4580 675 784 48 LF428 85 NE641 140 UA810 170 6847 850 7527 38 74259 115 LS152 14 LS342 20 4109 16 4581 675 785 48 LF429 85 NE642 140 UA810 170 6847 850 7528 38 74260 115 LS153 14 LS343 20 4110 16 4582 675 786 48 LF430 85 NE643 140 UA810 170 6847 850 7529 38 74261 115 LS154 14 LS344 20 4111 16 4583 675 787 48 LF431 85 NE644 140 UA810 170 6847 850 7530 38 74262 115 LS155 14 LS345 20 4112 16 4584 675 788 48 LF432 85 NE645 140 UA810 170 6847 850 7531 38 74263 115 LS156 14 LS346 20 4113 16 4585 675 789 48 LF433 85 NE646 140 UA810 170 6847 850 7532 38 74264 115 LS157 14 LS347 20 4114 16 4586 675 790 48 LF434 85 NE647 140 UA810 170 6847 850 7533 38 74265 115 LS158 14 LS348 20 4115 16 4587 675 791 48 LF435 85 NE648 140 UA810 170 6847 850 7534 38 74266 115 LS159 14 LS349 20 4116 16 4588 675 792 48 LF436 85 NE649 140 UA810 170 6847 850 7535 38 74267 115 LS160 14 LS350 20 4117 16 4589 675 793 48 LF437 85 NE650 140 UA810 170 6847 850 7536 38 74268 115 LS161 14 LS351 20 4118 16 4590 675 794 48 LF438 85 NE651 140 UA810 170 6847 850 7537 38 74269 115 LS162 14 LS352 20 4119 16 4591 675 795 48 LF439 85 NE652 140 UA810 170 6847 850 7538 38 74270 115 LS163 14 LS353 20 4120 16 4592 675 796 48 LF440 85 NE653 140 UA810 170 6847 850 7539 38 74271 115 LS164 14 LS354 20 4121 16 4593 675 797 48 LF441 85 NE654 140 UA810 170 6847 850 7540 38 74272 115 LS165 14 LS355 20 4122 16 4594 675 798 48 LF442 85 NE655 140 UA810 170 6847 850 7541 38 74273 115 LS166 14 LS356 20 4123 16 4595 675 799 48 LF443 85 NE656 140 UA810 170 6847 850 7542 38 74274 115 LS167 14 LS357 20 4124 16 4596 675 800 48 LF444 85 NE657 140 UA810 170 6847 850 7543 38 74275 115 LS168 14 LS358 20 4125 16 4597 675 801

obtain the characteristics, then the routine for obtaining the hyperbolic functions from these values, and finally assembles these into the array.

This article concludes the computational algorithms used to obtain the results defining the performance of a complete network from the component values entered. The remaining articles will cover the use of these calculations, such as the entry of values, the outputting of results as a table of values and two curves showing the variation of amplitude and phase angle over the frequency range covered. It seemed time therefore to give preliminary details of the general arrangement, so that readers who desire to use some of them before the series is finished, may have some guidance along these lines.

In Fig. 5.3 is shown the general arrangement of sections by type throughout the suite, and will show the possibly perplexing reason why those sections already given show such a wide variation of line numbers. It seemed desirable to explain in some detail how each of the algorithms worked, one at a time, so that the assembly into a complete set could be followed without having to divert attention as to what each section was doing. It seemed desirable however to allocate discrete blocks of numbers to specific types of function, so that when assembled, it would not be a haphazard search to find any particular part of the overall computation which one wished to examine. The next article will cover input of values, since once this routine is entered, any of the algorithms may be immediately and quickly used by means of a custom-built temporary routine in section 8000.

For guidance, should this be done, and for future reference, Fig. 5.4 shows schematically, but not in detail, the general logic to be employed in the further development of this suite. In future articles the detail of the subroutine calling will be shown, but this is so involved that it could not be shown on a single sheet, and the figure is intended to show the overall logic employed.

For guidance to the do-it-yourself readers who desire to use some of these algorithms separately, a listing is given of a number of debugging and assembly routines which have been found temporarily useful in developing the program. Some of them will be included in modified form in the complete set of programs, but all those given here have proved of use at some stage or other of the development.

Those in the 6000 series were used to print out intermediate results when checking local performance, or when chasing a 'bug' and running it to earth. A GOTO or GOSUB statement is inserted in a gap in the program to divert the computation at the desired point. It can then be removed again when it has served

its purpose. The 7000 series is concerned with machine code and USR routines. 7000 through 7070 allows trouble to be investigated in a program which has been entered in basic. At areas where it is desired to know exactly what the state of memory is, a few REM statements are inserted at locations which are to be examined. The statements are coded to allow each of them to be individually recognised.


Typical codings are:- REM INPUT INPUT INPUT, or REM FOR FOR FOR etc etc. By entering as commands the values to be scanned as LET A1 = LET A2 = and then GOTO 7000 the computer will quickly scan the area until 234 is found, and will then run on SLOW sending out onto the screen a column of values following the 234. If the stop is at one of the markers, the 234 will be followed by three such as 238 which will allow the exact location to be found. After the screen is full, and the contents have been noted, enter CONT, further entries may be seen, but if a continuance of fast scan is desired to locate a further marker, enter LET MS = 0 followed by GOTO 7050.

The routine 7100 through 7150 is a quick and convenient way of entering a section of machine code, to be called later on USR. The values of A1 and A2 should be entered as before, followed by GOTO 7100. The number of the location currently at memory will be shown on the screen, and the computer will halt while value to be entered there is keyed in. It will then display the next location, and wait for the next value to be entered, and so throughout the area designated. If this is done in an area previously preserved by a REM statement at the beginning of the basic program, it will remain undisturbed during running, and may be addressed at will. ■

FIG. 5.3. Organisation of Computations within complete suite of programs.


Scope of coverage	Lines
Specification of general variables	1 - 99
Data input and sorting to appropriate sections	100 - 149
Control of program progression	150 - 999
Complex arithmetic	1000 - 1999
Impedances and Matrices Computation	2000 - 3999
Matrix manipulation	4000 - 4299
Output of results	4300 - 4999
Date Entry	5000 - 5999
Debugging routines	6000 - 6999
Machine code routines	7000 - 7999
Scratchpad for custom built controls	8000 - 8999

FIGURE 5.4 GENERAL LOGIC

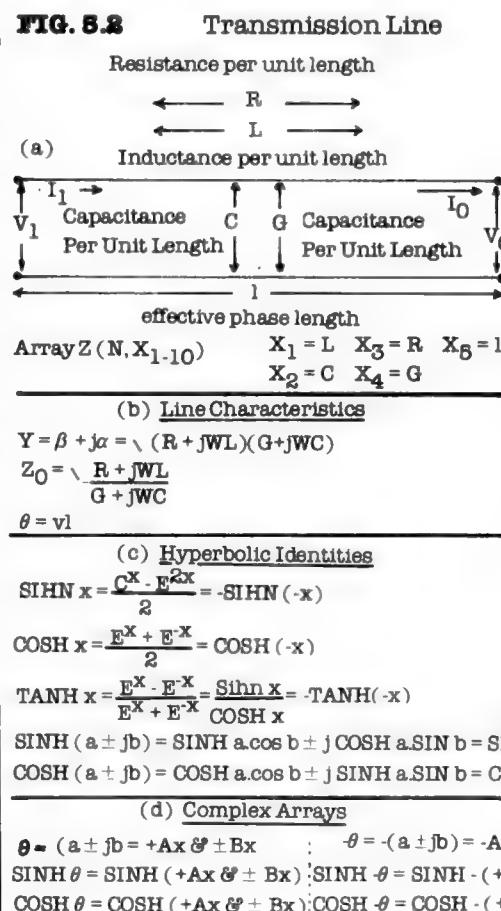

$$\begin{vmatrix} V_1 \\ I_1 \end{vmatrix} = \begin{vmatrix} \text{COSH } \theta & Z_0 \text{ SINH } \theta \\ Y_0 \text{ SINH } \theta & \text{COSH } \theta \end{vmatrix} \cdot \begin{vmatrix} -V_2 \\ I_2 \end{vmatrix}$$
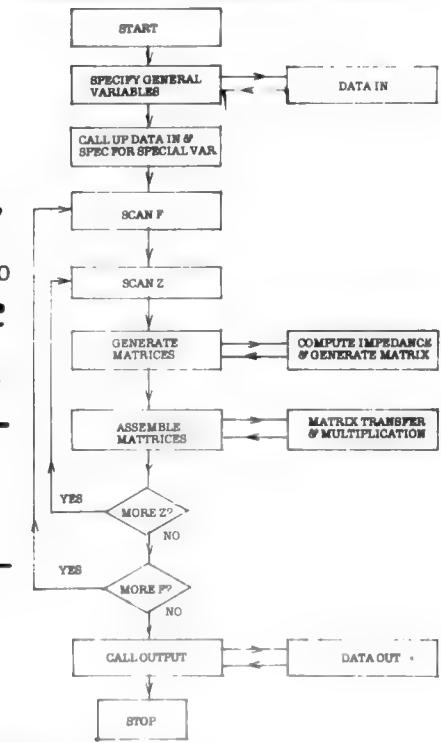
$$\begin{aligned} a_{11} &= \text{COSH } \theta \\ a_{12} &= Z_0 \text{ SIHN } \theta \\ a_{21} &= Y_0 \text{ SIHN } \theta \\ a_{22} &= \text{COSH } \theta \end{aligned}$$



Continued from Page 20.

the system has detected three consecutive pecks of the T-box it enters the data into storage. Figure 3 illustrates the insertion of three consecutive triplets of data values — in rows 1, 2 and 3 of the columnar tables.

Following the insertion of these sets of data the user has pecked the RESTART and RETRIEVE boxes in order to query the data base. Row 4 shows the entry of a single key (time=215) retrieval request followed by a two key search (temperature=163 and flow=368!). After the completion of the two retrieval transactions the user has returned to data insertion mode by pecking the RESTART and INSERT boxes. A further triplet of data values (0450, 139, 4463) is then entered into the data store.

Based upon what has been said above it is possible to summarise the data entry protocols as follows:

(A) Insertion
 <time-value>[T]<temperature-value>[T]
 <flow-value>[T]

(B) Retrieval
 <search-key>[T]<null-key>[T]
 <search-key-1>[T]<search-key-2>[T]

in which the variables enclosed in angular brackets represent decimal strings created by character stroking operations and [T] denotes a single peck of the T-box. The software in the host has the responsibility of checking that the sequence of characters that it receives from the hand print terminal actually constitute a valid transaction type — as defined by the above allowed protocols. It does this by (1) checking that the values are all numeric, and, (2) ensuring that they are all written in their correct places on the data capture document.

When designing algorithms for the software that will reside in the host computer two important tools are often used: state graphs and touch tables. The state graph (shown in figure 6A) reflects the way in which different parts of the software take control as a result of the various symbols written and pecks made by the operator on the surface of the document. As was indicated above, initially, the system resides in the transaction selection state. It passes out of this state only as a result of a peck directed at one of the option boxes in the horizontal menu. It returns to this state only as a result of a RESTART peck or for entry of a new document. The other two major states are insert and retrieve. From either of these states the system can pass into an associated field entry state. This happens as a result of the user writing a decimal digit at an appropriate place on the data capture document. The system remains in field entry mode until the terminate transaction box is touched. A return is then made to the parent insert/retrieve state. This enables

the value captured during field entry to be entered into the data base (DB) buffer. The system then returns to field entry mode. Should the context of field entry to be insert, then, if the sum of the T-pecks is a multiple of three, the DB insertion state is visited. This now allows the data base to be updated. Similarly, if the context of field entry is retrieve mode and the sum of the T-pecks is a multiple of two, the DB retrieve node takes control in order to search the data base thereby obtaining the information required by the terminal operator.

The touch table (illustrated in figure 6B) is used to define those areas of the document that the software must respond to when pecked or written on. Essentially, this table consists of a listing of all the names of the fields contained in the document being serviced. Associated with each name there is a series of values that define the position (row and column) at which the corresponding field occurs on the data capture form. For example, the INSERT box is positioned in row 1, column 30 of the document; the TEMP table commences in column 12 for each of rows 4 through 15; the T-box starts in column 30 for each of rows 15 and 16. In addition to specifying position data, field widths, data type, transaction type and order of entry may also be specified.

Once the state graph and touch table have been constructed, the formulation of algorithms to service the document becomes a simple matter. Algorithms for this case study are presented in pseudo-code form in figure 7. Getchar is a primitive input routine. When invoked it assigns values to the variables R (row number), C (column number) and A (ASCII value). These values correspond to those sent from the terminal for the last character written on its surface. The wait routine simply halts execution of the program for the period of time specified by its single argument. Isin is a primitive set membership operator that checks whether its left hand operand (an element value) is a member of the set specified as its right hand argument. Thus, the statement A isin[A .. 9] simply checks that the value of A lies in the range defined by the subset of the natural numbers 0 through 9.

In the algorithms presented in figure 7, step 6 is responsible for detecting a valid transaction selection peck. Step 7 then handles data insertion operations while step 8 specifies the actions to be taken in order to service a retrieval request. Notice that during an insertion transaction the order of field entry is dictated by the control software. On the other hand, when the system is operating in retrieval mode the order of field entry is user driven.

Algorithms of the type depicted in figure 7 are easily coded — manually or automatically — into either a high level language (such as BASIC, PASCAL or PL/I) or machine code, depending upon the response time required. We have programmed these algorithms using BASIC and have found them to work quite satisfactorily.

CONCLUSION

Electronic hardware and software technologies can be combined to produce a variety of novel machine interaction devices. These can often be employed to (1) realise many end-user applications of computer systems that might otherwise not be possible, and (2) provide new ways of enabling people to communicate with a computer. The hand print terminal is an example of an intelligent input device that allows human-machine interaction to be conducted through the medium of printed messages or by means of menu selection. In the latter case this is most easily accomplished through the use of pecking operations. Peripherals of this type are likely to offer many attractions to those who prefer not to use a keyboard or keypad device as their mechanism for computer data input. Several terminals of this type are now available commercially. Two examples are cited in the bibliography.

BIBLIOGRAPHY

- [1] Image Data Products Limited, 1-4 Portland Square, Bristol BS2 8RR, Technical Specifications for the Image Data Tablet.
- [2] Micropad Limited, 10 Whittle Road, Wimbourne, Dorset, BH21 7SD, Technical Specifications for the Micropad Hand Print Terminal.
- [3] P G Barker, The Magic of Touch, Interactive Systems Research Group Working Paper, March 1982.
- [4] P G Barker, Data Base Interaction Using a Hand Print Terminal, International Journal of Man-Machine Studies, in press, 1982.
- [5] K Ikeda, T Yamamura, Y Mitamura, S Fujiwara, Y Tominaga and T Kiyono, On-line Recognition of Hand-Written Characters Utilising Positional and Stroke Vector Sequences, PATTERN RECOGNITION, Volume 13, No. 3, 191-206, 1981.

16 BIT'ers

The trend towards 16 bit machines is now very firmly on and within 12 months the 8 bit micro, certainly in the commercial environment, is going to look as old hat as yesterdays 4 bit models. Does anyone remember 4 bit microprocessors even. At this years ONLINE show at Wembley the ACT Sirius again stole the show although there are now some other excellent 16 bit machines coming onto the market and Sirius could face some stiff competition in the coming months. The Almarc-Vector Graphic 8 16 bit model in particular can run existing 8 Bit CP M software (software availability is going to remain a big problem for 16 bit machines for another 12 months yet) and 16 bit as it becomes available. In addition it offers a 5 Megabyte Winchester plus 630K of floppy for about the same price as the Sirius. Don't phone me phone David Swain at Almarc.

WRIST COMPUTER

I was looking at the specification for a rather remarkable digital watch the other day: perhaps wrist computer is a better description for this little wonder.

Only 10mm thick it not only has time, day and date, but a stopwatch and an alarm which actually speaks to you. In a rather tinny but clear voice it reminds you that you didn't get up the first time the alarm went off, and that you really must get out of bed.

It made me realise how close a genuine home computer, the size of a digital watch really is. The display should be no problem, since alphanumeric displays capable of displaying rows of tiny characters, and even crude graphics already exist on digital watches. The chips themselves are no bigger than your little finger nail, and using CMOS technology (big microprocessor chips are already available in CMOS) a lithium battery should have no problems keeping the thing powered continuously for at least a year.

Only the keyboard is a problem, and this problem could be solved with the advent of voice recognition chips within the next few years. Circuits which are capable of recognising simple Basic computer language instructions, such as *PRINT*, *INPUT*, *GOTO*, *RUN* etc plus alphanumerics and a limited range of file names should present no real problems within the next couple of years. 256 spoken sounds should well cover it, and probably much

less. Data files not in main memory could be held on a miniature pocket tape recorder or even a bubble memory pack. Later versions could even dispense with or augment the display with the rather tinny synthetic voice circuit which started off this speculation in the first place.

What would anyone do with a wrist computer?

Well that depends as now on the amount of on-board memory, but since RAM memory prices continue to fall, and capacity increases dramatically, this could be even less of a problem than with present home computers. A wrist computer could have practical applications as a memory aide and portable look-up store. Certainly as a highly sophisticated and intelligent calculator and even to play quiz games on as you drive along. It could even tell you the time.

HOME COMPUTER SALES

This is not meant to appear as gloom doom etc., but I now know of 4 home computer shops who are losing money heavily because sales are so poor. One is discreetly on the market looking for a buyer. Two are being propped up by rich sugar daddies (one of them literally) and the other is in imminent danger of closing down. 4 is too small a sample to draw any real conclusions from I know, but with information I hear at exhibitions and trade shows (all in strict confidence, you understand) it really does seem that the recession is still biting hard. People are not exactly rushing out to buy the latest space invaders with real sound etc. Only Sinclair can do no wrong, and perhaps he is responsible for mopping up the sales which would otherwise have gone to the computer shops. With a reputed population now standing at 400,000 in the UK the ZX81 must be having quite an effect on home computer sales in this country.

MAGNETIC DATA STORAGE

For densities as high as 200,000 bits per inch on a floppy disc the next technological step is likely to be 'Vertical Recording'. With this technique the magnetised areas of the medium are orientated vertically

instead of parallel to the surface. Research is going on in the United States and Europe but instead of catching up from the rear the Japanese, this time are unquestionably in the lead.

It is still not clear just how much density can be achieved through vertical recording techniques and some of the first products will be floppies with a conservative density of 20,000 to 40,000 per inch, compared to about 10,000 per inch today.

However, densities of 80,000 to 100,000 have been demonstrated in the labs and such products could follow quickly, with 200,000 tracks per inch being a follow on.

In the USA, Vertimag may soon be offering 5-megabyte 5 inch floppy discs using vertical recording techniques. It is announced that delivery of the system will be in mid to late 1983 at an expected price of \$500 each in quantity, for the drives with discs at \$25 each.

It looks like the floppy disc is going to be with us a little longer yet.

**Remember
to ask
your
newsagent
for**
**Electronics
&
Computing
Monthly**

NEWLINE

16K for ZX81



3 Card Brag: The '81 plays, shuffles and deals like a real card sharp . . . can you play better than 'him'?

SUPERB Graphics – only £5.50



Craps: The Tumbling Dice game for up to four players. Roll them cubes and see how your luck is. Full graphics – yours for £3.95



Poker Dice/Pontoon: Both games on one cassette. Yet again we give you full graphic displays with great layout.

Cassettes: £3.50 each

Please make cheques/P.O.'s payable to: NEWLINE, and send to:- NEWLINE, 8 EWELL ROAD, WOLLATON, NOTTINGHAM NG8 2DE.

We at NEWLINE are so pleased with the results of our tapes, having found that they are ideally suited for the computing machine, that we are offering them at a bargain price so you may judge for yourself their quality.

**FOR A 3-pack OF BLANK CASSETTES —
ONLY £1.00**

For **ANY** order over £8.00 then you will receive a free blank cassette.

OFFER CLOSES: August 31st 1982!

Please tick which program required:-

BRAG CRAPS PONTOON/P.DICE

Name

Address

..... P/Code

If blank tapes wanted, state no. pks.



**Business & Leisure
Micro Computers**

16, The Square,
Kenilworth.
CV8 1EB.

SHARP

have done it again!

MZ80A £549.00 inc. vat

This magnificent machine comes complete with a software pack including GAMES — HOME FINANCE — EDUCATION — BASIC TUTORIAL This streamline all-in-one unit with the SHARP reputation for reliability has to be the one for **YOU!**

**Visit us now for a demonstration —
ring Kenilworth (0926) 512127**



WE ARE LOOKING FOR NEW
SOFTWARE AND WILL PAY TOP
MONEY FOR "UNUSUAL", "FUN" AND
"EDUCATIONAL" PROGRAMS AND
GAMES

 **COMPUTERS**

 **COMPUTERS**

All submissions will give the programmers 5%
discount on all future software.

All software must be on tape and accompanied by
instructions.

PHONE WALSALL 641772
or write to
No. 4 CANUTE CLOSE, HIGHGATE ROAD
WALSALL, WEST MIDLANDS



MICROFEST '82

Micro Fair and Seminar for all users
HARDWARE. SOFTWARE. PERIPHERALS.

ADMISSION

ADULT

CHILD (under 16)

(half price with coupon)

1.00

50p

Exhibition and other diversions for ZX, B.B.C. Micro, VIC, TRS, Sharp, Sorcerer, Video Genie, Tangerine, Nascom, Atari, Pet and Acorn user

- 10 Free draw for MICRO computer
- 20 Club Stands
- 30 Bring and Buy stall
- 40 Free parking
- 50 Review of Sinclair Spectrum
- 60 Lectures on small micro applications
- 70 Free Films
- 80 Bar and refreshments
- 90 Close to centre and Piccadilly station
- 100 Free Coffee
- 110 Facilities for the Disabled



UNIVERSITY OF MANCHESTER INSTITUTE OF SCIENCE AND TECHNOLOGY, SACKVILLE ST., MANCHESTER.

SATURDAY 24 10.30 - 21.00
SUNDAY 25 10.30 - 18.00 JULY 1982.

GRIMER

24 GLOUCESTER ROAD
BRIGHTON
Tel: 0273-698424

**EXPANDED ATARIS AT
LOW PRICES!**

ATARI 400 — 16K £260.00
— 32K £320.00

ATARI 800 — 16K £499.00
— 32K £539.00
— 48K £579.00



SHARP MZ-80A

Package including:


- 10 Games
- Educational
- Home Finance
- Basic Tutorial

Plus

'DATAFILE'
(Flexible Cassette Database)

£477

Phone for details of other packages

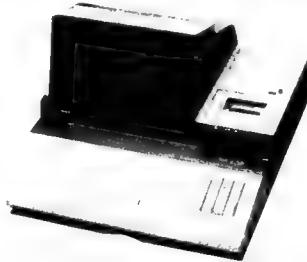

Also in stock —

VIC 20

ATOM

GENIE

TEXAS

MZ-80B

- Books, Accessories and Peripherals
- Software for ZX81 & BBC

Please add 15% VAT

Delivery Free

DIMMER CIRCUIT

by Harry Fairhead

Extensions to the range of kits available to the amateur are always to be welcomed so I was pleased to come across the range of kits produced by Velleman, a relative newcomer to the UK market. To retail kits successfully, a manufacturer needs to have as large a market as possible. In the United States there are some very large and highly successful organisations on the electronic kits scene — take Heathkit as a prime example — but in this country we have no real equivalent simply because the market is not big enough. It is therefore particularly heartening to find a European based company — Velleman is a Belgian firm — operating over a number of countries rather than confining itself to a single one.

Being an already established company, Velleman can offer an extensive range of kits and there are fifty items on its recent list which vary in price from under £5 to over £200. They are graded into three levels of difficulty. Those at grade 1 are intended for "the beginner with some soldering experience and the understanding of the external characteristics of the most common components". To assemble those at the next level "demands good soldering experience together with a reasonable knowledge of electronics" while those at difficulty grade 3 are mainly intended for professional use and require "perfect soldering technique".

One of the interests of sending for any technical equipment originating from another country is to read the documentation translated from a foreign language. These kits are no exception — the instructions caused me to smile and chuckle on numerous occasions. The odd usage of English causes you to ponder over some of the instructions but they do make sense if you persevere.

Confining my attention to the amateur kits in the first instance but still faced with a wide choice of kits, ranging from amplifiers to a lighting effects computer, I decided to start by picking one of difficulty grade 1 to discover how those of you less experienced at constructional projects would fare if you sent away for a Velleman kit.

My eye was originally drawn to the Dimmer circuit because of the unfamiliar term "Deparasite" printed in brackets beside it — this turns out simply to mean "suppressed" — but I decided it was a good choice because it is a popular and universally useful one. Most people can find a use for an extra dimmer but as this one can control 1000 Watts its more suitable as a master dimmer for a number of lights, a small electric fire controller or an electric drill speed controller.

Over the years, many designs for thyristor dimmer circuits have been published but because a dimmer circuit involves the mains supply beginners often look for a kit. It means that the quality of the kit is particularly relevant — a mistake could prove FATAL. I was therefore concerned to examine the kit in terms of its ease of assembly and from the point of view

of safety. In the instructions the following warning is printed,

"All the parts of the dimmer are at the mains potential and to touch them is extremely dangerous. As this kit was designed for people having some experience in electronics, we presume that people will take all the necessary insulating rules for a safe usage".

Personally, I thought that this warning was a rather poor substitute for spelling out the essential precautions, considering that this kit is in the lowest grade of difficulty.




Complete Dimmer Heat Sink.

My kit came with a printed sheet giving instructions in Flemish, French and German and a typewritten sheet giving an English translation. The manufacturers are in the process of preparing new documentation but in any case all the information given currently in the other languages appears to be included in the English sheet — there is one extra piece of information given in English on the printed sheet, namely advice about how to return a non-functioning kit to the manufacturer for attention — but the two kits I've looked at worked perfectly so it is to be hoped that that advice will not need to be followed too often.

The PCB for the dimmer measures 10cms by 5cms and is single sided. All the component positions have been silk screen printed on the top side, making assembly particularly easy. The parts comprise: 1 triac, 4 diodes, 1 diac, 2 condensers, 1 trimmer, 4 resistors, 1 "cooling fin" (i.e. heat sink) and 6 pins — whose purpose is nowhere explained but intended to be inserted into the holes in the PCB where external wires are to be connected. Specific to the "Parasitic" dimmer — which is rather more than twice as expensive as the basic dimmer — is a toroidal coil and an extra condenser which serve to suppress switching noise — rather charmingly translated from the original as "the hysteresis effect". With this number of components even a relatively inexperienced kit builder could expect to complete assembly in a couple of hours or less. Included with the documentation there is a parts identification chart. This is standard to a wide range of kits so components that do not actually occur in the dimmer kit appear on it, which might be just a little misleading. However, the diagrams are particularly clear which make component identification easy. A niggling criticism of the components list was that the colour coding of the various resistors was not included alongside their values in the list — this information is given instead in the section headed "Construction".

The instructions about construction are a simple list of operations with no additional detail to explain each step. There is a rather difficult, and misleading, instruction about the heat sink ("cooling fin"). We are asked to ensure that it does not touch the triac. This is of course quite impossible — for the heat sink to work it must touch the triac — and presumably what the instruction means is that it must not touch the pins of the triac. Moreover, the instructions do not give any guidance as to which way round to mount the heat sink and this is crucial. There is only one way it can be mounted in order not to foul the small variable resistor — the correct way appears to be so that the heat sink hangs over the edge of the board (see photograph).

In the kit I built there appeared to be two missing components. The first was a nut and bolt to hold the heat sink under the triac. Luckily this was easily provided from my tool box. The second was any way of securing the large suppressor coil on the far end of the board. The silk screen diagram indicates a nut that would be tightened to hold it in place. In the absence of any such component the coil hangs on the PCB simply by the two wires which it is connected to. This does not make it inoperable — if the circuit is mounted in a box and is not going to be subject to much movement the loose connections will probably suffice and if a more secure fastening is required, glue or masking tape could be used to secure it.

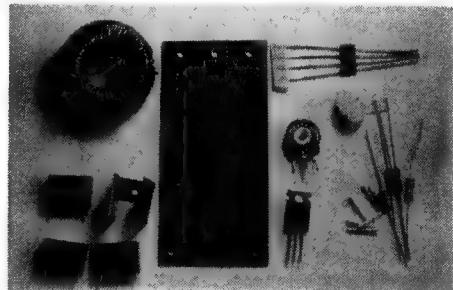

Components for Dimmer

Velleman do not provide the actual potentiometer to control the output claiming that the range of applications is so great that each user would need to choose either a miniature, a normal 6mm or a slider potentiometer according to the particular purpose intended. I think that this argument is slightly weak and that they could in fact provide a 1 Mohm standard miniature potentiometer which would suffice for 90 percent of applications. It is a bit frustrating not being able to test the kit once you've built it unless you've had the foresight to purchase a potentiometer.


On the subject of testing it is important to remember that the printed circuit board carries mains voltages that are unbuffered by a transformer. If you make the mistake of holding the circuit in your hand while testing it is unlikely that you will ever build another circuit! To test and use the circuit safely it is important that you mount it in a fully enclosed earthed metal or plastic box. Use a mains supply with a five amp fuse and do not disturb the circuit unless you disconnect it from the supply.

The list price of the 1000 Watt Dimmer is £5.59 and 1000 Watt Dimmer (Deparasite) is £12.64. A complete catalogue is available from Velleman UK, P.O. Box 30, St. Leonards-on-Sea, East Sussex TN3L 7NL.


FULLER FD SYSTEM FOR ZX80/81

THE MOST VERSATILE SYSTEM FOR EXPANDING YOUR ZX

STANDARD KEYBOARD AND CASE

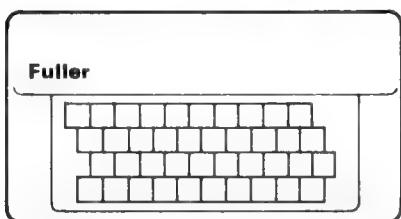

EXTENDED KEYBOARD AND CASE

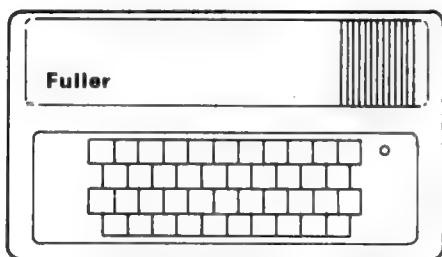

Keyboard Only Available!

Built £24.95

Kit £18.95 (+P.P. 80p)

This splendid keyboard and case houses your ZX81 printed circuit board, which is simply screwed into place, the keyboard plugs into the ZX. You can now enter data with ease. The 40 key switch board is a custom unit not made up out of other manufacturers parts. The keytops are our own design and have the ZX Qwerty and functions foil printed onto them. Access to the user port, TV, MIC, and ear sockets are as per the ZX case.

Built keyboard and case £36.70 or £30.70 as a kit plus £2.10 postage and packing.

The case is designed to house not only the keyboard and ZX but also our motherboard, power supply, RAM cards and two other boards, not necessarily of our manufacture. The injection moulded case measures 200 mm x 350 mm x 60 mm and houses a 42 keyswitch board, the extra keys can be assigned to other functions. The case is supplied with a "Power On" LED.

Built keyboard and case £39.95 or kit £33.95 plus £2.50 postage and packing. Motherboards £15.95 plus 80p postage and packing. 16k RAM board £35.95. 64k RAM board £79.95.

Send SAE for details to:-

FULLER MICRO SYSTEMS, The ZX Centre,
Sweeting Street, Liverpool 2.
Telephone: 051-236 6109

chrisalid -

EPSON MX80

You won't find lower prices
ANYWHERE!!!


MX80t £315 / MX80ft1 £355 / MX80ft2 £355

genie 1 & 2 HUGE
DISCOUNTS

ACORN Atom TO **EPSON** interface - COMPLETE

NASCOM 2 kit £220 built £280

BERKHAMSTED'S COMPUTER CENTRE

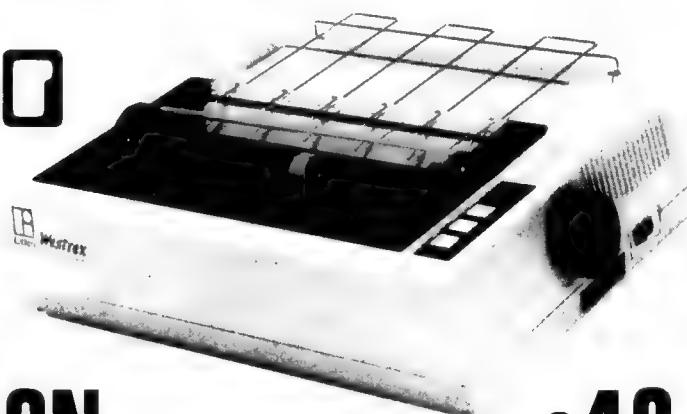

**£40
IN STOCK
£399**

micro-ed

CUMANA twin 40 track drive · *genie* / trs80 £370

Barclaycard Access & Phoned Orders Welcome

ALL PRICES EXCLUDE VAT 15%

13 High Street Berkhamsted Herts TEL: (04427) 5704 and
24569

PROGRAM POWER PROGRAM POWER

PROGRAM

Quality Acorn ATOM & BBC MICRO
SOFTWARE from

PROGRAM POWER


PROGRAM POWER



CHESS (12K)

Improved graphics, plays black or white, mid game level changes, look ahead up to 8 moves, offensive, normal & defensive play, 10 sub levels, castling, 'En passant' by player. Rejects illegal moves. Take back moves & action replay with take over. Set up problem games.


£7.95

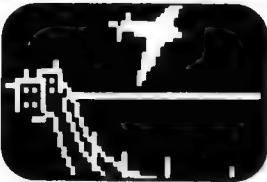

AIR ATTACK (12K)

Command an East Coast anti-aircraft battery. Destroy enemy fighters, bombers and doodle-bugs. Ingenious graphics depict planes approaching, veering and flying off. Search the sky and scan the landscape through 360 degs. GOOD SOUND. GREAT ENTERTAINMENT


£7.95

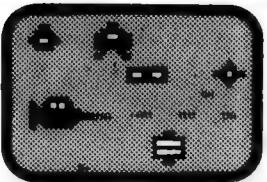

SPACE FIGHTER (6K + 3Kgr)

Super High speed "Defender" game. 5 types of intelligent aliens. Repeating laser cannon, smart bombs, hi-score, rankings, bonus points. 6 skill levels. Exciting sound effects.

£7.95

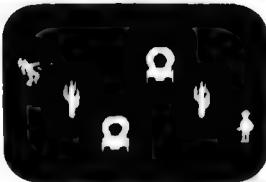

COWBOY SHOOT-OUT (12K)

Full feature, two player, arcade shooting game. Cactus plants, wagons, animated cowboys. Superb graphics and sound £8.95

PROGRAMMER'S TOOLBOX

(PACKED 4K EPROM) £24.50

- ★ 1200 BAUD CASSETTE OPERATING SYSTEM
- ★ VISIBLE LOAD & SAVE

• TRACE (X)	READ
• ITRACE	DATA
• STEP	RESTORE
FIND	LIST
VAR	WHILE
LVAR	ENDWHILE
DELETE X, Y DUMP	

ON ERROR	HEX
BNUMBER X Y	OFF
AUTO X, Y	VICTIM
CURSOR X, Y	ZERO
BEEP X, Y	POP
KEY X	STOP
INKEY \$X	

• VIA chip required
Suitable for 400K memory

1000
ATOM USERS
CAN'T BE
WRONG!

Now available from many Atom Dealers.

ROM SELECTOR BOARD

Suffering from congestion? (PROGRAMMER'S TOOLBOX, WORD PROCESSOR etc.) Switch between up to 4 ROMS located at Hex A000. Assembled and tested unit with compact, professionally produced PCB and good quality components. Fits easily into the Utility Socket (IC 24). Only £19.50

Adventure

ALL THE EXCITEMENT, INTRIGUE AND FRUSTRATION

OF A MAIN-FRAME ADVENTURE! 12K

Explore the tortuous forests, dark caverns & castle dungeons. Beware the maze of twisting tunnels and the desert wastelands. Outwit the predators. Rescue the PRINCESS and carry off the treasures.

Great skill & imagination are required to play this excellent game & you may still never exhaust all the possibilities.

By devising methods of condensing messages, the author has been able to include many features which would otherwise be available only on much larger computers. Start your adventure now - £7.95

ATOM SPECIAL OFFER

Deduct £1 per cassette when ordering TWO or more.

WRITTEN ANY PROGRAMS!
WE PAY 20% ROYALTIES
FOR ATOM, NASCOM &
BBC MICRO PROGRAMS

BBC

Special Offer

EXTENDED TO

31st JULY — SAVE £££'s

We are giving Fabulous discounts on all our BBC MICRO Programs
IF YOU BUY NOW.

CHESS (£7.95) now £4.95.

STAR TREK (£7.95) now £4.95. MUNCHYMAN, DISASSEMBLER & SPACE MAZE (£5.95); Now

£3.95 GOMOKU (£3.95) now £2.95

Please add 50p order P & P + VAT at 15%
MICRO POWER LTD.
8 & REGENCY STREET,
LEEDS LS7 4PE.
Tel. [0532] 683186

PROGRAM POWER PROGRAM POWER

THE MATHS BOX

Incorporating LEICESTER TYPEWRITER Co. Ltd.

RECESSION



...Survival of the fittest!

It is a frightening but simple fact that in twelve months time, many of today's companies will be in liquidation. Every day brings news of more redundancies, more closures, more short time – even from firms with household names. But why and who will be next?

Who's next?

Every businessman knows why – it's the old law of supply and demand – the main question is – Who's next?



With a smaller market firms automatically look for sales over a wider area and sell at even more competitive prices. But that is not enough!


In these highly competitive times, immediate access to accounts information, stock movement and control and profitability analysis is essential to enable your decision makers to predict losses before they occur and encourage sales of more profitable lines.

Be honest. Do you know the exact value of your company at today's close of business? Are all your lines or services profitable? What is the real value of customers who expect discounts and extended credit? Do your prices include all the recent increases in raw materials, labour, petrol etc., etc? If you only think you know the answers then the simple truth is that you probably don't!

What's the answer?

To be frank there is no simple solution but immediate access to information is essential. At The Maths Box we have a highly skilled team who really understand the complexities of the latest generation of microcomputers and would be pleased to sit and discuss your individual requirements. We will carry out a diagnosis on your problem. What have you got to lose? We have a ready made range of systems for first time buyers or can supply custom made units for more detailed problems. Personal leasing facilities are even available and we offer an after sales service that we believe is second to none.

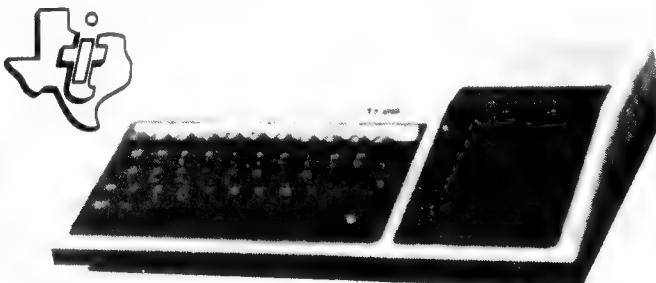With so much at stake, isn't it worth an hour of your time to come, look and evaluate the benefits for yourself?



The TI-99/4A is a sophisticated computer, ideal for the beginner, with its ease of operation, but powerful enough to satisfy the needs of the professional enthusiast. With a combined RAM/ROM capacity of up to 110K byte and a full range of peripherals and software, your Home Computer can grow as your knowledge of computers increases.

With over 600 programs available worldwide, including more than 40 on easy-to-use Solid State Software (RI) modules, the Texas Instruments Home Computer system is as versatile as you are.

So why not check out the winning combination of Texas Instruments' high technology and value for money now – you can't go wrong.

WRITE, VISIT OR PHONE US TODAY


112 EAST STREET, SOUTHAMPTON
Tel: Southampton 24703

SHARP 1st & FOREMOST

MZ80A 48K PERSONAL COMPUTER



£546

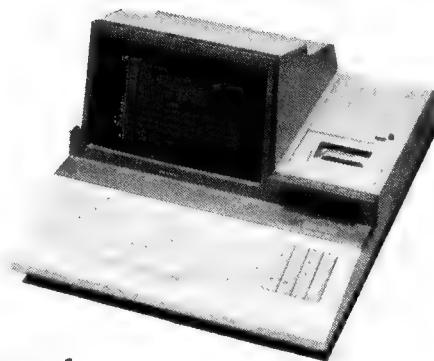

Full range of software available

W.B. COMPUTER SERVICES LTD

**11 ALDERGATE,
TAMWORTH, STAFFS.
0827 55937**

ZX81 QUALITY SOFTWARE FOR THE SERIOUS USER

VIDEO - INDEX
Build your own index of up to 1000 entries on your 16K ZX81

- Designed specifically for the ZX81.
- Over 1000 references possible in 16K RAM.
- Up to 57 characters of text generated for each reference.
- Ingenious machine coded encryption technique.
- Fast and powerful machine coded search procedure.
- Minimum keystroke data entry procedure.
- Menu driven, easy to operate and crash proofed.
- Documented to the usual high Video Software standard.
- Includes demonstration index of ZX812 magazine references.

This is probably the best serious program yet written for the ZX81 and is available from good software retailers or by mail order direct from ourselves.



VIDEO
SOFTWARE LIMITED

PRICE £9.95 inc. VAT
Plus £1.00 p. & p.
Send large SAE for our full catalogue of software products.

Personal callers welcome during office hours Send s.a.e. for further details

In May I reviewed a rather dated book concerning computers and amateur radio. Since then I've found a new and well written book on the same topic.

Computers and the Radio Amateur

by Phil Anderson, 208 pages, £14.20.

Published by Prentice/Hall International.


This hard-back book was written by Phil Anderson, an American radio amateur — call sign WOX1. It starts off by presenting a very exciting prospect — the computer is seen not only as a Morse code keyer and reader but also for "CW voice", the idea being that you put a speech synthesiser in the computer and transmit codes that cause speech to be output. The last section of Chapter One suggests that the hams' ideal is a completely automated station with CQ search scanning, automatic QSO machines — it almost suggests that you can switch your radio on and leave the computer in charge to carry out the entire exchange! The next few chapters cover a general introduction to computers, programming and logic. Chapter Seven is about interfacing, in particular how to interface amateur radio equipment. It is at this point that Phil Anderson starts to give practical advice and information to actually put into reality some of the ideas presented at the beginning of the book. The remaining five chapters each present a project using the TRS-80. Chapter Eight gives constructional and software details about a computer morse keyer. Chapter Nine complements this by giving a random code generator for morse practice — again complete with program listing. The next chapter demonstrates how the computer can be used as an automatic morse code reader, including a program and hardware details of the interface. Next comes a software project to enable a computer to be used to administrate radio amateur competitions in the U.S.A. Finally there are some fairly standard programs, for example, calculating the size of a dipole, or the number of turns you need on a coil, which give an idea of the ways in which a computer can be used to do standard ham/electronics calculations.

I found the first chapter of the book really exciting but current technology meant that only the less interesting projects could be developed in the practical sections later.

How to Use Op Amps

by E.A. Parr, 154 pages, £2.25.

Published by Bernard Babani.

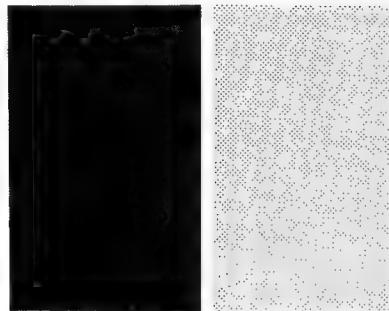

This is one of the very latest books to be published and is a really worthwhile addition to the electronics bookshelf. It presents a mixture of the theory of operational amplifiers and examples of practical applications which are of interest in themselves and are clearly illustrated with well drawn diagrams. The first two chapters are about theory and basic circuits. Chapters Three to Six are about practical applications including oscillators, audio circuits and filters. Chapter Seven comprises a short but useful reference section of extracts from data sheets about the most commonly occurring op amps. Chapter Eight contains a number of circuits suitable for powering op amps and the final chapter is an extremely short one on fault finding and constructional techniques.

The subject of op amp design is usually dealt with in more theoretical terms by books costing a lot more than this one — so all in all this book is likely to be considered very good value.

STOP PRESS

As the months go by I'm accumulating lots of books I want to tell you about and I've realised that I'll never get to the bottom of the pile if I give them all a proper review. So I'm going to mention a few of the most recent ones briefly and hope that you'll be able to find them in your local bookshops to discover more about them for yourselves.

First on my list is a book by Mike James whose name will be familiar to regular readers of E&C Monthly. It's "THE 6809 COMPANION" a reference work that will be invaluable to anyone interested in the 6809 microprocessor, which is becoming increasingly important and popular. The book covers all the topics needed in a machine companion and includes a fully commented instruction set. The chapter on

how to convert programs from 6800 code which will be particularly welcomed by anyone upgrading to the 6809 from a 6800. Published by Bernard Babani, this book costs £1.95.

There are another two recent titles from the same publisher that might interest those of you keen on constructional electronics. The first is "IC PROJECTS FOR BEGINNERS" by F.G. Rayer, price £1.95, which presents a number of circuits with their stripboard layouts. The second is "POPULAR ELECTRONICS CIRCUITS BOOK 2" by R A PENFOLD, price £2.25, which is a collection ranging from amplifiers and test gear to radios, including over 70 practical circuit diagrams giving component values — no layouts are given.

Among the new titles for the ZX-81 is one that stands out for being extremely nicely produced. It is an introductory volume for the 1K machine with details of how to get the machine up and running as well as plenty of programs. By Ian Stewart and Robin Jones it is entitled "PEEK, POKE, BYTE & RAM" and is published by Shiva at £5.95. This book takes a very light-hearted approach to the subject but while I was occasionally irritated by the style of the text I was always amused by the cartoons.

THE EXPLORERS GUIDE TO THE ZX81 — Mike Lord Timedata.

This is a well presented and interesting book which is not intended to be a beginners guide to either Basic or the ZX81, but carries on where the ZX81 Basic Manual leaves off.

Chapter 1 is concerned with saving space, other Basics and gives hints on how to use some of the functions of the ZX81.

Chapter 2 contains a range of games and novelty programs. Brief explanations of how the programs work are given and suggestions are made as to how the reader could modify them.

Chapter 3 deals with applications which put the ZX81 to work in a more serious capacity, and gives some useful programs.

Chapter 4 gives an insight into machine language, giving explanations of what it is and its uses. Some programs illustrating machine code are given at the end of the chapter.

Chapter 5 covers the ROM explaining its more important functions, ROM tables, Load and Save, Display and keyboard scanning.

Chapter 6 contains many useful hints on improving the ZX81 hardware, dealing with known problems, and in some cases giving circuits which will overcome them. I did not try all the programs in the book, but those I did try worked.

MICROWARE

Retail Shop in **LEICESTER**
 Home Computer Accessories
 Essentially for **SINCLAIR** Computers

See our ever
 changing and
 increasing display
 of **ZX81** software

Note - Holiday Closing
 The shop will be closed
 Tues. 29th June
 Wed. 30th June
 Tues. 6th July
 Wed. 7th July

OPEN Mon., Fri., Sat.
 these weeks

Hardware, Software,
 Books, Periodicals, Monitors, etc.

Games, Serious, Educational and
 Business Programs.

Coming soon:
 Software and
 Books for

ZX SPECTRUM

BBC
VIC 20

Also VIC 20
 RAM Packs

S.A.E. brings
 catalogue

MICROWARE
131 MELTON ROAD,
LEICESTER

Tel: 0533 681812

OPEN 9.30 - 5.30 CLOSED Thursdays

MICROWARE **MICROWARE**

SHARP

*MZ80A — 48K Personal Computer	£477
MZ80B — 64K Scientific/Educational	£995
PC1211 — Pocket Computer	£69
PC1500 — New Pocket Computer	£145

*Full range of Sharp peripherals available. Also software and consumables.
 All prices exclude delivery and VAT.

*We will take your MZ80K in part exchange subject to condition.

M S Consultants (Cambridge) Ltd.

152 High Street
 Huntingdon PE18 6TF
 Telephone: (0480) 51721

51 Canterbury Street
 Cambridge CB4 3QG
 Telephone: (0223) 521192



OK1-PRINTER OFFER

£260

plus VAT
Serial Interface
£85+VAT

OKIDATA

£399

plus VAT
Dual Interfaces

ORDER FORM

Printer Required	Tick here	Cash Price	Credit Charge	Credit Price
Microline 80	<input type="checkbox"/>	£299.00	£29.90	£328.90
Microline 80+ serial I/F	<input type="checkbox"/>	£367.75	£39.68	£436.43
Microline 82A	<input type="checkbox"/>	£458.85	£45.89	£504.74

Name Tel (day)

Address
 Cash Customers — enclose cheque/purchase order for full amount which includes VAT/Delivery by Securicor.
 Delivery — Cash customers allow 10 days. Credit customers allow 14 — 21 days.

MICROLINE 82A

Standard Features

- 80 cps
- 80 columns with standard characters
- 132 columns with condensed characters
- Graphics
- 200,000,000 character head warranty
- Connects to TRS 80™, APPLE®, others
- Continuous operation
- Plain paper — up to 3 parts
- Full 96 character ASCII set
- Double width characters
- 6 and 8 lines per inch
- Paper tear bar

- Operates with TRS 80™, APPLE®, others
- Plain paper — up to 4 parts
- Full 96 character ASCII set
- Double width characters
- 6 and 8 lines per inch
- Paper tear bar

DEFERRED PAYMENT SCHEME

Spread the cost of your Microline printer over 11 months! Credit customers pay only 10% extra (equivalent APR 23.4%). Complete order form and send with cheque for first monthly payment as deposit. We will send you a simple Musters Finance loan form. When you complete and return it, we will send your printer!

Microline 80	only £29.90 p.m.
Microline 80+ ser. I/F	only £39.68 p.m.
Microline 82A	only £45.89 p.m.

MAIL TO: JSP COMPUTERS, 18 HAMILTON ROAD, NOTTINGHAM

MAKE SURE OF GETTING YOUR COPY! HAVE IT DELIVERED EVERY MONTH

"Electronics & Computing Monthly" has become required reading for thousands of Engineers, Technicians, Managers, Company Directors, Teachers, University Lecturers and Students plus many other electronics and computing enthusiasts.

The magazine has a unique blend of theory, projects, software and technical features supported by technology updates — science and general features on a wide variety of high technology topics.

If science, electronics and computing are your areas of interest then you can guarantee a good read in "Electronics & Computing Monthly". Special product features each month will combine interesting articles on a particular product theme with special promotions by advertisers. Special products on offer will beat all others on price. Scopes, digital multimeters and home computers are among the variety of goods which will be available at new low prices throughout the year.

Please send Electronics & Computing Monthly for the next 12 issues to commence from Issue.

I have enclosed a cheque/Postal order for £9.50

Name

Address

Town

(Free Post No Stamp Needed)

ELECTRONICS & COMPUTING

SUBSCRIPTIONS DEPT

(FREEPOST)

76 High Street Daventry
Northants NN11 4BQ.

ELECTRONICS & COMPUTING

MONTHLY

classified

FOR SALE

ZX81 KEYBOARD SOUNDER. made from easily obtained components, send £3 for instructions, p.c.b. and transducer or s.a.e. for details to R. Mitchell, 20 Gorse Close, Portslade, Sussex. (090309)

AMAZING ELECTRONIC PLAN LASERS — Superpowered, cutting rifle, Pistol, Light Show, Ultra Sonic force-field, Pocket Defence Weaponry, Giant Tesla, Satellite TV, Pyrotechnics, 150 More Projects — Catalogues 95p from Plancentre, 16 Mill Grove, Bilbrook, Codshall, Wolverhampton. (EC08)

VISIT THE COMPUTER JUNK SHOP S.A.. leaflet 10 Waterloo Road, Widnes, Cheshire. WA8 0PY (0907 T/C)

HEX KEYBOARDS. Supplied with 20 keys, full click action, coloured, p.c. board. £10.50. Details. Kitswitch, 31 Ellensbrook Lane, Hatfield, Herts. Tel. Hatfield 63953.

5K ZX81 EXPANSION. Expand your Sinclair to 5K, write programs over 25 times bigger. Best value memory available. £19 including fast-action "Break-out" on cassette. M. A. McNair, 13 Oxford Close, Berkhamsted, Herts. HP4 3NE.

LOGABAX 180 MATRIX PRINTER. 180 characters per second. Data flow control and large buffer. Upper and lower case and italics-£190.00. Phone Northampton 36953.

VIDEO GENIE EG3003. Under six months old, complete with original manuals and packaging. Plus lots of software. Price new, including software, approx. £380. Bargain at £250. Luton (0582) 391857, after 6 p.m.

UK101 ARCADE SOFTWARE MINI PUCK-MAN. Breakout and Defender. £3 each, 3 for £5. C. Duff, 1 Ulceby Road, Riddings, Scunthorpe, South Humberside.

ZX81 SINCLAIR BUILT. Only four months old, five books plus loads of mags and software. Good condition, (worth £95), £60 o.n.o. Phone 01-764-8657.

BBC MICRO CASSETTE of four games: Fruit Machine/Depth Charge/Hangman/Code-breaker. £6. Also cassette of eight 16K ZX81 programs including Bank Account, Two Adventures and Codebreaker. Just £5. R. Shperherd, 22 Green Leys, Alderbury Road, Maidenhead, Berks.

MZ80K HORSE RACE ANALYSIS. Winners galore. A serious program. Not a game. Cassette: £5.75. Details: paragon, "Moorside", Woodlands, Wimborne, Dorset.

ZX81 PLUS LARGE KEYBOARD and two books worth £125. Bargain only £50. Tel-061-6812875. 1 Duxford Walk, Moston, M10 9JN.

ZX81, 16K RAM. Books and mags. Masses of programmes, power supply. All perfect condition. Price £130 o.n.o. Phone Corin 722-8450.

VIC 20 plus cassette deck, almost new, £210 the lot. **CBM/PET 4016** plus cassette deck, almost new, £435 o.n.o. Part exchange also considered. Telephone (05827) 66026.

**Send to:-
ECM CLASSIFIED, 67 HIGH STREET, DAVENTRY, TEL: 03272 71841**

RATES

1-3 insertions £7 per scc
4-11 insertions £6.50 per scc
12 insertions £6 per scc
24p per word (min. 15 words)
Box No. on application
All advertisements in this section must be pre-paid.

CLOSING DATE

25th day of each month preceding publication date.
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

VIDEO MONITOR 12" B & W. Plastic cased Sharp picture approx. three months old. Only £40 Phone Chelmsford, 440520.

TELETYPE KSR33 PRINTER. Excellent Condition. RS232 Interface. Demo on Nascom 2. £95. Keyboard plus case. 80 Keys £10. Crowtherne 6894.

ATOM EXPANSION DACN £80 ONO Apple II programs on disk £15 2x Spectram software S.A.E. J.M. Bonnett, Morcroft, Rhosneigr, Gwynedd. LL645 JL.

ZX81 16K RAM. Full size keyboard manual all leads, 4 cassettes, 3 months old. Phone Caterham 49664. Price £105.

MICROTAN 65. With new V2.3 Monitor, Keypad, Graphics option and Space Invasion ROM. Any offers (021) 523-0733 after 5.00 pm.

ZX81 PLUS 16K RAM PACK. Complete with P.S.U., manual, connectors, 2 books, 4 games tapes, excellent condition, under guarantee. £95. Phone Strathaven 21221.

UK101 8K. Uncased, complete with manual, £40, game tapes, also Prog Sound Generator unfinished, £180.00. Home No. 01-699-1146. Office 01-693-9961.

DIGITAL WATCH REPLACEMENT Parts, batteries, displays, backlights, etc. Also reports, publications, charts. SAE for full list. Profords, Copnersdrive, Holmergreen, Bucks HP15 65GB.

ATOM UTILITY ROM £19.95

The Willow Software 4K Utility ROM simply plugs into the spare utility socket in your Atom and provides 18 powerful new commands and facilities including: Full renumber, Range Delete, Find, sophisticated Auto line numbering, Program compression, Disassembler, true Keyboard Scanning, Memory Dump, Variable Dump, Register Dump, Keyboard sounder and much more. The Utilities are professionally written and fully tested. All standard Atom facilities are unaffected, and no textspace memory is used. Send cheque/PO for £19.95 for delivery by return of post, or write for further details.

**WILLOW SOFTWARE
PO BOX 6, CREDITON,
DEVON EX17 1DL.**

ZX SOFTWARE

ZX8D 16K. Asteroids and Galaxy Invaders £4.99; Space Invaders and Missile Command £4.99; all four £7.95 with Defender Free! All games on cassette. Cassette with listings. R. Bhattacharya, 3 Wensley Close, Harpenden, Herts.

1K ZX81 CHESS. Machine code program. Display shows computer test legal moves and take best. Flicker free on cassette. £5. D. R. Horne, 126 Southridge Rise, Crowborough, Sussex.

SUPERIOR JOYSTICK FOR ZX81. Do-it-Yourself, firebutton, construction from about £2. Full details send £1.30. Thompson, 8 Sharpen Drive, Leek, Staffs.

SINCLAIR ZX81 (16K) EDUCATIONAL SOFTWARE. G.C.E. "O" Level French: 3 Grammar programs + 3 Vocabulary programs. G.C.E. "O" Level Maths: 1 Teach & Test program + 2 programs of generated "O" level questions. Junior Maths: 12 programs on 2 cassettes. Junior English: 12 programs on 2 cassettes. Education Quiz: 4 programs covering General Knowledge, Reasoning, Maths & English. £4.50 per cassette or send s.a.e. for catalogue to: Rose Cassettes, 148 Widney Lane, Solihull, West Midlands B91 3LH.

BUSINESS GAMES ZX81 16K. "AUTOCHEF" As MD you must negotiate for leases, decide on menu prices, level of wages, advertising and dividends and forecast levels of inflation. If you are not successful you will be, made to resign! "AIRLINE" You must decide on number of aircraft to operate, loan and fuel contracts, whether to buy or charter, and levels of staffing and maintenance. "PRINTSHOP" Operate a Print company, decide on level of staff and stock, schedule work through print shop, quote for jobs and see results in P & L and Cash Flow Statements. £4.75 each, £8.00 for two or £11.50 for three. C.C.S., 14 Langton Way, London SE3 7TL. Tel. 01 858 0763.

ZX81 ACCOUNTS. Budget your spending. Saves Datafiles separately from program. Cassette (16K). £3.45. Dataprint, provides equivalent of data and print using statements. M/C code. Cassette. £2.50. A. N. Wilson, The Vicarage, Whitworth Square, Rochdale, Lancs. OL12 8PY.

ZX81 16K: Lair — adventure game. Full 16K used. Plenty of action. Plus detective game of logic. (2-4 players). Both on cassette. £3.50. S. Taylor, 2 Greenway, Eltham, London SE9 5SZ.

ZX81 PROGRAMMING AID. Audible keypress indicator component cost £4. Send £1 + s.a.e. for plans. Bell, 17 Beaumont Vale, Havelland, Suffolk.

SPECTRUM - ZX81

JOIN

ZX - GUARANTEED

(Newsletter Club now exclusively for Spectrum & ZX81)

All items/listings guaranteed error free.

ZX - GUARANTEED is intended to be educational to the user. Includes Games/Programs, Articles on Peek, Poke, Machine Code, Program Techniques, Hints & Tips, etc.

Club is ran April to April. If joining late, all current years back issues sent.

Membership £5 per year Europe £6.50 Others £11
(Can only accept Sterling Drafts from overseas).

Sample back issue (for ZX80/81) £1 plus s.a.e.

Now ready — *Super Graphic Action Packed 16K Game Cassette* (called VENTURE) for ZX81 £5
With colour/sound for Spectrum £6

G. A. BOBKER

29 CHADDERTON DRIVE, UNSWORTH, BURV, LANCS BL9 8NL
Telephone: 061-766 5712

YOUR QUICK-LEARN WAY TO PROGRAMMING OR ENGINEERING

IN YOUR OWN HOME,
IN YOUR OWN TIME,
AT YOUR OWN PACE.

Learn computer programming quickly and easily through the renowned ICS "Open College" system, taking the course at your own pace and in your own time.

Use the famous ICS study texts, backed up by your own expert tutor, and learn computer programming, the proven way, with ICS home study.

Courses:

Introduction to Computer Programming


Programming in BASIC
Programming in COBOL

The ICS School of Electronics offers home study courses in:

Basic Electronic Engineering

Computer Engineering

Microprocessors

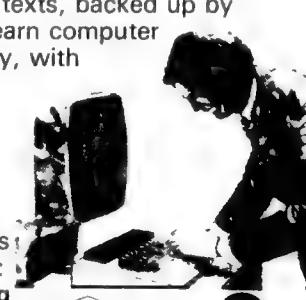

CACC Approved by CACC Member of ABCC

ALL DETAILS FREE—SIMPLY RETURN THE COUPON BELOW

PLEASE SEND ME YOUR PROSPECTUS ON

COMPUTER PROGRAMMING
ELECTRONICS - PLEASE TICK



Name _____

Address _____

Post to: Dept 348W

ICS School of Computer Programming
160 Stewarts Road,
London SW8 4UJ

DIV. NATIONAL
EDUCATION
CORPORATION



ZX81/SPECTRUM WORKSTATION



... IS A STYLISH AND ERGONOMIC PLINTH FOR THE SINCLAIR ZX81, WHICH RAISES AND TILTS THE TV TO AVOID EYESTRAIN, HOLDS THE 16K RAM FIRMLY AND HAS ROOM BEHIND FOR WIRING, POWER SUPPLY AND EXTRAS. MODEL 1 IS SHOWN HERE, WHICH COSTS £15. MODEL 2 HAS SPACE FOR THE PRINTER AND COSTS £16, AND MODEL 3 FEATURES A FULL SIZE KEYBOARD AT £44 FULLY BUILT. A VERSION TO SUIT THE NEW SPECTRUM IS DUE SOON AT £16.00.

TWO EXTRAS ARE AVAILABLE — A POWER SWITCH AT £3 AND AN ALLOY FLOOR, WITH FIXINGS, FOR £3.50.

PRICES INCLUDE VAT, BUT POSTAGE IS £2.00 EXTRA.

EXPORT AND TRADE WELCOME ANSWERPHONE SERVICE.

VISA AND ACCESS ACCEPTABLE

PETER FURLONG PRODUCTS
UNIT 5, SOUTH COAST ROAD INDUSTRIAL
ESTATE, PEACEHAVEN, E. SUSSEX.
TEL. (07914) 81637.

Sumlock

Manchester



microcomputer world

SHARP

First and foremost

MZ-80 A



MZ 80A 48K COMPUTER £549.00 (inc VAT)*

THE NEW FULL KEYBOARD COMPUTER FROM SHARP

*COMPLETE WITH SOFTWARE PACK:

EDUCATION-HANGMAN, GEOGRAPHY, ARITHMETIC

GAMES-LUNAR LANDER, TEN-PIN BOWLING,

SPACEFIGHTER, IDENTIKIT, CLEVER CRIBBER

D-DAY, BREAKOUT, STAR TREK, SCRABBLE,

SPACE INVADERS

HOME FINANCE - HOME BUDGET, BANK RECOUL,
BANK LOAN, MORTGAGE

BASIC TUTORIAL - BASIC TUTORIAL 1

- BASIC TUTORIAL 2

- BASIC TUTORIAL 3

- BASIC TUTORIAL 4



TWO YEAR WARRANTY ON SHARP HARDWARE parts and labour

Computer books now in stock

commodore

THE HOME COMPUTER

by commodore

VIC 20



still
only
£189.95 INC VAT

		(inc. VAT)
VIC 1530	cassette deck	44.95
VIC 1515	printer	230.00
VIC 1540	single floppy drive	396.00
VIC 1210	3K ram cartridge	29.95
VIC 1110	8K ram cartridge	44.95
VIC 1111	16K ram cartridge	74.95
VIC 2501	introduction to basic (1)	13.95
VIC 1906	Alien ROM game	19.95
VIC 1907	Super Lander ROM game	19.95
VIC 1904	Super Slot ROM game	19.95
VIC 1212	Programmers Aid Cartridges	34.95
VIC 1211A	Super Expander Hi Res Cartridge	34.95
VIC 1213	Machine Code Monitor Cartridge	34.95
VIC 1311	Joystick	7.50
VIC 1909	Road Race ROM Game	19.95

audiogenie stockist

COMPLETE LIST OF HARDWARE AND SOFTWARE AVAILABLE BY REQUEST

We only advertise what we have in stock at the time.

All items are ex stock. Telephone/mail order
despatched within 24 hours. Carriage free U.K. mainland



keep up to date
join our free mailing list

Sumlock Manchester
Dept MC1
Royal London House
198 Deansgate
Manchester
M3 3NE

OPEN MONDAY TO SATURDAY
PARKING WATSON ST. N.C.P.

061 834 4233

MAPLIN the people for Atari



3 Consoles available:

Atari 400 with 16K RAM	(AF36P)	£299
Atari 400 with 32K RAM	(AF37S)	£395
Atari 800 with 16K RAM	(AF02C)	£599

AF36P and AF02C special price for limited period only

Lots of other hardware:

Cassette Recorder	(AF28F)	£50.00	16K RAM Module	(AF08J)	£65.00
Disk Drive	(AF06G)	£345.00	32K RAM Module	(AF44X)	£125.35
Thermal Printer	(AF04E)	£265.00	32K Upgrade for 400	(AF45Y)	£75.00
Printer Interface for 400	(AF41U)	£59.95	Floppy Disk	(YX87U)	£2.75
Printer Interface for 800	(AF42V)	£59.95	Le Stick	(AC45Y)	£24.95
Interface Module	(AF29G)	£135.00	Joystick Controllers	(AC37S)	£13.95
Versawriter	(AF43W)	£169.00	For full details ask for our hardware leaflet	(XH54J)	SAE appreciated



NOW YOU CAN JOIN THE U.K. ATARI COMPUTER OWNER'S CLUB. An independent user's group.

Four issues of the club magazine for only £1.60! Address your subscription to Ron

THE CHOICEST GEMS OF ATARI SOFTWARE FROM MAPLIN

Adventure Games

Star Warrior	-C-32K-(BQ24B)	£28.95
Rescue At Rigel	-C-32K-(BQ21X)	£22.45
Invasion Orion	-C-32K-(BQ23A)	£18.95
Datestones of Ryn	-C-32K-(BQ22Y)	£14.95
Galactic Empire	-C-24K-(BQ14Q)	£14.95
Hi Res Adventure //2	-D-48K-(BQ25C)	£24.95
Analog Adventure	-D-32K-(BQ33L)	£24.95
Adventure Land	-C-24K-(BQ00A)	£14.95
Pirates Adventure	-C-24K-(BQ01B)	£14.95
Mission Impossible	-C-24K-(BQ02C)	£14.95
Voodoo Castle	-C-24K-(BQ03D)	£14.95
The Count	-C-24K-(BQ04E)	£14.95
Strange Odyssey	-C-24K-(BQ05F)	£14.95
Mystery Fun House	-C-24K-(BQ06G)	£14.95
Pyramid of Doom	-C-24K-(BQ07H)	£14.95
Ghost Town	-C-24K-(BQ08J)	£14.95
Savage Island I	-C-24K-(BQ09K)	£14.95
Savage Island II	-C-24K-(BQ10L)	£14.95
Golden Voyage	-C-24K-(BQ11M)	£14.95
Energy Czar	-C-16K-(YGS3H)	£9.95
Kingdom	-C-8K-(YGS5M)	£9.95

Teach-Yourself Programs

Conversational French	-SC-16K-(YG44X)	£39.95
Conversational German	-SC-16K-(YG45Y)	£39.95
Conversational Spanish	-SC-16K-(YG46A)	£39.95
Conversational Italian	-SC-16K-(YG47B)	£39.95
Touch Typing	-2C-16K-(YQ49D)	£15.95
States & Capitals	-C-24K-(YQ56L)	£9.95
European Countries & Capitals	-C-16K-(YQ57M)	£9.95
Learn Programming	-C-8K-(YQ43W)	£15.95
Invitation to Programming	-C-32K-(BQ57M)	£9.95
Basics of Animation	-D-32K-(BQ58N)	£10.95
Player Missile Graphics	-C-16K-(BQ59P)	£18.95
Player Missile Graphics	-D-24K-(BQ60D)	£19.95
Display Lists	-C-16K-(BQ51F)	£9.95
Display Lists	-D-24K-(BQ52G)	£10.95
Horiz / Vertical Scroll	-C-16K-(BQ53H)	£9.95
Horiz / Vertical Scroll	-D-24K-(BQ54J)	£10.95

Send see now for our new software leaflet with details of all the above programs. Order As XH52G — Issue 2.

Subscribe now to America's leading Atari-only magazine — Analog — 6 issues per year for just £9.00. Order as GG24B.

New titles this month

Learn Programming:

Invitation to Programming 2 - C-16K-(BQ67X) £22.95
Invitation to Programming 3 - C-16K-(BQ68Y) £22.95

Business Programs:

Personal Financial Management - D-32K-(BQ65V) £49.00
Mortgage and Loan - C-16K-(BQ66W) £13.95

Arcade Games:

Caverns of Mars	-D-32K-(BQ69A)	£24.50
Centipede	-E-16K-(BQ70M)	£29.95
Pac-Man	-E-16K-(BQ71N)	£29.95
K-Razy Shoot Out	-E-16K-(BQ63T)	£29.95
Mous kattack	-D-32K-(BQ77J)	£26.95
Ghost Hunter	-C-16K-(BQ64U)	£24.50
Galactic Chase	-D-32K-(BQ61R)	£17.95
Galactic Chase	-C-16K-(BQ62S)	£15.95

Home Programs:

Video Easel - E-16K-(BQ72P) £24.50

Computer Languages: Microsoft Basic - D-32K-(BQ74R) £59.95
Pilot (Educator) - E-8C-16K-(BQ75S) £79.95

Utilities: Macro Assembler - D-32K-(BQ73Q) £59.95
K-DOS (Superior disk operating system) - D-32K-(BQ76H) £53.95

Key C = Cassette, D = Disk, E = Cartridge,
2C = 2 Cassettes etc. 8K, 16K etc. shows
minimum memory requirement.

Maplin Electronic Supplies Ltd
P.O. Box 3, Rayleigh, Essex.
Tel: Southend (0702)
552911/554155.

MAPLIN

Note: Order codes shown in brackets

Prices correct at time of going to press

(Errors excluded)

Demonstrations at our
shops NOW
See Atari and Vic in action at
159-161 King St., Hammersmith W6
Tel: 01-748 0926
or at 284 London Road,
Westcliff-on-Sea, Essex.
Tel: (0702) 554000

Who takes care of your EPROMS?

... WE DO!



CONTROLS

- 24 key pad includes hexadecimal keyboard and function keys.
- 12 address LED's.
- 4-function LED's (error, prog, ok and size).
- 2 hexadecimal displays.

**Assembled £270
Kit Form £180**

Prices exclude V.A.T.

TECHNICAL INFORMATION

- power supply: 220/110V AC 50/60 Hz
- supply current: typ 70mA/220V
150mA/110V
- 2K byte STATIC RAM STANDARD
(expandable to 4K byte)
- microprocessor controlled
- CMOS/TTL LOGIC
- Textool test socket

MECHANICAL SPECIFICATIONS

- length: 420mm
- depth: 190mm
- height: 78mm
- weight 3.75Kg

MICROPROCESSOR CONTROLLED EPROM PROGRAMMER


Qualified by INTEL and new to the UK, Velleman UK, are offering you their K2578 EPROM programmer. This compact unit is complete with the power supply and available assembled or in kit form.

The K2578 will test, verify, copy and programme the following EPROMS with **No need for any other personality module** — 2716 (Intel or equivalent) - 2732 (Intel or equivalent - 2732A (HMOS version of Intel) and TMS2516 (Texas Instruments).

Ideal for industry, repair shops, schools or the home enthusiast, the K2578 works independently and has no specific relation with any development system.

FUNCTIONS

- blank test
- verify test
- program with automatic blank and verify test
- input or modify data in user RAM at any desired address
- load RAM function to fill the RAM area with data from a preprogrammed PROM to perform a copy
- Parallel load capability from a DMA controlled RAM field
- size selection (16/32K) with single push-button
- OK indication for successful executed functions
- ERROR indication with error codes on display
- blank error
- verify error
- illegal address access error
- increment function which stores the input data via hex. keyboard and jumps to the next address in user RAM
- reset

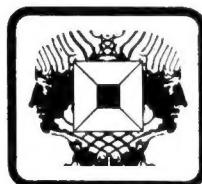

VELLEMAN UK. Limited

P.O. Box 30, St. Leonards-on-Sea, East Sussex TN37 7NL Tel : Hastings (0424) 753246

OLIVETTI JOIN THE THRONG

This time next year we should be knee deep in 16-bit micros if they continue being launched at the present rate. Olivetti, have announced it will make its entry into the small business and personal computer markets this year with its model M20, 16-bit, Z8001 based computer. This will provide 128K of RAM and one or two built-in mini floppies. The price of the machine is expected to be around 3000 dollars in the USA where it is initially being launched.

Information technology awareness programme

This is the first in a series of articles covering the Information Technology Awareness Program which is designed to run for three or four years. The first year coincides with Information Technology Year. This is being organised via the efforts of IT82 Ltd. which is jointly funded by the Department of Industry. This program is intended to increase the awareness of new technology, in particular that associated with the recording, access and use of information. There has been defined three basic target populations with objectives of:

1. Increasing efficiency by full utilisation of new technology, i.e. incorporating micro chips into more products. Closely akin to this is the use of micro-processors in industry. This is still of great interest to the DfI as indicated by their Microprocessor Application Project.
2. Causing people in design and creative areas to look at new ways to use micro chips and to evolve new industries around them.

Third Commodore Computer Show

The third Commodore computer show will be held at the Cunard Hotel, Hammersmith, London between 3rd and 5th June 1982. It will be their biggest to date with over 100 exhibitors and is expected to attract 20,000 visitors. A complete range of Commodore's new machines will be on display including the Ultimax, Vic 40, Commodore 64 and the CBM 128 and 256 machines. These new products should add a bit of fuel to the already fired-up 16 bit computer market, plus making the choice of buying a personal computer in 1982 that much more difficult.

3. Bringing more information to the general public and improving their access to this information. (Teletext and Prestel for example).

Various events; exhibitions, competitions etc. are being organised to support IT. This column will be giving further information about the project and events over the next few months.

E Midlands Inter-County Schools Business Competition

Five schools from each East Midlands County (Notts. Derbys. Lincs. Leics. Northants.) are being invited to participate in a business competition. A postal competition will decide the county champions who will each receive a prize of a prestel adaptor donated.

\$1 Billion Investment Japanese Gear up for Mass Production

Luton, England . . . Japan's Top 20 semiconductor manufacturers invested a staggering \$1 billion on new semiconductor plant and equipment in 1981, and are poised to spend the same amount again in 1982 as the Japanese industry gears up for mass production of VLSI devices, claims a report now available from Mackintosh.

The report, 'Semiconductor/Microelectronics Industry in Japan' reveals that, collectively, Japan's Top 20 semiconductor manufacturers are spending 20% of their annual sales value on investment in production facilities alone, excluding Research and Development expenditure.

The cost of setting up a typical LSI production line with a monthly output of 1 million units of 16K bit memory is approximately \$18.4 million. This sum, states the report, is approximately half the cost required to set up a similar production line manufacturing 64K bit memory, which it claims the Japanese industry will commence mass production in 1982.

The market leader, NEC, is steadily increasing its investment in production capacity; investment accounted for 24% of semiconductor sales in 1981, compared with 22% in 1980 and 19% in 1979. Other manufacturers are taking even bigger gambles, with Oki Electric, ranked 11th largest manufacturer in Japan, spending a colossal 62% of its semiconductor sales revenue on capital expenditure in 1981,

valued at over \$63 million. Fujitsu spent over 44% of its semiconductor revenues on investment in 1981, Sharp 35% and Sony 55% (but for these three, 40-50% of output is for internal use).

US suppliers are also announcing firm plans to join Texas Instruments, the only foreign manufacturer in Japan, with both Intel and Motorola expected to be in full production after 1983 and IBM will also have its own internal facility from 1983, currently being constructed at its main Yasu plant.

With regard to overall growth of output Japanese production of Integrated Circuits is expected to expand at 12% per annum 1981-6, compared with 29% per annum between 1976-81, when growth rates were higher starting from a much lower base level. Total Japanese IC output (excluding Hybrids) in 1981 was approximately \$3bn, and is expected to rise to \$5.2bn in 1986, when the overall Semiconductor Industry (Discretes + ICs + Hybrids) will produce some \$8.3bn worth of devices, compared with \$5bn in 1981, at an average annual growth rate of 10.5%.

'Semiconductor / Microelectronics Industry in Japan' has been prepared by Yano Economic Research Institute Co. Ltd., Tokyo and comprises 217 pages, over 100 exhibits, size 280mm x 210mm and is available from Mackintosh Publications Limited, Luton.